


Biassing Bipolar Junction Transistors

Al Ward

W5LUA

January 31, 2007

Various BJT Biasing Networks

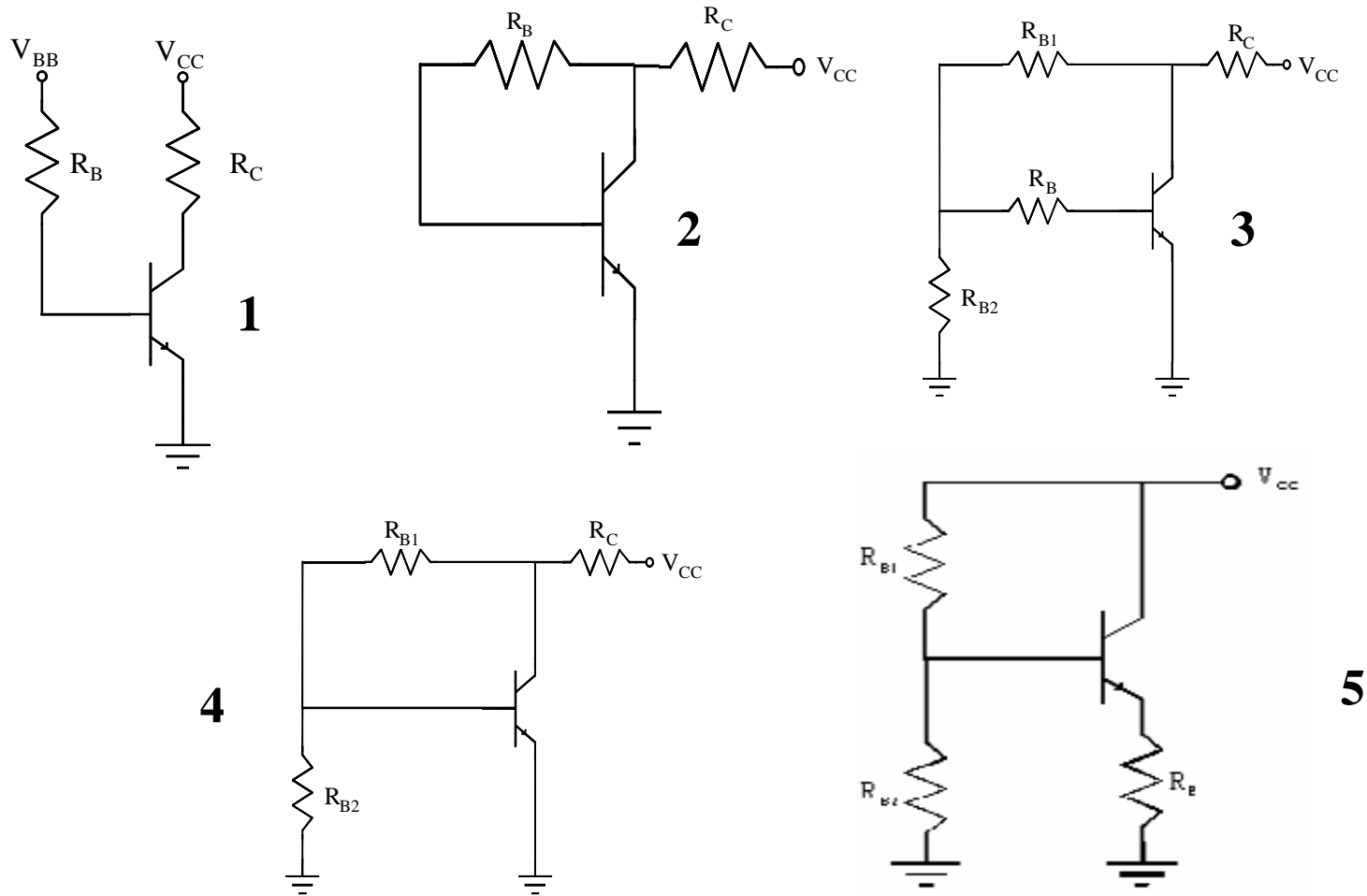

AT-41486


Electrical Specifications, $T_A = 25^\circ\text{C}$

Symbol	Parameters and Test Conditions	Units	Min.	Typ.	Max.
$ S_{21E} ^2$	Insertion Power Gain; $V_{CE} = 8\text{ V}$, $I_C = 25\text{ mA}$	$f = 1.0\text{ GHz}$ $f = 2.0\text{ GHz}$		17.5 11.5	
$P_{1\text{ dB}}$	Power Output @ 1 dB Gain Compression $V_{CE} = 8\text{ V}$, $I_C = 25\text{ mA}$	$f = 2.0\text{ GHz}$		18.0	
$G_{1\text{ dB}}$	1 dB Compressed Gain; $V_{CE} = 8\text{ V}$, $I_C = 25\text{ mA}$	$f = 2.0\text{ GHz}$		13.5	
NF_O	Optimum Noise Figure; $V_{CE} = 8\text{ V}$, $I_C = 10\text{ mA}$	$f = 1.0\text{ GHz}$ $f = 2.0\text{ GHz}$ $f = 4.0\text{ GHz}$		1.4 1.7 3.0	1.8
G_A	Gain @ NF_O ; $V_{CE} = 8\text{ V}$, $I_C = 10\text{ mA}$	$f = 1.0\text{ GHz}$ $f = 2.0\text{ GHz}$ $f = 4.0\text{ GHz}$	17.0	18.0 13.0 9.0	
f_T	Gain Bandwidth Product; $V_{CE} = 8\text{ V}$, $I_C = 25\text{ mA}$			8.0	
h_{FE}	Forward Current Transfer Ratio; $V_{CE} = 8\text{ V}$, $I_C = 10\text{ mA}$		30	150	270
I_{CBO}	Collector Cutoff Current; $V_{CB} = 8\text{ V}$				0.2
I_{EBO}	Emitter Cutoff Current; $V_{EB} = 1\text{ V}$				1.0
C_{CB}	Collector Base Capacitance ^[1] ; $V_{CB} = 8\text{ V}$, $f = 1\text{ MHz}$			0.25	

Note:

1. For this test, the emitter is grounded.

Bipolar Transistor Bias Network Analysis

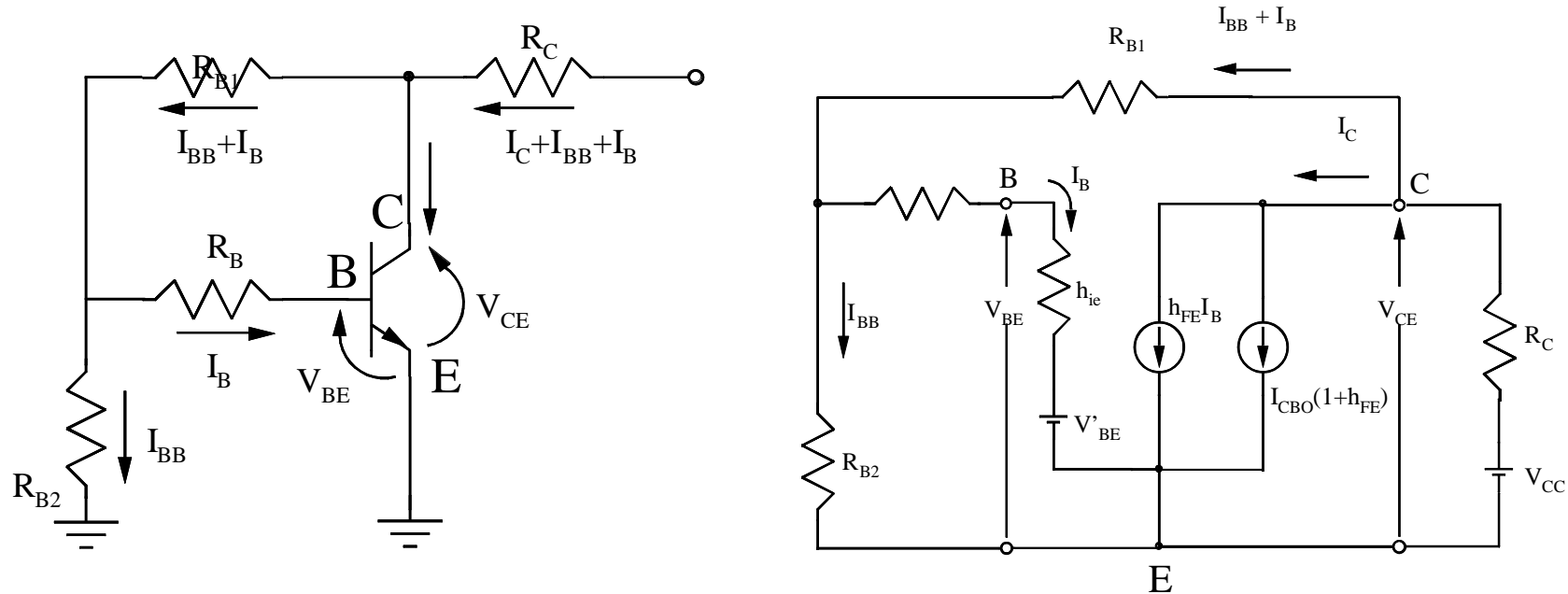

A. Bias circuit showing only the DC components.

B. The equivalent circuit of figure A used in DC stability analysis.


$$I_C = h_{FE} I_B + I_{CBO} (1+h_{FE})$$

- where h_{FE} is the DC current gain of the transistor and I_{CBO} is the current flowing through a reverse biased PN junction.

$$V_{BE} = V'_{BE} + I_B h_{ie}$$

- where V'_{BE} is internal to the transistor and h_{ie} is the equivalent Hybrid Π input resistance of the transistor and is equal to $h_{FE} / (\lambda I_C)$ where $\lambda=40$ @ +25 degrees C. h_{ie} is generally much smaller than R_b

Temperature Sensitive Parameters

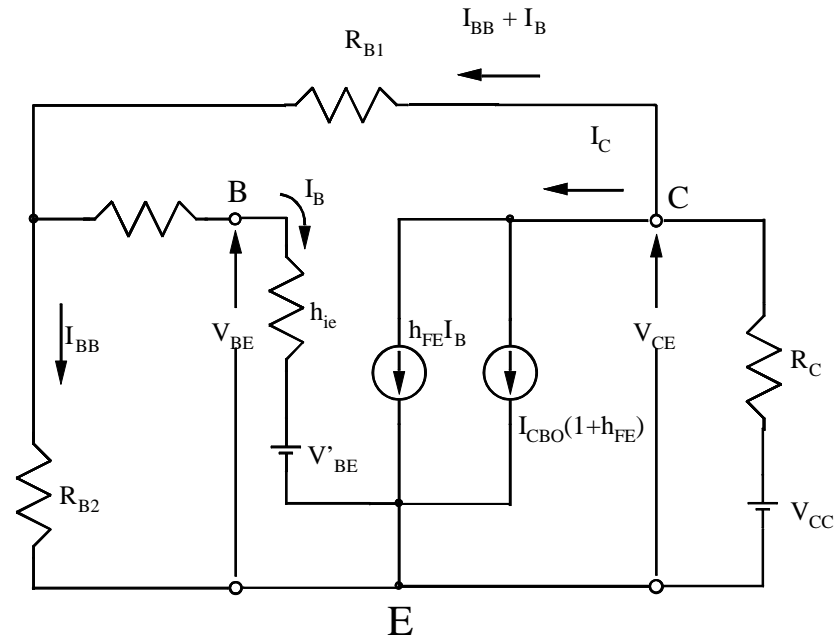

The equivalent circuit of the voltage feedback and constant base current source bias network used in DC stability analysis.

$$V'_{BE}, h_{FE}, I_{CBO}$$

V'_{BE} has a typical negative temperature coefficient of $-2\text{mV}/^\circ\text{C}$.
 h_{FE} typically increases with temperature at the rate of $0.5\%/^\circ\text{C}$.
 I_{CBO} typically doubles for every 10°C temperature rise.

Non-Stabilized Bias Network #1


$$V_{CC} = V_{BB} = 2.7V, V_{CE} = 2V, I_C = 5 \text{ mA}, h_{FE} = 80, 50 \text{ min}, 150 \text{ max}$$

$$V_{BE} = 0.78 \text{ V}, I_{CBO} = 1 \times 10^{-7} \text{ A @ } +25 \text{ deg C}$$

$$R_B := \frac{V_{CC} - V_{BE}}{I_B} \quad R_C := \frac{V_{CC} - V_{CE}}{I_C}$$

$$R_B = 30770 \text{ ohms}$$

$$R_C = 140 \text{ ohms}$$

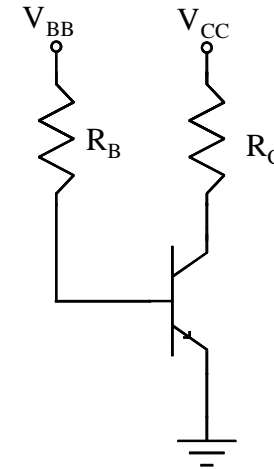

Non-Stabilized Bias Network #1

$$V_{CC} = V_{BB} = 2.7V, V_{CE} = 2V, I_C = 5 \text{ mA}, h_{FE} = 80, 50 \text{ min}, 150 \text{ max}$$


$$V_{BE} = 0.78 \text{ V}, I_{CBO} = 1 \times 10^{-7} \text{ A @ } +25 \text{ deg C}$$

$$I_C := \frac{h_{FE} \cdot (V_{CC} - V_{BE})}{(h_{ie} + R_B)} + I_{CBO} \cdot (1 + h_{FE})$$

Based on h_{FE} alone

$$I_C \text{ max} = 9.27 \text{ mA}$$

$$I_C \text{ min} = 3.14 \text{ mA}$$

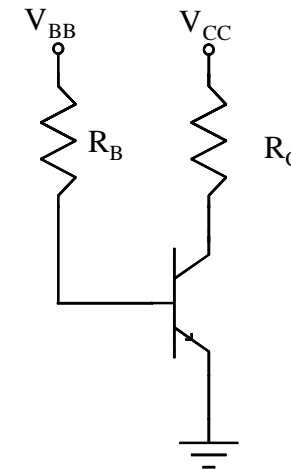


Voltage Feedback Bias Network #2

$$V_{CC} = 2.7V, V_{CE} = 2V, I_C = 5 \text{ mA}, h_{FE} = 80, 50 \text{ min}, 150 \text{ max}$$

$$V_{BE} = 0.78 \text{ V}, I_{CBO} = 1 \times 10^{-7} \text{ A @ } +25 \text{ deg C}$$

$$R_B := \frac{V_{CE} - V_{BE}}{I_B} \quad R_C := \frac{V_{CC} - V_{CE}}{I_C + I_B}$$
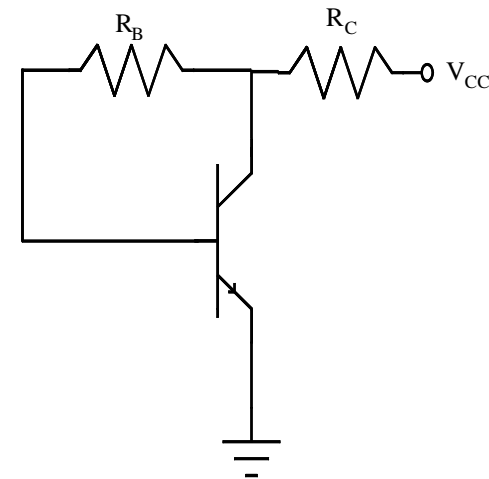
$$R_B = 19552 \text{ ohms} \quad R_C = 138 \text{ ohms}$$



Voltage Feedback Bias Network #2

$$V_{CC} = 2.7V, V_{CE} = 2V, I_C = 5 \text{ mA}, h_{FE} = 80, 50 \text{ min}, 150 \text{ max}$$


$$V_{BE} = 0.78 \text{ V}, I_{CBO} = 1 \times 10^{-7} \text{ A @ } +25 \text{ deg C}$$

$$I_C := \frac{h_{FE} \cdot (V_{CC} - V_{BE}) + I_{CBO} \cdot (1 + h_{FE}) \cdot (h_{ie} + R_B + R_C)}{h_{ie} + R_B + R_C \cdot (1 + h_{FE})}$$

Based on h_{FE} alone

$$I_C \text{ max} = 7.09 \text{ mA}$$

$$I_C \text{ min} = 3.63 \text{ mA}$$

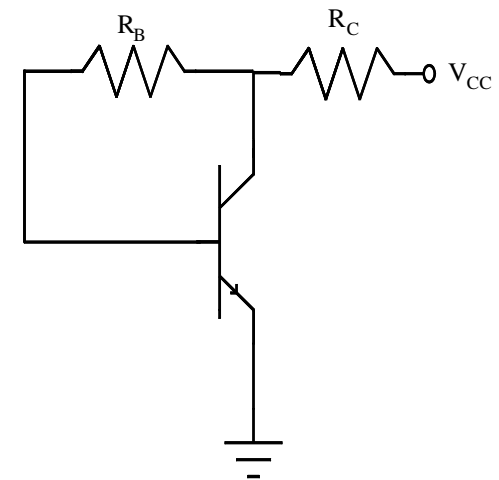

Voltage Feedback and Constant Base Current Source Bias Network #3


$$V_{CC} = 2.7V, V_{CE} = 2V, I_C = 5 \text{ mA}, h_{FE} = 80 \text{ typ}, 50 \text{ min}, 150 \text{ max}$$

$$V_{BE} = 0.78 \text{ V}, I_{CBO} = 1 \times 10^{-7} \text{ A @ } +25 \text{ deg C}$$

Choose V_{RB2} , in which $V_{CE} > V_{RB2} > V_{BE}$. Suggest a V_{RB2} of 1.5V
Suggest a voltage divider current of .5mA.

$$R_C := \frac{V_{CC} - V_{CE}}{I_C + I_{B2} + I_B} \quad R_B := \frac{V_{RB2} - V_{BE}}{I_B}$$
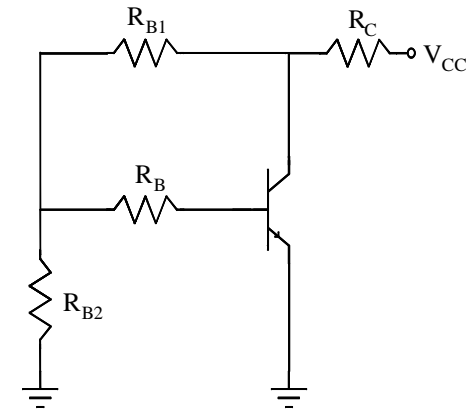
$$R_{B1} := \frac{V_{CE} - V_{RB2}}{I_{B2} + I_B} \quad R_{B2} := \frac{V_{RB2}}{I_{B2}}$$



$$R_C = 126 \text{ ohms}$$

$$R_B = 11,539 \text{ ohms}$$

$$R_{B1} = 889 \text{ ohms}$$

$$R_{B2} = 3000 \text{ ohms}$$


Voltage Feedback and Constant Base Current Source Bias Network #3

$$V_{CC} = 2.7V, V_{CE} = 2V, I_C = 5 \text{ mA}, h_{FE} = 80 \text{ typ, } 50 \text{ min, } 150 \text{ max}$$

$$V_{BE} = 0.78 \text{ V}, I_{CBO} = 1 \times 10^{-7} \text{ A @ } +25 \text{ deg C}$$

$$I_C := \left[\frac{-V_{BE} \cdot (R_{B1} + R_{B2} + R_C) - R_{B2} \cdot [R_C \cdot I_{CBO} \cdot (1 + h_{FE}) - V_{CC}]}{(R_B + h_{ie}) \cdot (R_{B1} + R_{B2} + R_C) + R_{B2} \cdot (h_{FE} \cdot R_C + R_C + R_{B1})} \right] \cdot h_{FE} + I_{CBO} \cdot (1 + h_{FE})$$

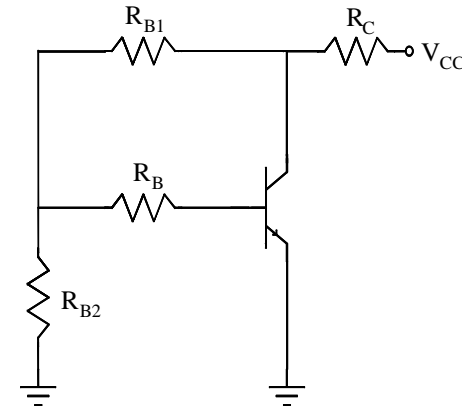Based on h_{FE} alone
 $I_C \text{ max} = 6.98 \text{ mA}$
 $I_C \text{ min} = 3.66 \text{ mA}$



Voltage Feedback Bias Network #4

$$V_{CC} = 2.7V, V_{CE} = 2V, I_C = 5 \text{ mA}, h_{FE} = 80 \text{ typ}, 50 \text{ min}, 150 \text{ max}$$


$$V_{BE} = 0.78 \text{ V}, I_{CBO} = 1 \times 10^{-7} \text{ A @ } +25 \text{ deg C}$$

Choose I_{B2} , suggest a voltage divider current of .5mA, to calculate R_{B2} .

$$R_{B2} := \frac{V_{BE}}{I_{B2}}$$

$$R_{B1} := \frac{V_{CE} - (I_{B2} \cdot R_{B2})}{I_B + I_{B2}}$$
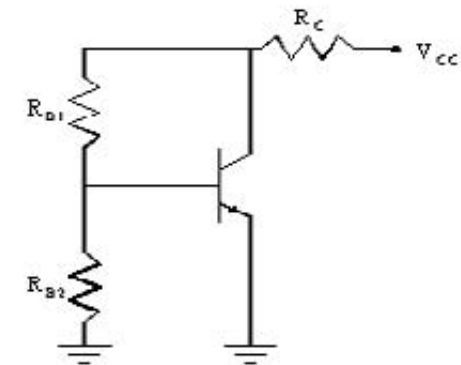
$$R_C := \frac{V_{CC} - V_{CE}}{I_C + I_B + I_{B2}}$$



$$R_C = 126 \text{ ohms}$$

$$R_{B1} = 2169 \text{ ohms}$$

$$R_{B2} = 1560 \text{ ohms}$$

Voltage Feedback Bias Network #4

$$V_{CC} = 2.7V, V_{CE} = 2V, I_C = 5 \text{ mA}, h_{FE} = 80 \text{ typ, } 50 \text{ min, } 150 \text{ max}$$


$$V_{BE} = 0.78 \text{ V}, I_{CBO} = 1 \times 10^{-7} \text{ A @ } +25 \text{ deg C}$$

$$I_C := \frac{\left[\frac{-R_C}{h_{FE}} I_{CBO} - R_C I_{CBO} + \frac{R_C}{R_{B2}} V_{BE} - \frac{R_C}{(R_{B2} \cdot h_{FE})} h_{ie} I_{CBO} - \frac{R_C}{R_{B2}} h_{ie} I_{CBO} - \frac{R_{B1}}{h_{FE}} I_{CBO} - R_{B1} I_{CBO} + \frac{R_{B1}}{R_{B2}} V_{BE} - \frac{R_{B1}}{(R_{B2} \cdot h_{FE})} h_{ie} I_{CBO} - \frac{R_{B1}}{R_{B2}} h_{ie} I_{CBO} + V_{BE} - \frac{1}{h_{FE}} h_{ie} I_{CBO} - h_{ie} I_{CBO} - V_{CC} \right]}{\left[R_C + \frac{R_C}{h_{FE}} + \frac{R_C}{(R_{B2} \cdot h_{FE})} h_{ie} + \frac{R_{B1}}{h_{FE}} + \frac{R_{B1}}{(R_{B2} \cdot h_{FE})} h_{ie} + \frac{1}{h_{FE}} h_{ie} \right]}$$

Based on h_{FE} alone

$$I_C \text{ max} = 5.44 \text{ mA}$$

$$I_C \text{ min} = 4.53 \text{ mA}$$

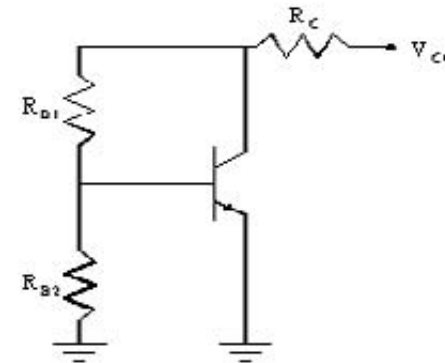

Emitter Feedback Bias Network #5


$$V_{CC} = 2.7V, V_{CE} = 2V, I_C = 5 \text{ mA}, h_{FE} = 80 \text{ typ, } 50 \text{ min, } 150 \text{ max}$$

$$V_{BE} = 0.78 \text{ V}, I_{CBO} = 1 \times 10^{-7} \text{ A @ } +25 \text{ deg C}$$

$$R_E := \frac{V_{CC} - V_{CE}}{\left[\frac{I_C - I_{CBO} \cdot (1 + h_{FE})}{h_{FE}} \right] + I_C} \quad R_1 := \frac{V_{CC} - I_{B2} \cdot R_2}{I_{B2} + I_B}$$

Pick I_{B2} of 10% of I_C which is equal to .0005
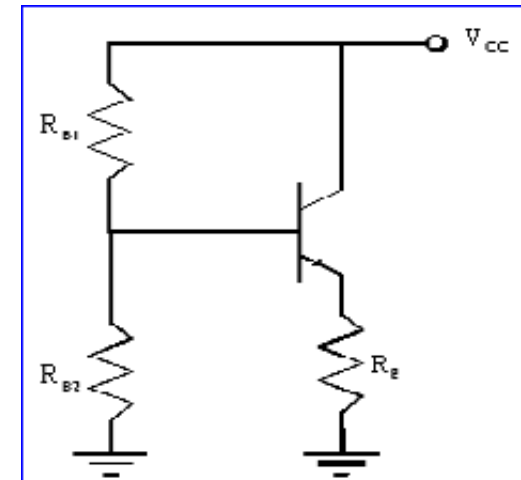
$$R_2 := \frac{V_{RB2}}{I_{B2}} \quad V_{RB2} := V_{BE} + (I_B + I_C) \cdot R_E$$



$$R_E = 138 \text{ ohms}$$

$$R_{B1} = 2169 \text{ ohms}$$

$$R_{B2} = 2960 \text{ ohms}$$


Emitter Feedback Bias Network #5

$$V_{CC} = 2.7V, V_{CE} = 2V, I_C = 5 \text{ mA}, h_{FE} = 80 \text{ typ}, 50 \text{ min}, 150 \text{ max}$$


$$V_{BE} = 0.78 \text{ V}, I_{CBO} = 1 \times 10^{-7} \text{ A @ } +25 \text{ deg C}$$

$$I_C := \frac{\left[V_{BE} - \frac{1}{h_{FE}} h_{ie} I_{CBO} - h_{ie} I_{CBO} - \frac{R_E}{h_{FE}} I_{CBO} - R_E I_{CBO} + \frac{R_1}{R_2} V_{BE} - \frac{R_1}{(R_2 h_{FE})} h_{ie} I_{CBO} - \frac{R_1}{R_2} h_{ie} I_{CBO} - \frac{R_1 R_E}{R_2 h_{FE}} I_{CBO} - \frac{R_1}{R_2} R_E I_{CBO} - \frac{R_1}{h_{FE}} I_{CBO} - R_1 I_{CBO} - V_{CC} \right]}{\left[\frac{1}{h_{FE}} h_{ie} + \frac{R_E}{h_{FE}} + R_E + \frac{R_1}{(R_2 h_{FE})} h_{ie} + \frac{R_1 R_E}{R_2 h_{FE}} + \frac{R_1 R_E}{R_2} + \frac{R_1}{h_{FE}} \right]}$$

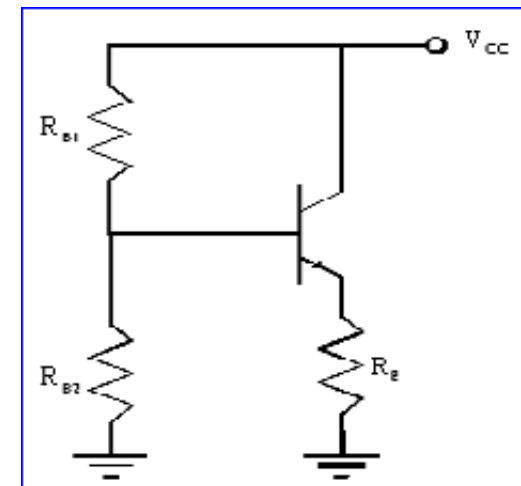Based on h_{FE} alone
 $I_C \text{ max} = 5.27 \text{ mA}$
 $I_C \text{ min} = 4.70 \text{ mA}$



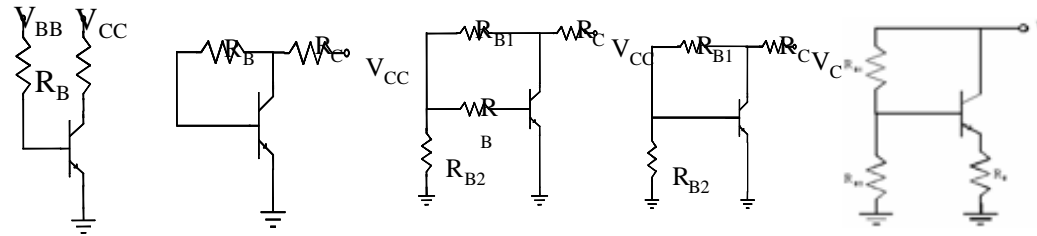Summary of I_C Variation vs h_{FE} For All Bias Circuits



Bias Circuit	Non-stabilized Bias Network	Voltage Feedback Bias Network Feedback	Voltage Feedback w/Current Source Bias Network	Voltage Feedback w/Voltage Source Bias Network	Emitter Feedback Bias Network
I_C (mA) @ minimum h_{FE}	3.14	3.63	3.66	4.53	4.70
I_C (mA) @ typical h_{FE}	5.0	5.0	5.0	5.0	5.0
I_C (mA) @ maximum h_{FE}	9.27	7.09	6.98	5.44	5.27
Percentage change in I_C from nominal I_C	+85% -37%	+42% -27%	+40% -27%	+9% -9%	+5.4% -6%

Bias circuit #5 offers best control on h_{FE} variation but requires emitter resistor
 Bias circuit #4 offer best control on h_{FE} variation without the use of an emitter resistor
 Bias circuits #2 and #3 are very similar in performance.

Use of Stability Factors

$$I_{CBO} = \frac{\partial I_C}{\partial I_{CBO}} \quad h_{FE}, V'_{BE} = \text{constant}$$

$$V'_{BE} = \frac{\partial I_C}{\partial V'_{BE}} \quad I_{CBO}, h_{FE} = \text{constant}$$

$$h_{FE} = \frac{\partial I_C}{\partial h_{FE}} \quad I_{CBO}, V'_{BE} = \text{constant}$$

$$\Delta I_C = S_{I_{CBO}} \bullet \Delta I_{CBO} + S_{V'_{BE}} \bullet \Delta V'_{BE} + S_{h_{FE}} \bullet \Delta h_{FE}$$

First Calculate the stability factors for V'_{BE} , I_{CBO} , and h_{FE} . Then, to find the change in collector current at any temperature, multiply the change from 25°C of each temperature dependent variable with its corresponding stability factor and sum.

Calculating ΔI_{CBO} , $\Delta V'_{BE}$, and Δh_{FE}


Example: Calculate deltas from +25° C to +65° C

I_{CBO} is typically 100nA @ +25° C and typically doubles for every 10° C temperature rise. Therefore $I_{CBO} = 1600\text{nA}$ @ +65° C. $\Delta I_{CBO} = 1600 - 100 = 1500 \text{ nA}$

V'_{BE} measured at .755V @ 25° C and has a typical negative temperature coefficient of -2mV/°C. Therefore V'_{BE} will be .675V @ +65° C making $\Delta V'_{BE}$ equal to .675 - .755 = -.08V

h_{FE} is 80 @ +25° C and typically increases 0.5%/° C. Therefore h_{FE} will increase from 80 to 96 @ +65° C making Δh_{FE} equal to 96 - 80 = 16

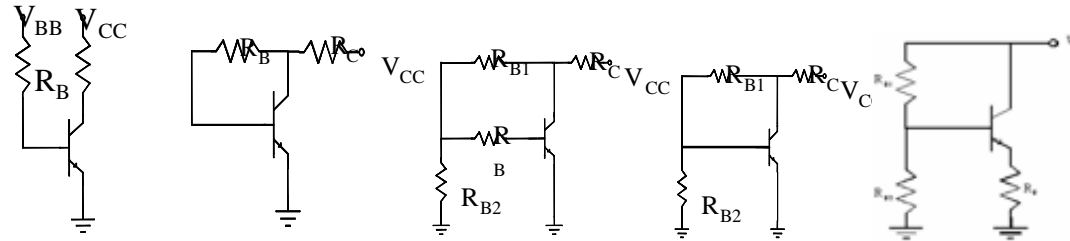Bias Stability Analysis @ +65°C using HBFP-04XX



Bias Circuit	#1 Non-Stabilized	#2 Voltage Feedback	#3 Voltage Feedback w/Current Source	#4 Voltage Feedback	#5 Emitter Feedback
I_{CBO} Stability Factor	81	52.238	50.865	19.929	11.286
V'_{BE} Stability Factor	-2.56653×10^{-3}	-2.568011×10^{-3}	-3.956×10^{-3}	-0.015	-6.224378×10^{-3}
h_{FE} Stability Factor	6.249877×10^{-5}	4.031×10^{-5}	3.924702×10^{-5}	1.537669×10^{-5}	8.707988×10^{-6}
ΔI_C due to I_{CBO} (mA)	0.120	0.078	0.076	0.030	0.017
ΔI_C due to V'_{BE} (mA)	0.210	0.205	0.316	1.200	0.497
ΔI_C due to h_{FE} (mA)	0.999	0.645	0.628	0.246	0.140
Total ΔI_C (mA)	1.329	0.928	1.020	1.476	0.654
Percentage change in I_C from nominal I_C	26.6%	18.6%	20.4%	29.5%	13.1%

Bias Circuits

- #1 non-stabilized
- #2 volt feedback
- #3 volt feedback w/current source
- #4 voltage feedback
- #5 emitter feedback

Bias circuits #2 and #3 similar in performance at temp and superior to #1 and #4

Bias circuit #5 is superior but requires emitter resistor and emitter bypass

Calculating ΔI_{CBO} , $\Delta V'_{BE}$, and Δh_{FE}


Example: Calculate deltas from +25° C to +85° C

I_{CBO} is typically 200nA @+25° C and typically doubles for every 10°C temperature rise. Therefore $I_{CBO} = 12800\text{nA}$ @ +85° C. $\Delta I_{CBO} = 12800 - 200 = 12600 \text{ nA} = 12.6 \text{ uA}$

V'_{BE} measured at .755V @ 25° C and has a typical negative temperature coefficient of -2mV/°C. Therefore V'_{BE} will be .635V @ +85° C making $\Delta V'_{BE}$ equal to .635 - .755 = -.120V

h_{FE} is 150 @ +25° C and typically increases 0.5%/ ° C. Therefore h_{FE} will increase from 150 to 195 @ +85° C making Δh_{FE} equal to 195 - 150 = 45

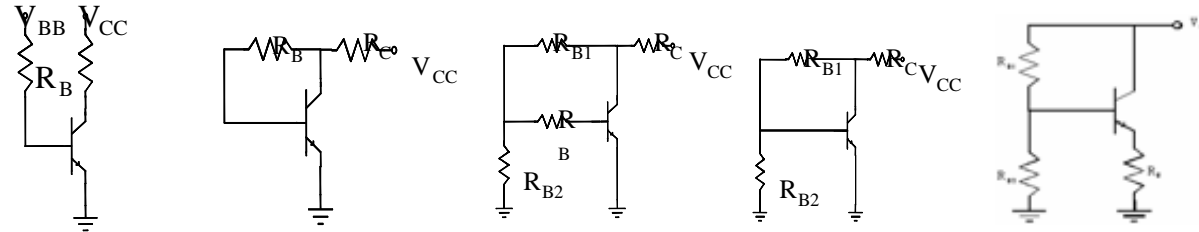Bias Stability Analysis @ +85°C using HBFP-04XX



Bias Circuit	#1	#2	#3	#4	#5
I_{CBO} Stability Factor	81	52.238	50.865	19.929	11.286
V'_{BE} Stability Factor	-2.56653×10^{-3}	-2.568011×10^{-3}	-3.956×10^{-3}	-0.015	-6.224378×10^{-3}
h_{FE} Stability Factor	6.249877×10^{-5}	4.031×10^{-5}	3.924702×10^{-5}	1.537669×10^{-5}	8.707988×10^{-6}
ΔI_C due to I_{CBO} (mA)	1.021	0.658	0.641	0.251	0.142
ΔI_C due to V'_{BE} (mA)	0.308	0.308	0.475	1.800	0.747
ΔI_C due to h_{FE} (mA)	2.812	1.814	1.766	0.692	0.392
Total ΔI_C (mA)	4.141	2.780	2.882	2.743	1.281

Bias Circuits

#1 non-stabilized

#2 volt feedback

#3 volt feedback w/current source

#4 voltage feedback

#5 emitter feedback

Bias circuits #2, #3 and #4 similar in performance at temp and superior to #1

Bias circuit #5 is superior but requires emitter resistor and emitter bypass
 I_{CBO} and h_{FE} variations are major contributors at elevated temperature

Avago Technologies AppCAD

AppCAD - [Bipolar Transistor Bias]

File Calculate Options Help

Main Menu [F0]

V Feedback, Constant I Source Bias Network

$R_{B1} = 910 \text{ Ohm}$ $R_C = 130 \text{ Ohm}$ $V_{CC} = 27 \text{ V}$
 $R_B = 12 \text{ kOhm}$ $I_C = 5 \text{ mA}$ $I_{CC} = 5.38 \text{ mA (typ, see Help)}$
 $R_{B2} = 3 \text{ kOhm}$ $V_{CE} = 2 \text{ V}$

Transistor Parameters

$h_{FE} = 50 \text{ min } 80 \text{ typ } 150 \text{ max}$
 $I_{CBO} = 0.1 \text{ uA}$ $\theta_{JC} = 300 \text{ }^\circ\text{C/W}$
 $T_C = -25 \text{ min } 25 \text{ typ } 65 \text{ max } ^\circ\text{C}$

Design Rules

$V_{RB2} = 0.75 \times V_{CE} = 1.50 \text{ V}$
 $I_{RB2} = 0.1 \times I_C = 0.500 \text{ mA}$
 $V_{BE} = 0.78 \text{ V}$ $\partial I_{CBO}/\partial T \text{ factor} = 2 / 10 \text{ }^\circ\text{C}$
 $\partial V_{BE}/\partial T = -2 \text{ mV}/^\circ\text{C}$ $\partial h_{FE}/\partial T = 0.5 \text{ } \%/^\circ\text{C}$

1. Enter values for V_{CC} , V_{CE} , and I_C .
 2. Enter Transistor Parameters.
 3. Calculate bias resistors and analyze circuit. Calculate [F4]

Collector Current, I_C (mA):

$h_{FE} =$	50	80	150
-25 $^\circ\text{C}$	2.70	3.72	5.01
25 $^\circ\text{C}$	3.56	4.86	6.81
65 $^\circ\text{C}$	4.34	5.87	8.35


$I_C \text{ max/min ratio} = 3.1$ $T_{j \text{ max}} = 70.0 \text{ }^\circ\text{C}$

Stability Analysis:

	Stability Factor	Delta I_C (mA): typ h_{FE} , T_C
I_{CBO}	5.11E+01	0.005
V_{BE}	3.83E-03	0.329
h_{FE}	3.78E-05	0.650
Delta I_C, Total =		1.075


Normal Click for Web: APPLICATION NOTES - MODELS - DESIGN TIPS - DATA SHEETS - S-PARAMETERS

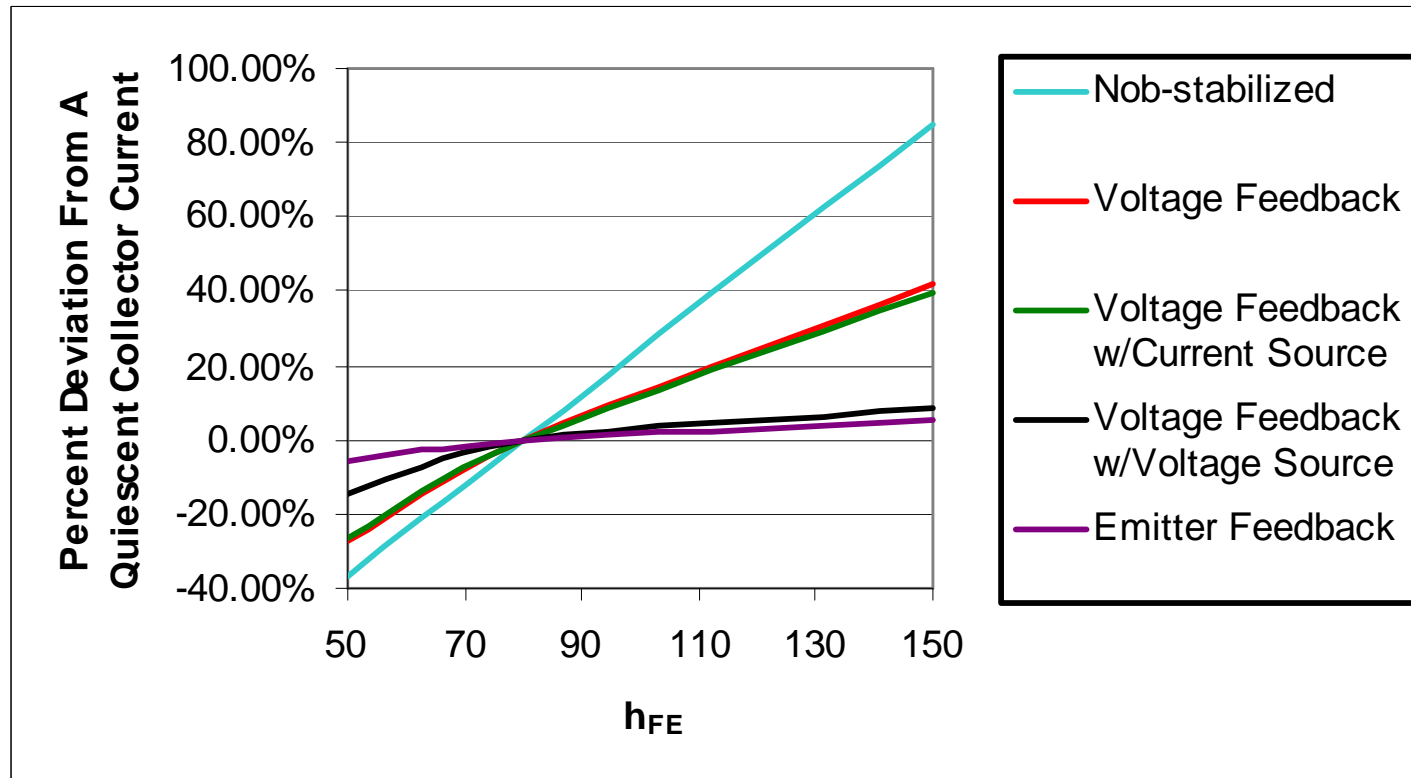Percent Change in Quiescent Collector Current versus h_{FE} for the HBFP-0405




$V_{CC}=2.7V$
 $V_{CE}=2V$
 $I_C=5\text{ mA}$
 $T_J=+25^\circ C$

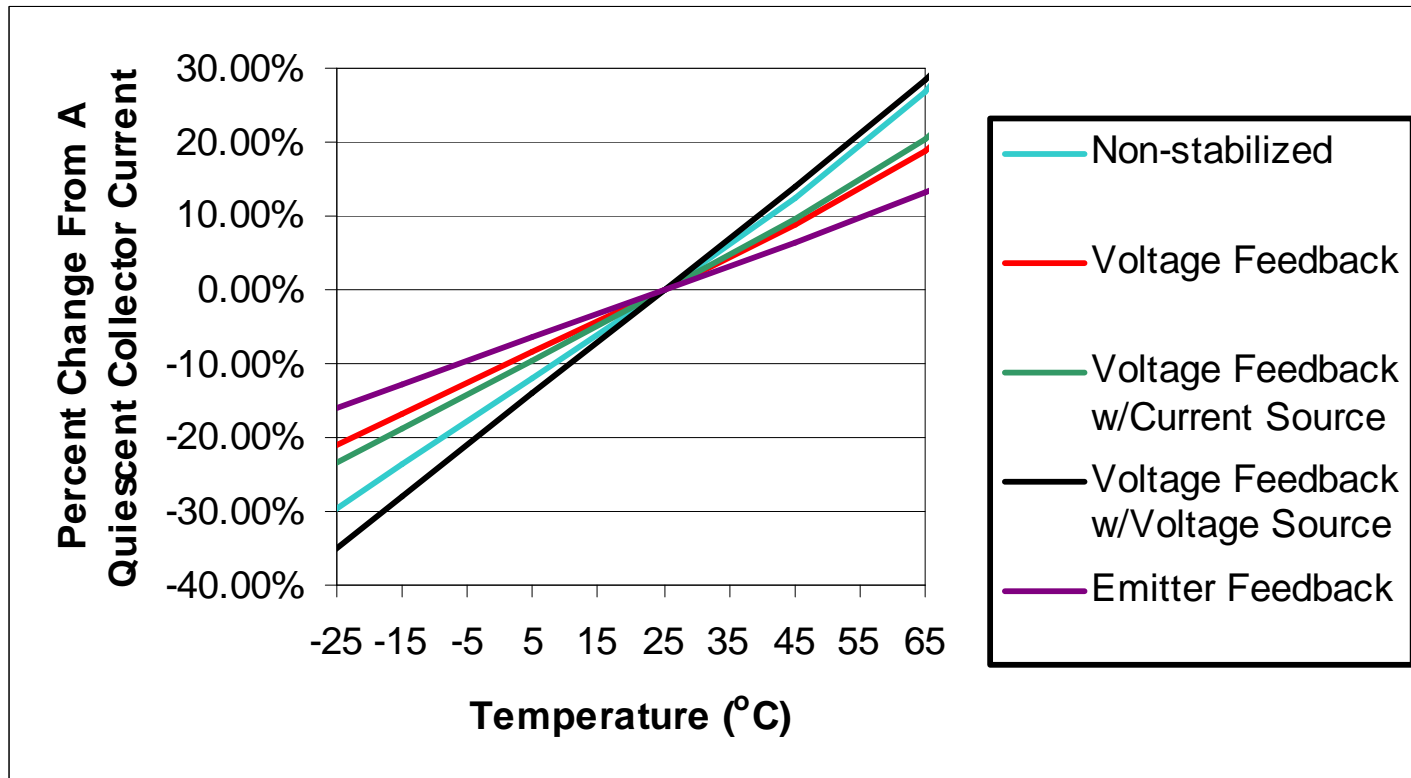Percent Change in Quiescent Collector Current versus Temperature for the HBFP-0405




$V_{CC}=2.7V$
 $V_{CE}=2V$
 $I_C=5\text{ mA}$

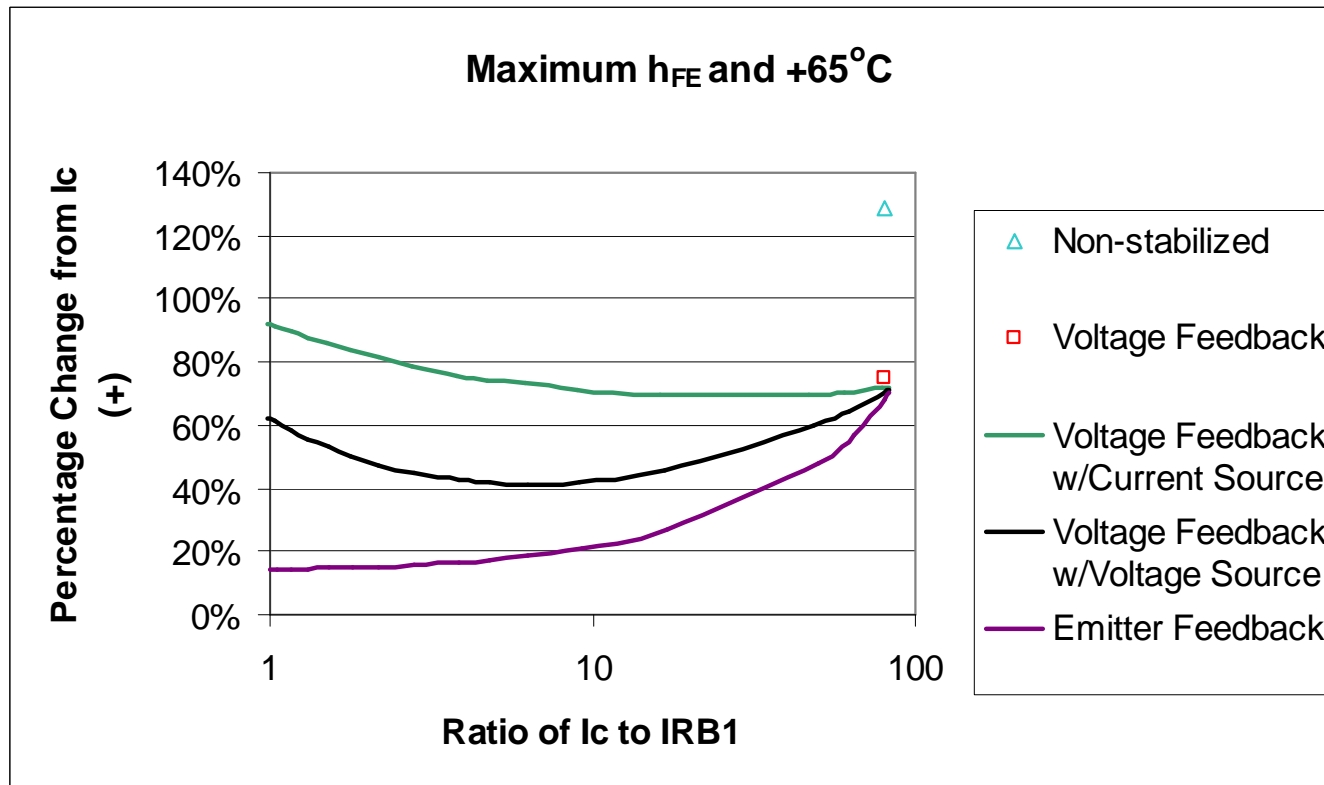Percent Change in Quiescent Collector Current versus Ratio of I_C to I_{RB1} for Max. h_{FE} and $+65^\circ\text{C}$ for the HBFP-0405



$V_{CC}=2.7\text{V}$
 $V_{CE}=2\text{V}$
 $I_C=5\text{ mA}$

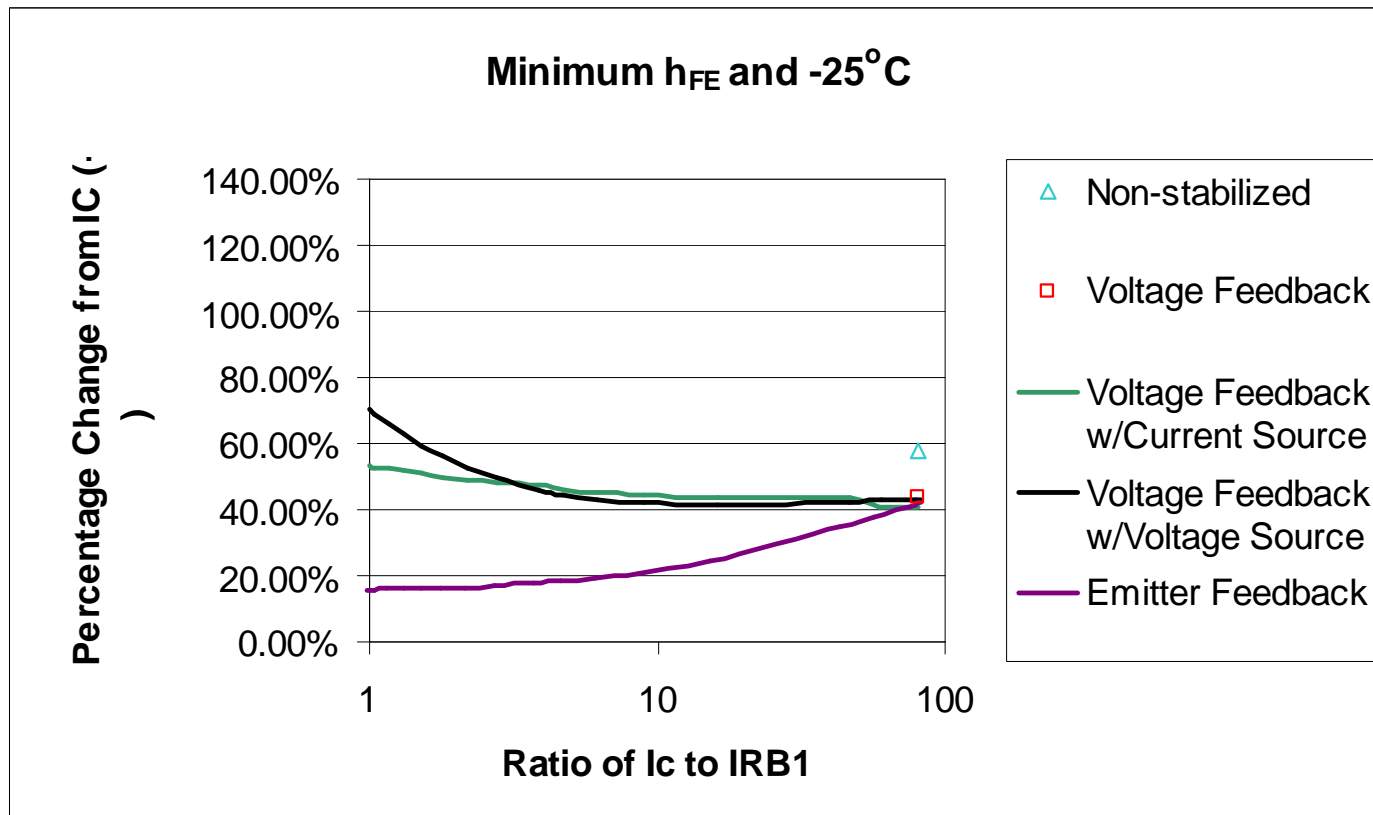Percent Change in Quiescent Collector Current versus Ratio of I_C to I_{RB1} for Min. h_{FE} and -25°C for the HBFP-0405



$V_{CC}=2.7\text{V}$
 $V_{CE}=2\text{V}$
 $I_C=5\text{ mA}$

Conclusions

Emitter feedback in circuit #5 offers the best control on h_{FE} variations from device to device and over temperature. However, an emitter bypass capacitor is needed to provide a good RF short. The inductance associated with the bypass capacitor quite often causes circuit instabilities with high f_t transistors.

Best alternative is circuit #4 followed by circuit #2. Circuit #4 offers best control on h_{FE} variation from device to device and circuit #2 provides best performance up to +65 degrees C. At +85 degrees C, circuit #4 performs as well as circuit #2.

Additional Thoughts

Higher V_{cc} can improve the performance of all bias circuits

Additional base bias resistor current can often improve bias regulation

An increase in the value of the emitter resistor for circuit #5 will offer increased bias circuit regulation.

Active bias network offers best regulation but requires additional components.

Related Application Notes and Articles

AN 1084 Two-Stage 800 – 1000 MHz Amplifier using the AT-41511 Silicon Bipolar Transistor – 5964-3853E (11/99)

AN 1085 900 and 2400 MHz Amplifiers using the AT-3 Series Low Noise Silicon Bipolar Transistors – 5964-3854E (11/99)

AN 1131 Low Noise Amplifiers for 320 MHz and 850 MHz Using the AT-32063 Dual Transistor – 5966-0781E (11/99)

AN 1293 A Comparison of Various Bipolar Transistor Biasing Circuits – 5988-6173EN June 27, 2006

AN S014 750 – 1250 MHz Voltage Controlled Oscillators – 5988-0273EN (9/00)

A Comparison of Various Bipolar Transistor Biasing Circuits by Al Ward (W5LUA) and Bryan Ward (N5QGH), Agilent Technologies, Applied Microwave & Wireless, April 2001, pages 30-44