

Stability & LNAs

Microwave Update

Enfield, CT.

Al Ward

W5LUA

October 14, 2011

Requirements for an LNA


- **Absolute lowest noise figure possible**
- **Good gain to overcome second stage noise figure**
- **Gain only where we need it**
- **Good large signal handling capabilities**
- **Must be stable at all frequencies when installed in the system between the antenna and/or feed and converter – probably the most difficult task....**
- **Good indicators of instability are excessive gain, high out-of-band gain and positive return loss**

The Process

- **Understand what the S Parameters are telling you about a device**
- **Make good engineering decisions based on noise figure, gain and stability – both in-band and out-of-band**
- **Let's start by taking a look at S Parameters.....**

Start with S-parameters?!??!

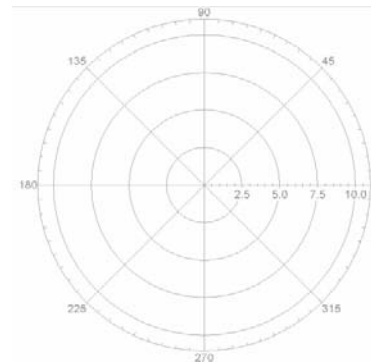
- A three-terminal two-port, such as the FET shown, has four S-parameters.
- S_{nn} = voltage reflection coefficient, both amplitude and phase relative to 50Ω source impedance
- S_{21} and S_{12} are commonly displayed on a polar chart.
- $S_{11} = \Gamma_{input}$ displayed on Smith chart
- $S_{22} = \Gamma_{output}$ displayed on Smith chart



Polar chart



Smith chart

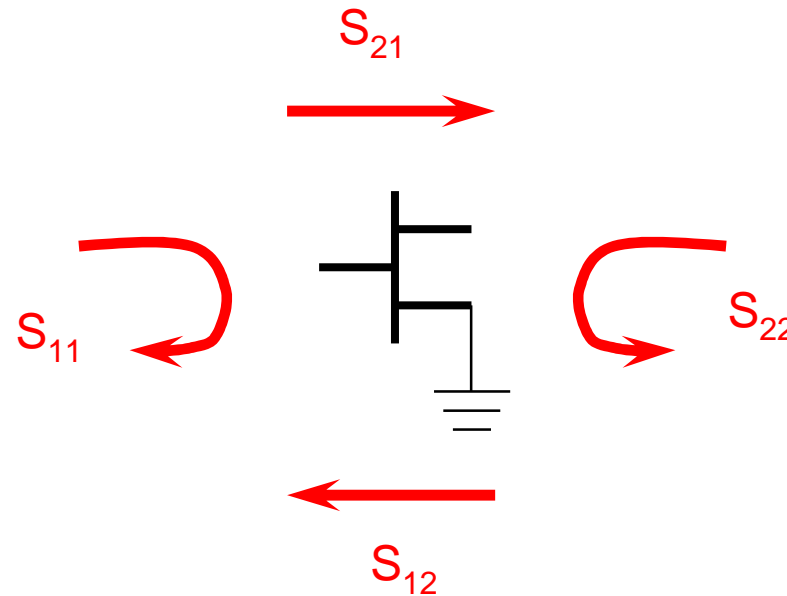

ATF-36077 S and Noise Parameters

```

F360772A - Notepad
File Edit Format View Help
!ATF-36077
!S AND NOISE PARAMETERS at vds=1.5V Id=10mA. LAST UPDATED 06-27-94
!EXTRAPOLATED DOWN TO 50 MHZ
# ghz s ma r 50
0.05 0.999 -1 5.050 179 0.005 89 0.60 -1
0.5 0.998 -9 5.050 171 0.009 83 0.60 -7
1 0.99 -17 5.010 163 0.016 78 0.60 -14
2 0.97 -33 4.904 147 0.030 66 0.59 -28
3 0.94 -49 4.745 132 0.043 54 0.57 -41
4 0.90 -65 4.556 116 0.054 43 0.55 -54
5 0.86 -79 4.357 102 0.063 33 0.53 -66
6 0.82 -93 4.162 88 0.069 24 0.50 -78
7 0.78 -107 3.981 75 0.074 16 0.48 -89
8 0.75 -120 3.820 62 0.078 8 0.46 -99
9 0.72 -133 3.682 49 0.080 1 0.44 -109
10 0.69 -146 3.566 37 0.082 -6 0.42 -119
11 0.66 -159 3.473 25 0.083 -13 0.40 -129
12 0.63 -172 3.401 13 0.085 -19 0.38 -139
13 0.61 175 3.349 1 0.086 -25 0.37 -149
14 0.60 161 3.315 -12 0.087 -32 0.35 -160
15 0.58 147 3.296 -24 0.089 -39 0.33 -171
16 0.57 131 3.289 -37 0.091 -47 0.31 177
17 0.56 114 3.289 -50 0.092 -55 0.29 164
18 0.57 97 3.291 -64 0.094 -65 0.26 148

.05 0.30 0.98 1 0.60
0.5 0.30 0.97 6 0.50
1 0.30 0.95 12 0.40
2 0.30 0.90 25 0.20
4 0.30 0.81 51 0.17
6 0.30 0.73 76 0.13
8 0.37 0.66 102 0.09
10 0.44 0.60 129 0.05
12 0.50 0.54 156 0.03
14 0.56 0.48 -174 0.02
16 0.61 0.43 -139 0.05
18 0.65 0.39 -100 0.09
    
```

ATF-36077 S Parameters

Freq (GHz)	S11 Mag Ang		S21 Mag Ang		S12 Mag Ang		S22 Mag Ang	
0.05	0.999	-1	5.050	179	0.005	89	0.60	-1
0.5	0.998	-9	5.050	171	0.009	83	0.60	-7
1	0.99	-17	5.010	163	0.016	78	0.60	-14
2	0.97	-33	4.904	147	0.030	66	0.59	-28
3	0.94	-49	4.745	132	0.043	54	0.57	-41
4	0.90	-65	4.556	116	0.054	43	0.55	-54
5	0.86	-79	4.357	102	0.063	33	0.53	-66
6	0.82	-93	4.162	88	0.069	24	0.50	-78
7	0.78	-107	3.981	75	0.074	16	0.48	-89
8	0.75	-120	3.820	62	0.078	8	0.46	-99
9	0.72	-133	3.682	49	0.080	1	0.44	-109
10	0.69	-146	3.566	37	0.082	-6	0.42	-119
11	0.66	-159	3.473	25	0.083	-13	0.40	-129
12	0.63	-172	3.401	13	0.085	-19	0.38	-139
13	0.61	175	3.349	1	0.086	-25	0.37	-149
14	0.60	161	3.315	-12	0.087	-32	0.35	-160
15	0.58	147	3.296	-24	0.089	-39	0.33	-171
16	0.57	131	3.289	-37	0.091	-47	0.31	177
17	0.56	114	3.289	-50	0.092	-55	0.29	164
18	0.57	97	3.291	-64	0.094	-65	0.26	148


$$RL = 10 \log |\Gamma|^2 \quad VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} \quad G = 20 \log |\Gamma|$$

ATF-36077 Noise Parameters

Freq (GHz)	Fmin (dB)	Gamma Opt (Γ_o)		Rn
		Mag	Ang	
.05	0.30	0.98	1	0.60
0.5	0.30	0.97	6	0.50
1	0.30	0.95	12	0.40
2	0.30	0.90	25	0.20
4	0.30	0.81	51	0.17
6	0.30	0.73	76	0.13
8	0.37	0.66	102	0.09
10	0.44	0.60	129	0.05
12	0.50	0.54	156	0.03
14	0.56	0.48	-174	0.02
16	0.61	0.43	-139	0.05
18	0.65	0.39	-100	0.09



What about Noise Parameters?!??!

- Γ_o (Gamma Opt) is the reflection coefficient of the source impedance presented to the device that allows the device to produce its' f_{min}
- Matching circuit losses often limit the ability of the amplifier to achieve a noise figure equivalent to device f_{min}
- Γ_o not necessarily equal to $S11^*$ which means noise match is not equivalent to a gain match
- R_n (Noise Resistance) is used to calculate the device's sensitivity in noise figure to changes in source impedance, r_n is normalized to 50Ω .

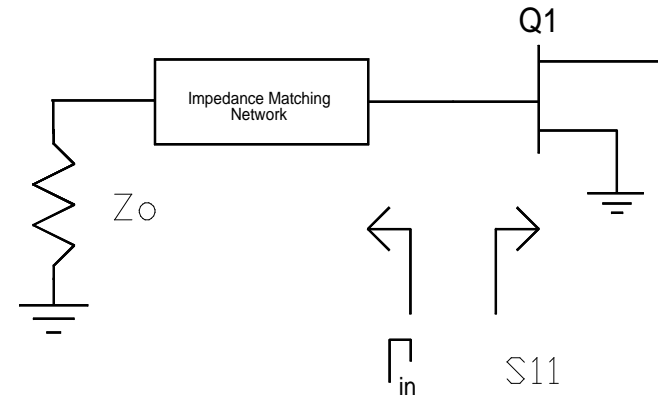


For minimum NF, $\Gamma_{in} = \Gamma_o$
 For maximum gain, $\Gamma_{in} = S11^*$

Input Impedance Match

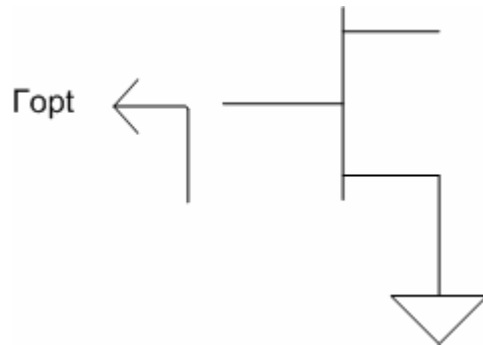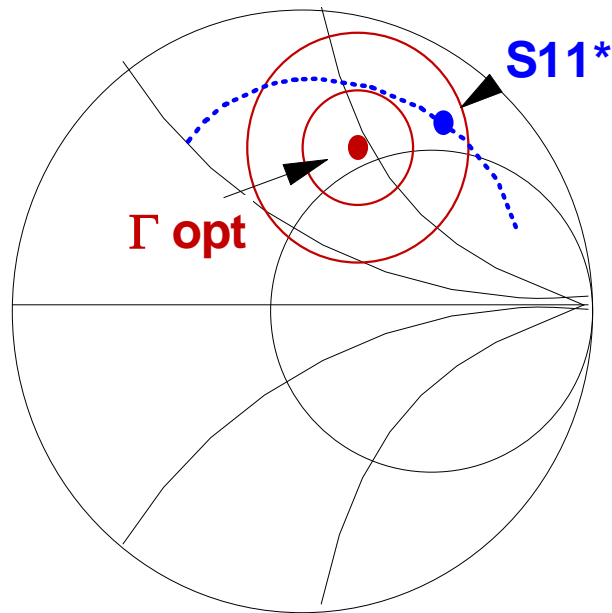


- Match to Γ_{opt} for minimum noise figure
- Noise degrades in circular contours as match moves away from Γ_{opt}
- Degree of noise degradation is dependent on R_n , the noise resistance
- Most amateur applications aim for minimum noise figure and accept input VSWR


Simultaneous Input VSWR and Noise Match

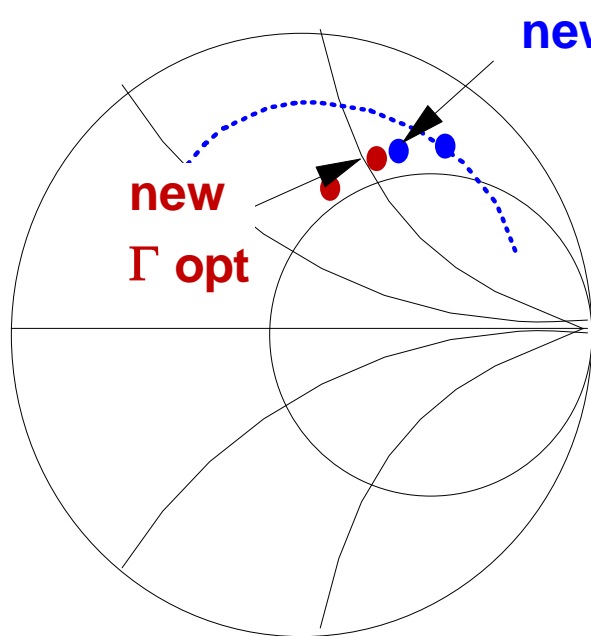

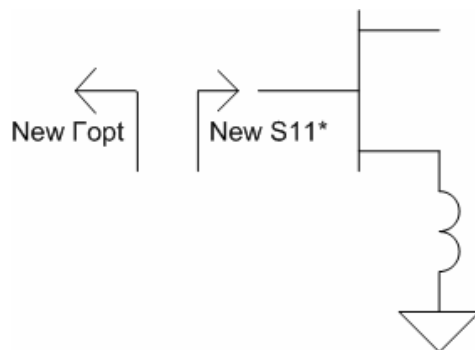- Adding source inductance rotates Γ_{opt} towards S_{11}^*
- Source inductance is series feedback which effects gain and stability
- Its' effect must be analyzed over as a wide a bandwidth as the device has gain



Output Impedance Match

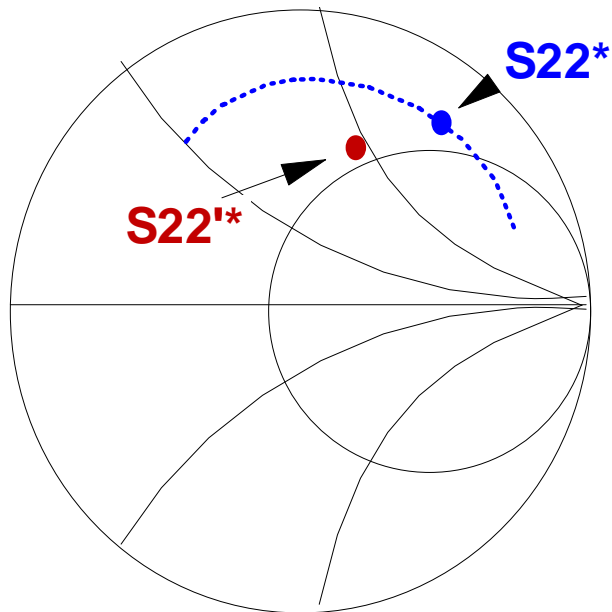

$$\Gamma_L = \left[S_{22} + \frac{S_{12} S_{21} \Gamma_O}{1 - S_{11} \Gamma_O} \right]^*$$

- $S_{22}'^* = \Gamma_L$ is the reflection coefficient of the output matching network with input terminated in Γ_{opt} , not 50Ω
- Match to $S_{22}'^* = \Gamma_L$ for best gain/output VSWR
- LNA may not be unconditionally stable when matched for best output VSWR - Some resistive loading may be required to reduce gain to improve stability
- Best output VSWR does not necessarily guarantee best P1dB and IP3.

ATF-36077 S21, MSG & MAG

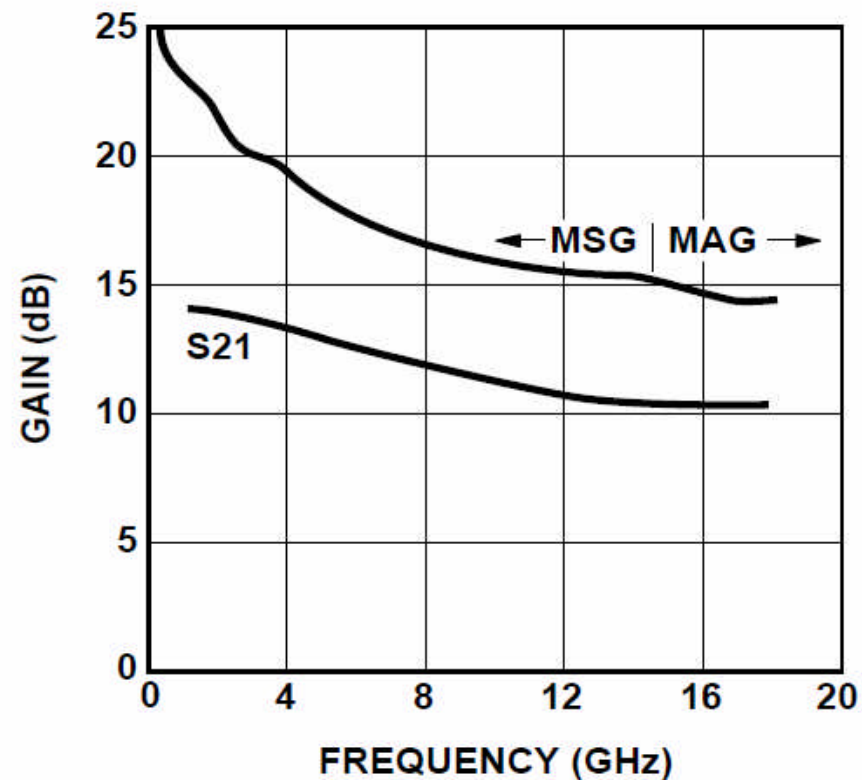


Figure 2. Maximum Available Gain, Maximum Stable Gain and Insertion Power Gain vs. Frequency. $V_{DS} = 1.5$ V, $I_D = 10$ mA.

Evaluating LNA Stability

- Two factors are typically used to evaluate LNA stability. The first is the Rollett Stability factor K . $K > \text{or} = 1$ for unconditional stability

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |D|^2}{2|S_{12}||S_{21}|}$$

$$D = S_{11}S_{22} - S_{12}S_{21}$$

- The second is μ and μ'


This measurement gives the distance from the center of the Smith chart to the nearest output (load) stability circle. This stability factor is given by:

$$\mu = \{1 - |S_{11}|^2\} / \{|S_{22} - \text{conj}(S_{11}) * \Delta| + |S_{12} * S_{21}|\}$$

where Δ is the determinant of the S-parameter matrix. Having $\mu > 1$ is the single necessary and sufficient condition for unconditional stability of the 2-port network.


- Both are calculated using LNA S parameters over a wide frequency range for reasons that will be discussed shortly

ATF-36077 1296 MHz LNA

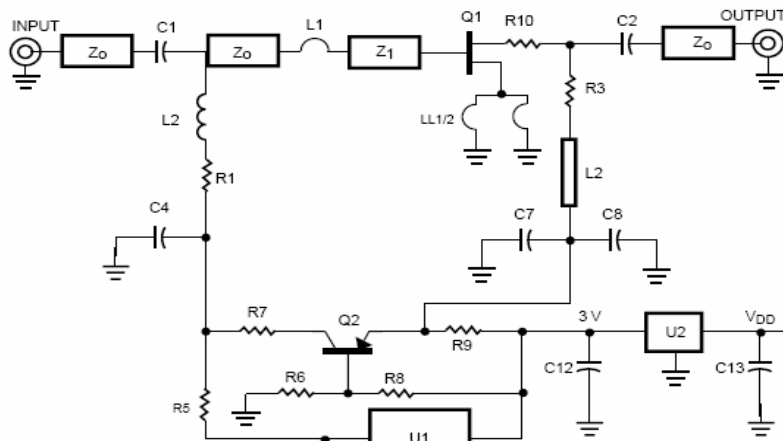



- C1 = 22 pF CHIP CAPACITOR
- C2 = 100 pF CHIP CAPACITOR
- C3 = NOT USED
- C4, C7 = 1000 pF CHIP CAPACITOR
- C5, C6 = NOT USED, GROUND SOURCES DIRECTLY
- C9 = NOT USED
- C8, C12, C13 = 0.1 μF CHIP CAPACITOR
- C10, C11 = 10 μF CHIP CAPACITOR
- L1 = 6T 0.007" DIA. WIRE, 0.050" ID, 0.14" LENGTH
- L2 = 0.18 TO 0.33 μH RFC
- LL1, LL2 = PLATED THROUGH HOLES TO BACKSIDE GROUNDPLANE DIRECTLY UNDER EACH LEAD
- Q1 = AGILENT TECHNOLOGIES ATF-36077 PHEMT
- R1 = 100 OHM CHIP RESISTOR
- R2 = NOT USED
- R3 = 50 OHM CHIP RESISTOR
- R4 = NOT USED
- R5, R7 = 10 k OHM CHIP RESISTOR
- R6 = 1.3 k OHM CHIP RESISTOR
- R8 = 2.7 k OHM CHIP RESISTOR (SETS DRAIN VOLTAGE)
- R9 = 270 OHM CHIP RESISTOR (SETS DRAIN CURRENT)
- R10 = 16 OHM CHIP RESISTOR (UP TO 27 OHMS OK)
- U1 = LINEAR TECHNOLOGY LTC1044CS8 VOLTAGE CONVERTER
- U2 = 5 VOLT REGULATOR TOKO TK11650U

Agilent ADS Simulation

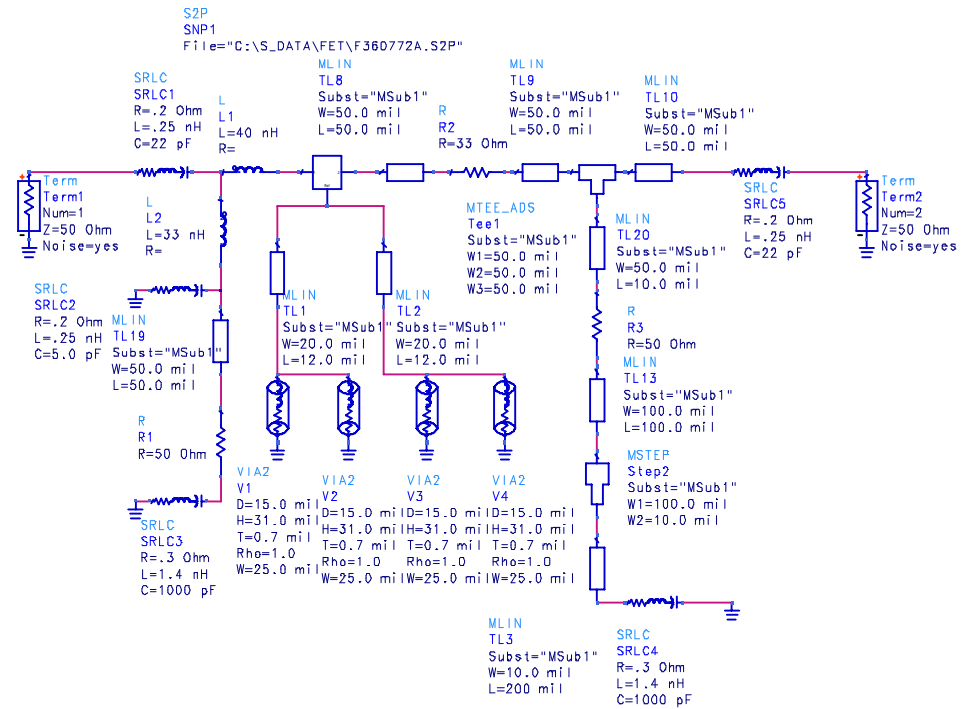


Adding a 5 pF cap to ground at the junction of L2 and R1 will lower noise figure

Source Grounding

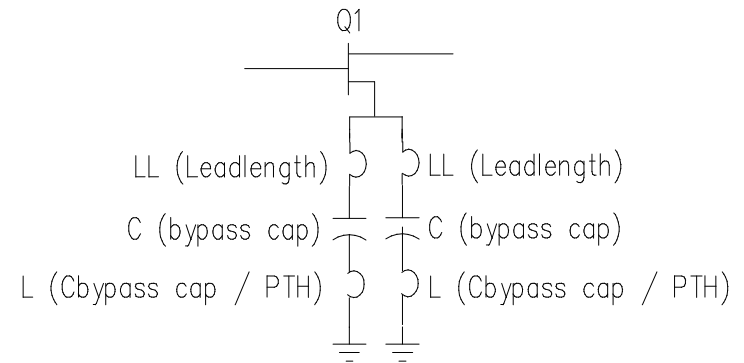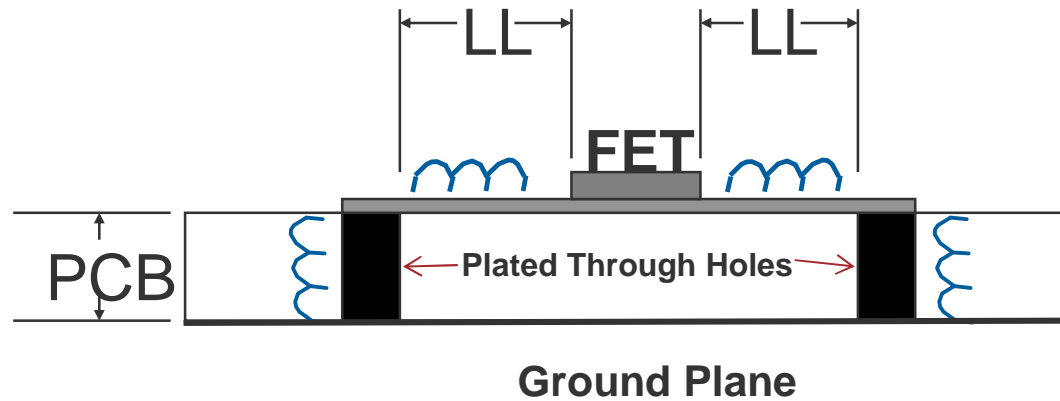

Source inductance can be the biggest problem with most LNAs. Usually there are two source leads so the inductance can effectively be cut in half. Source inductance is made up from several factors including the length of the source lead, the length of the VIA to the bottom side of the circuit board ground plane and any additional circuit trace that connects the source lead to the VIA. If self biasing is used then the equivalent series inductance of the bypass capacitor must be included in the analysis. In a good LNA design, this inductance amounts to a few tenths of a nH, but the effects are significant.....


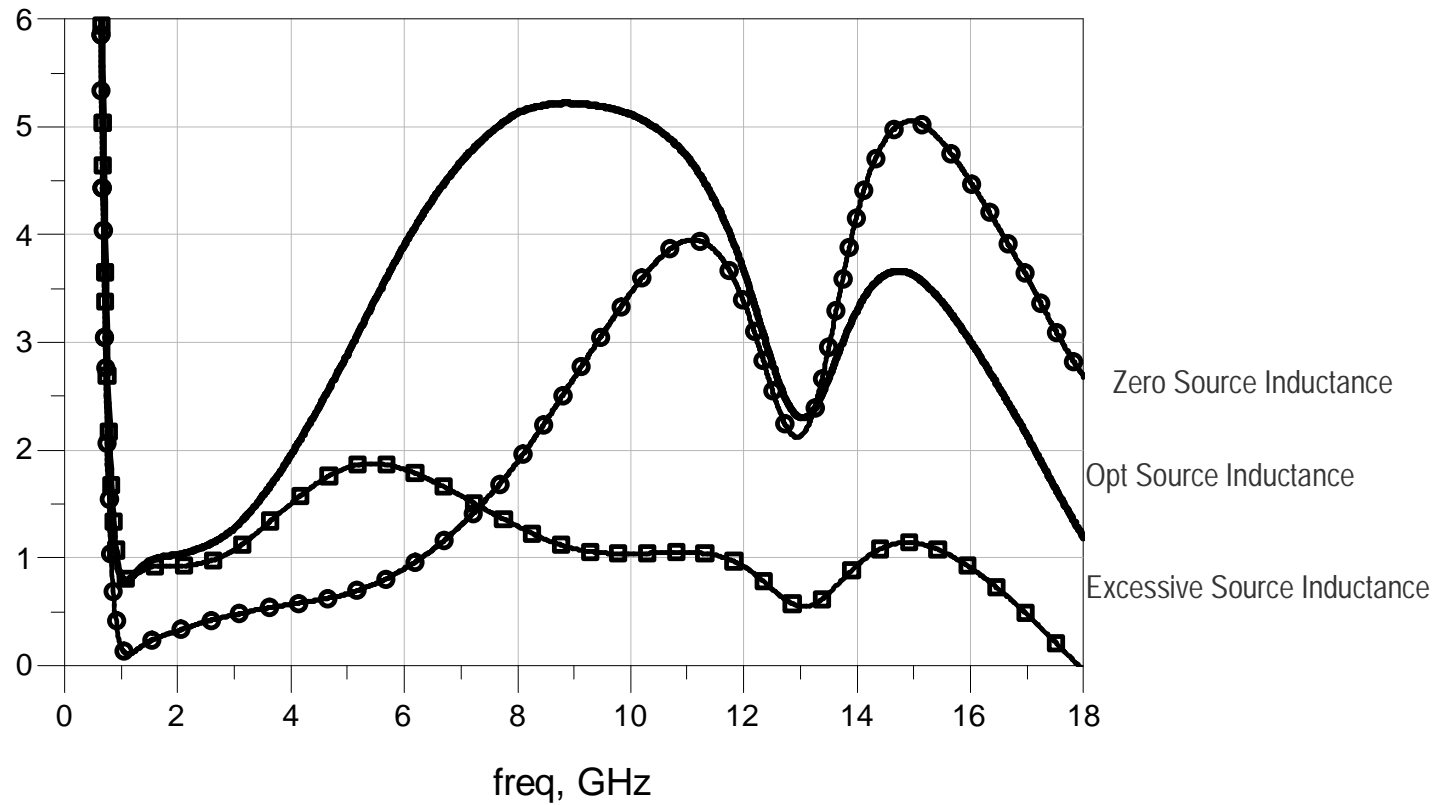
Evaluating LNA Stability K versus Frequency




$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |D|^2}{2|S_{12}||S_{21}|}$$

$$D = S_{11}S_{22} - S_{12}S_{21}$$

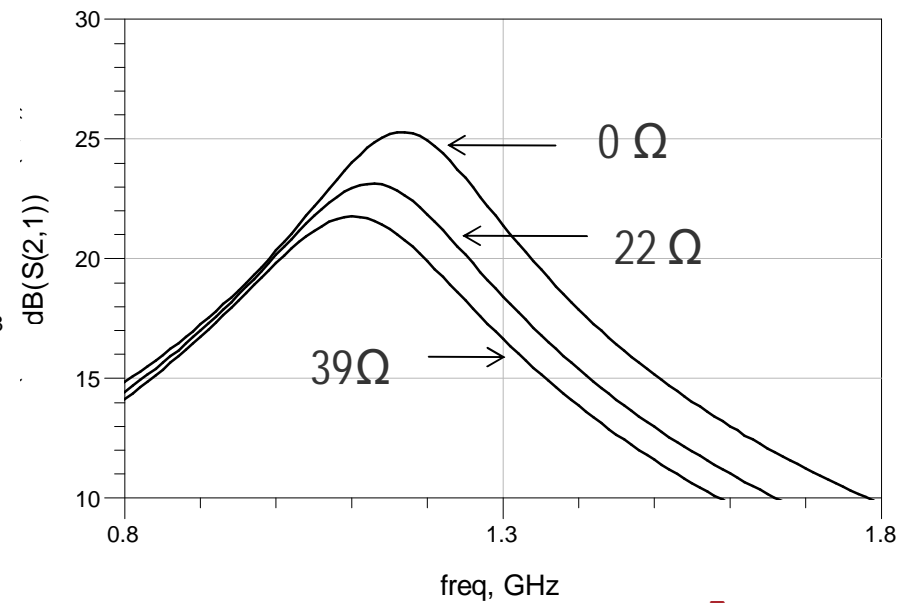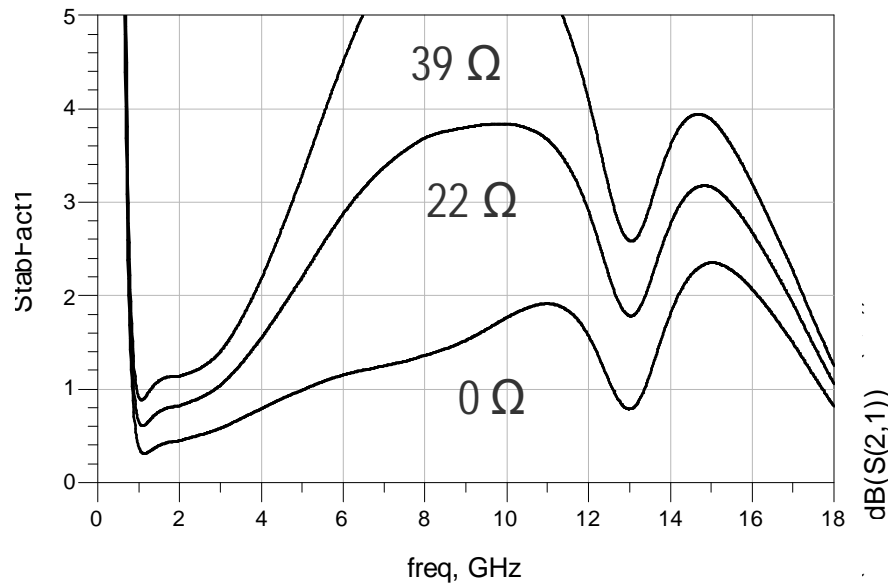
Improving Stability with Resistance in the Drain Once the Optimum Source Inductance has been determined



Noise Figure vs Drain Resistance

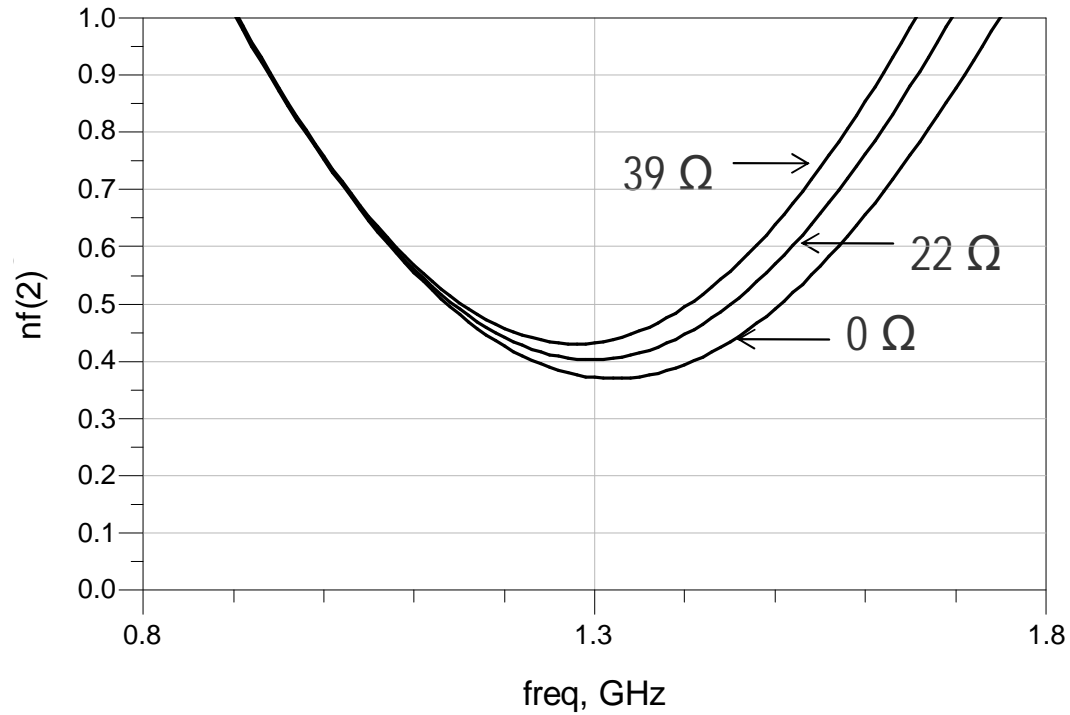


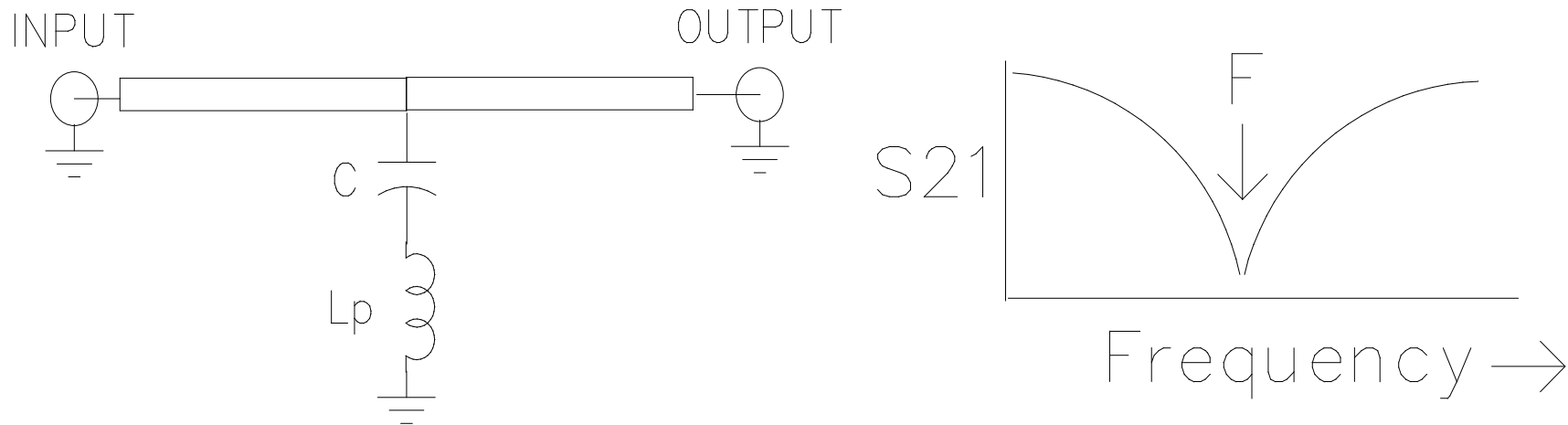Chip Capacitor Parasitics - A First Approximation



- A capacitor shunted across a microstripline exhibits a first order series resonance at a frequency where the capacitance C and its' associated parasitic lead inductance Lp resonate. The effect is shown as a reduction in S21 at frequency F
- OR
- Lp can then be easily calculated by $\omega = 2 \pi F = 1 / \text{SQRT} (L C)$

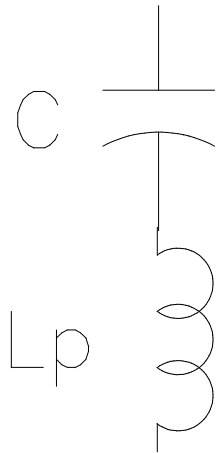Chip Capacitor Parasitics - A First Approximation




Capacitor (pF)	Associated Inductance Lp (nH)
1	0.71
8.2	0.78
27	0.79
1000	1.2

Sample data


- Capacitors are ATC 0.050” square ceramic
- Parasitic inductance should be included in circuit designs for best correlation between simulation and actual bench performance

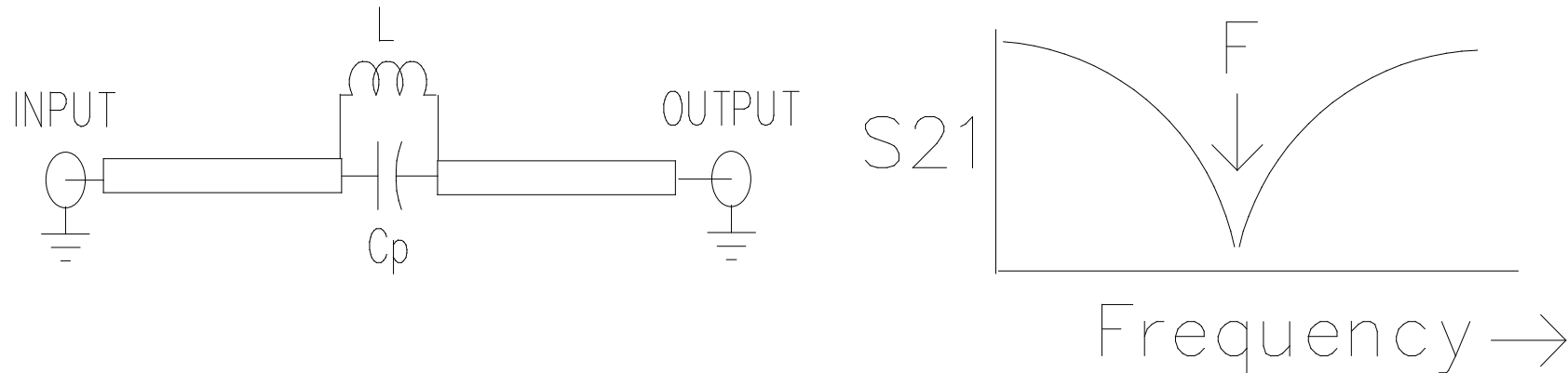Chip Inductor Parasitics - A First Approximation



- An inductor inserted in series with a microstripline exhibits a first order parallel resonance at a frequency where the inductor L and its' associated shunt parasitic capacitance C_p resonate. The effect is shown as a reduction in S_{21} at frequency F OR
- L_p can then be easily calculated by $\omega = 2 \pi F = 1 / \text{SQRT} (L C)$

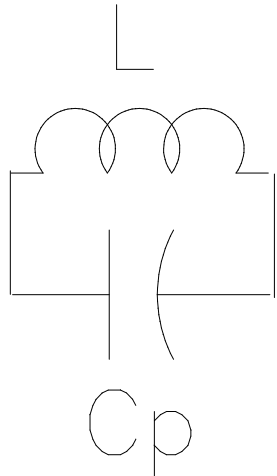Chip Inductor Parasitics - A First Approximation









Inductor (nH)	Associated shunt capacitance Cp (pF)
4	0.048
10	0.076
27	0.170
560	0.128

Sample data

- Inductors are Coilcraft 1008CS style
- Parasitic shunt capacitance should be included in circuit designs for best correlation between simulation and actual bench performance

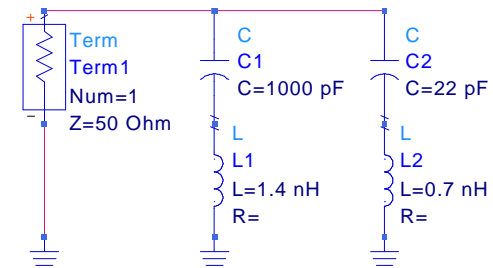
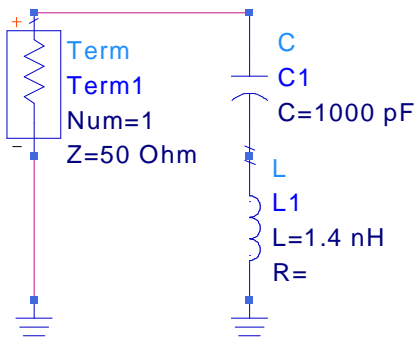
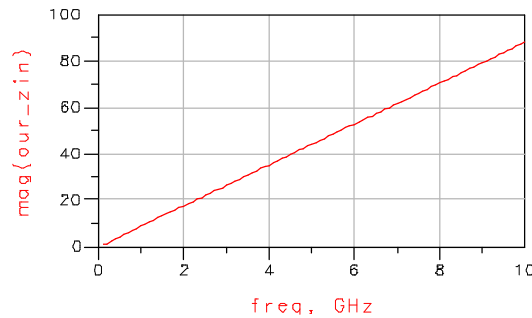
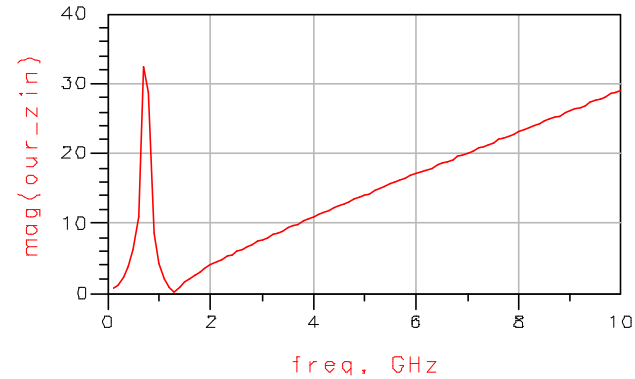
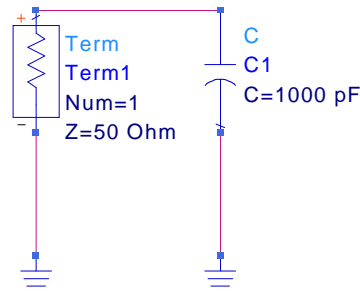
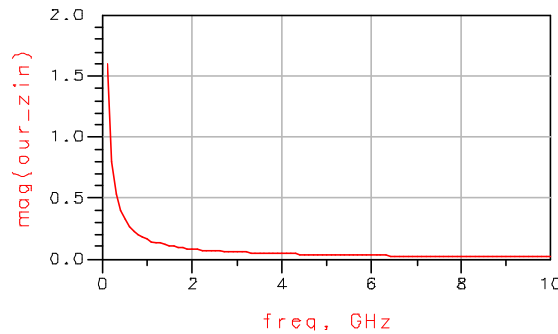
Effect of paralleling two capacitors of different values






Paralleling 2 caps of equal C and L cuts Z in half at all freq

Paralleling 22 pF cap with 1000 pF cap may lower Z at 1.2 GHz, however, Z at 0.8 GHz increases dramatically

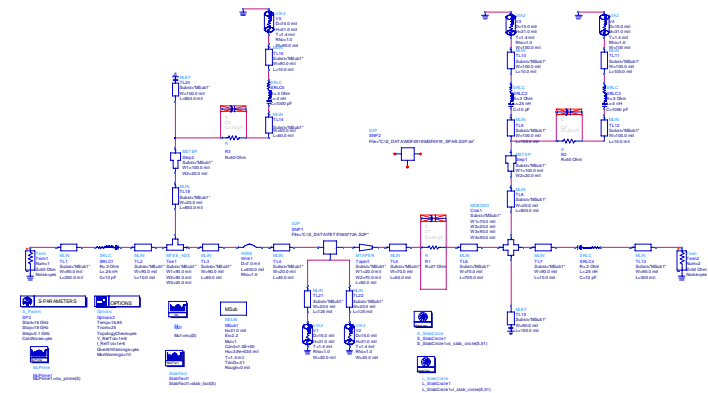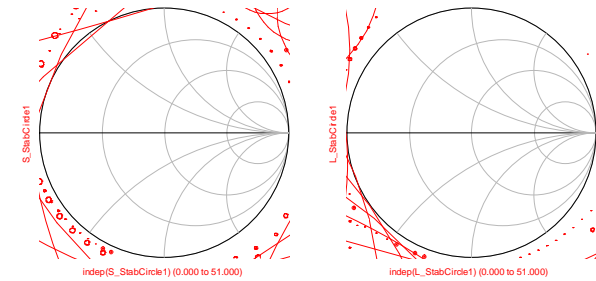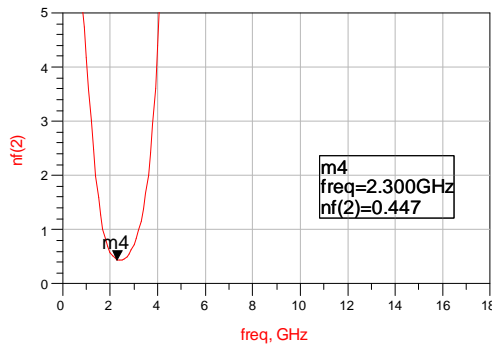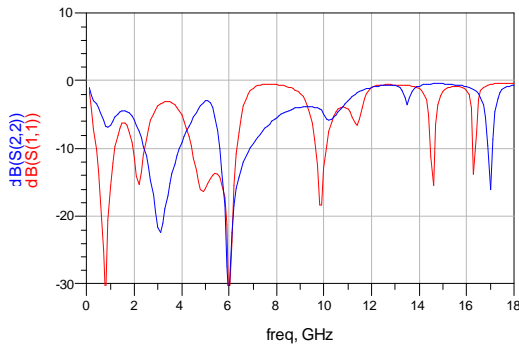
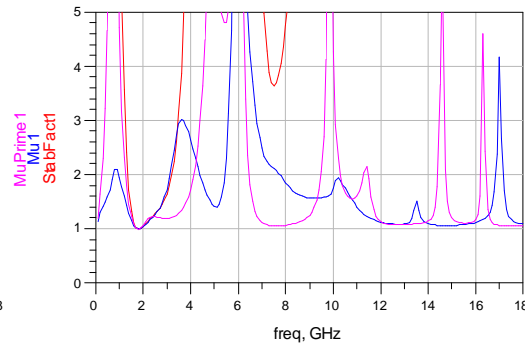
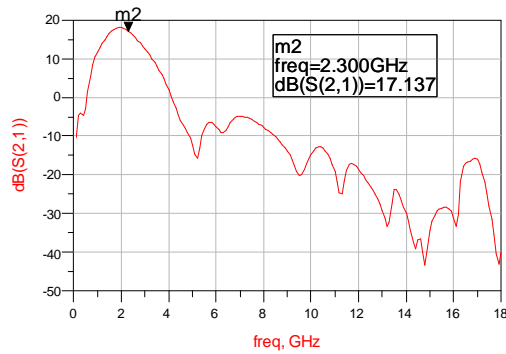
Single Stage ATF-36077 2304 MHz LNA with Nominal Source Inductance & 22Ω Drain Resistor



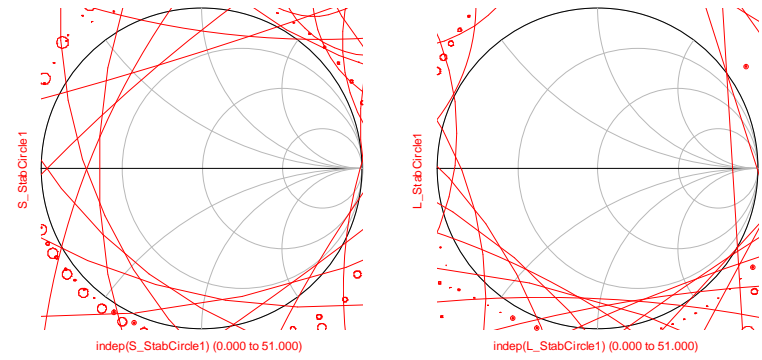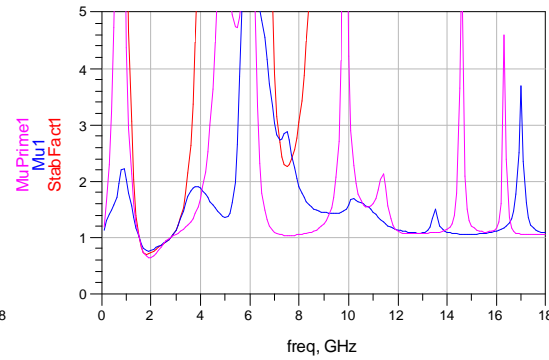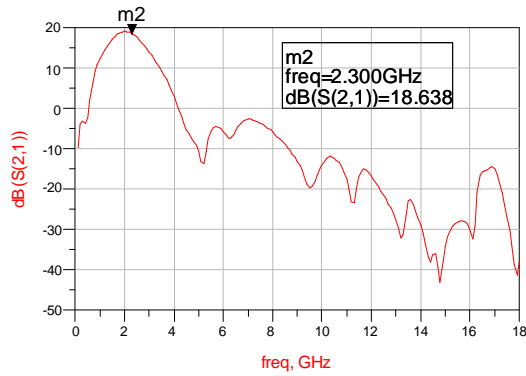Single Stage ATF-36077 2304 MHz LNA with Nominal Source Inductance & no Drain Resistor






Source and Load Stability Circles

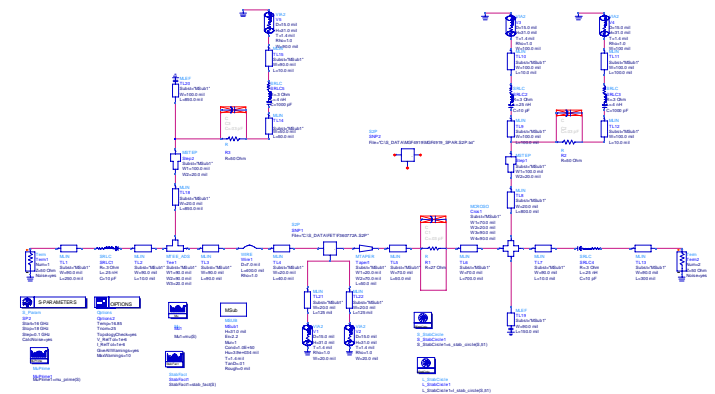
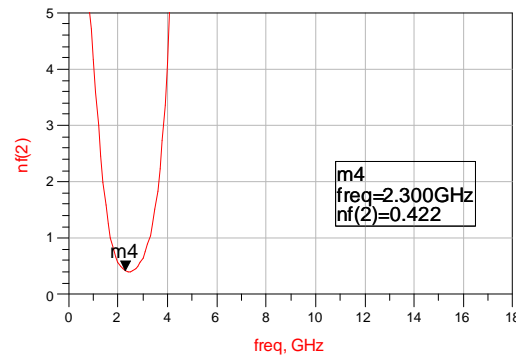
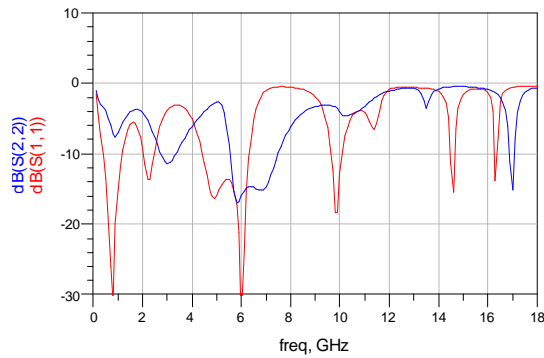


ADS Schematic

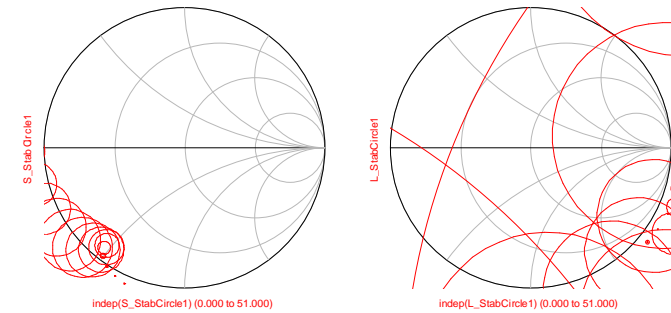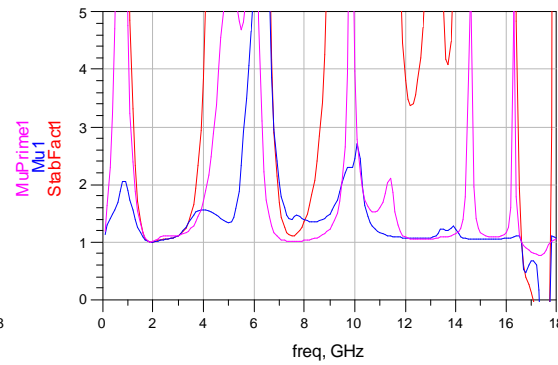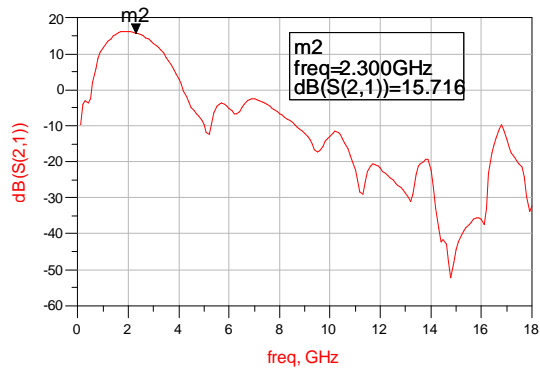Single Stage ATF-36077 2304 MHz LNA with Excessive Source Inductance



Source and Load Stability Circles

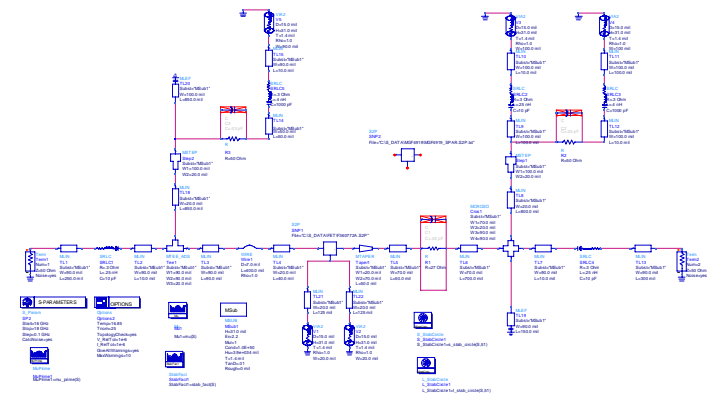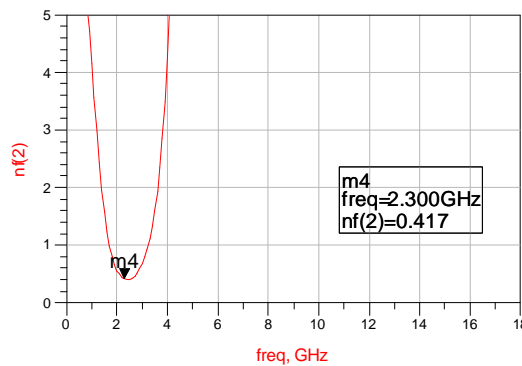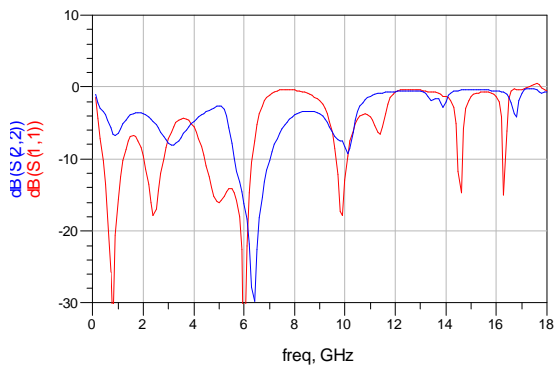

ADS Schematic





Single Stage LNA Designs

- **Easy to obtain low noise figure but difficult to obtain good stability mainly because of either gain peaking above or below the desired frequency of operation.**
- **Picking the right combination of source inductance and drain resistance can be difficult**
- **Best solution is a multi-stage LNA**





2 Stage LNA Designs

- The noise figure of a properly designed 2 stage LNA will only increase the noise figure of the LNA by the second stage contribution based on the gain of the first stage.
- Gain at the frequency of operation will normally be up to twice the gain of one stage with the exception at lower frequencies where 30 or 31 dB for a 2 stage may be the desired maximum based on stability.
- Provide a band-pass type response at the frequency of operation by rolling off the gain at lower frequencies and minimizing gain peaks especially at higher frequencies.
- Input return loss can often be optimized with the interstage network.





2304 MHz 2 Stage ATF-36077 LNA

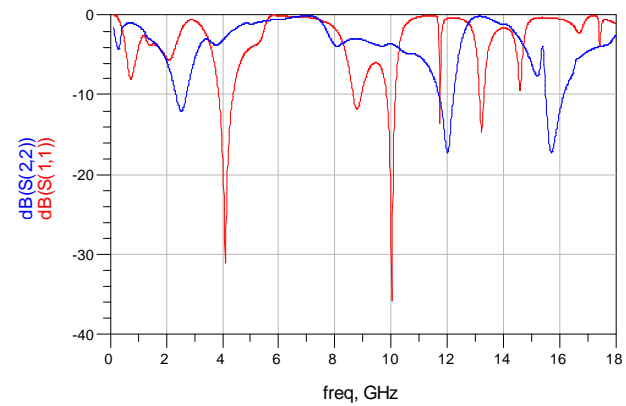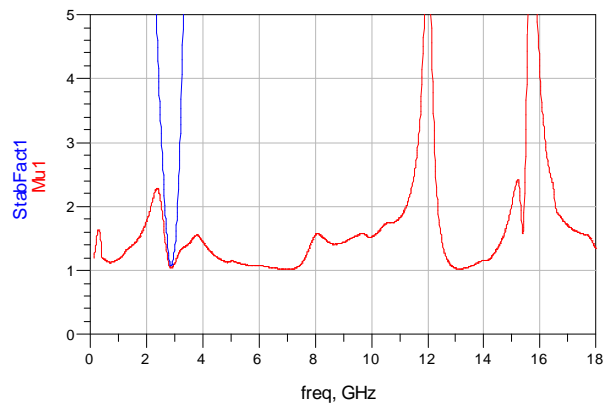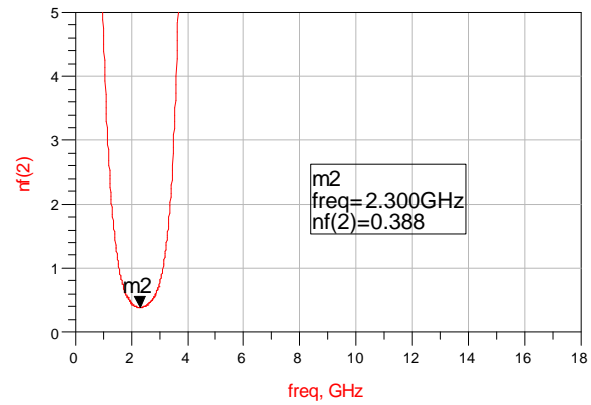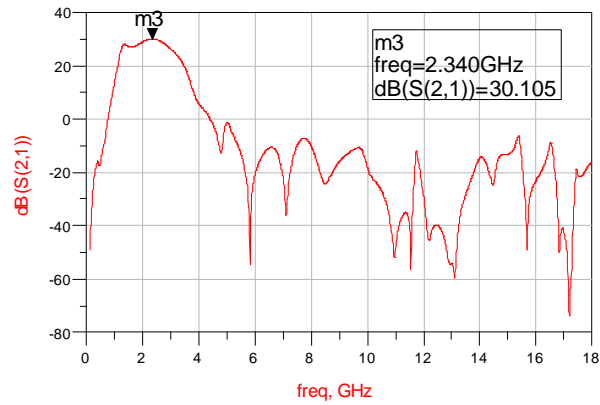





3456 MHz 2 Stage ATF-36077 LNA

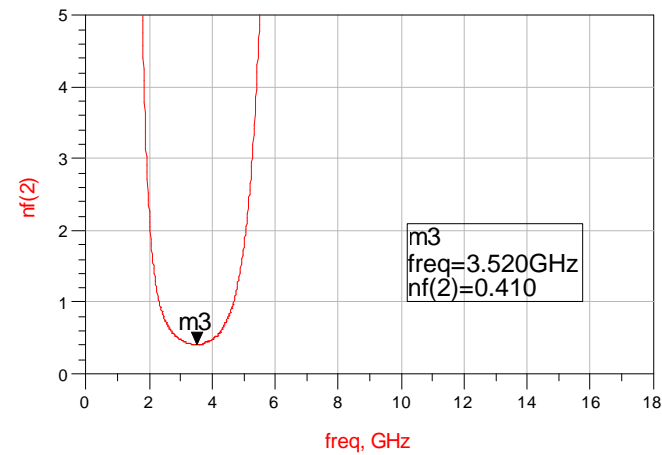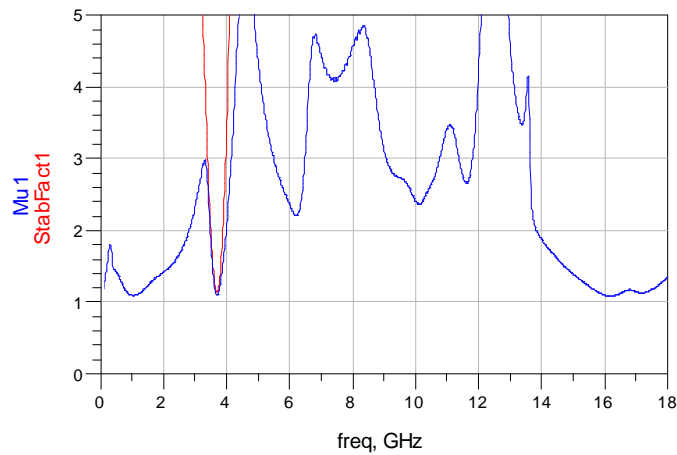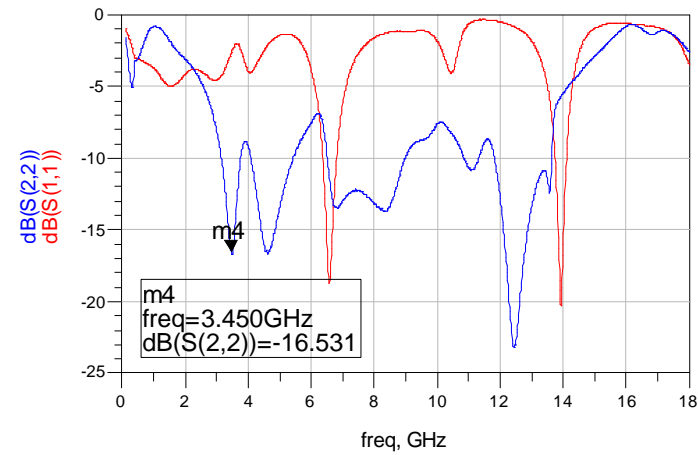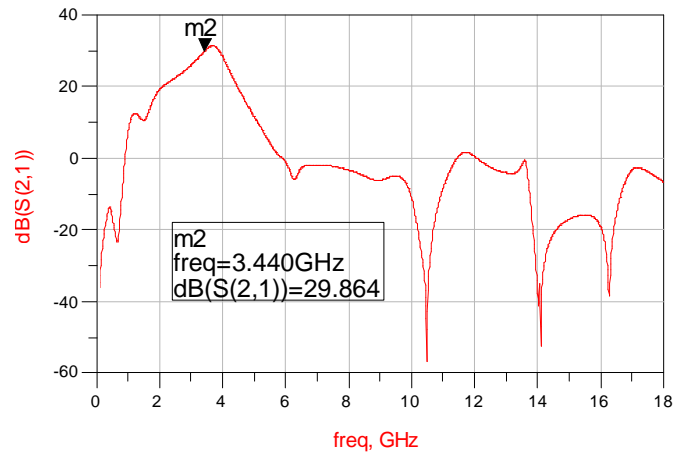


5760 MHz 2 Stage ATF-36077 LNA

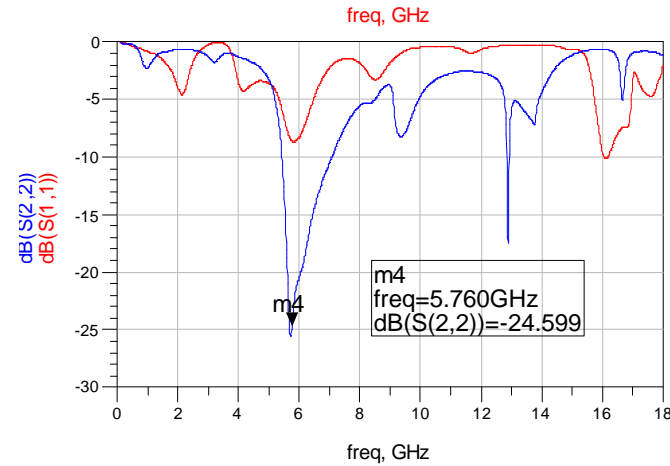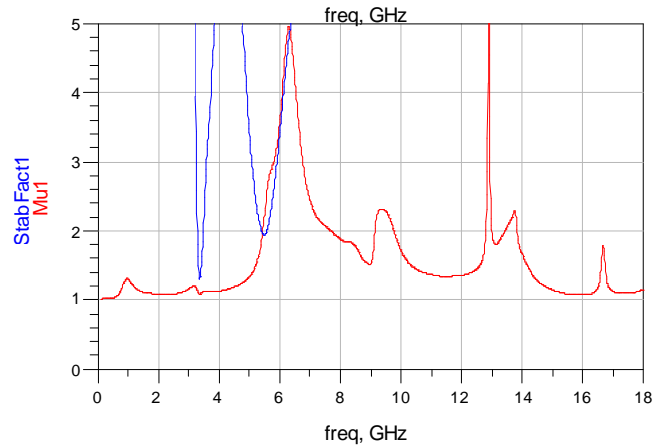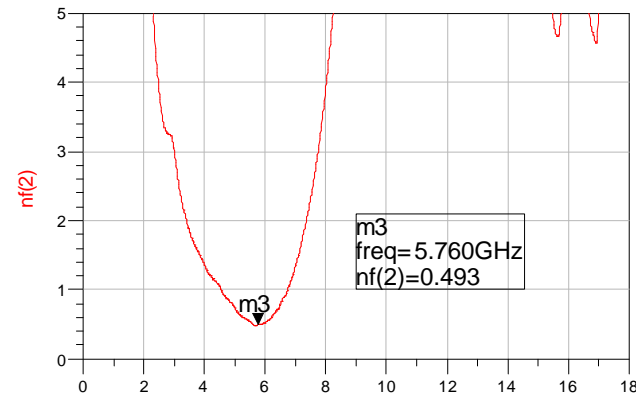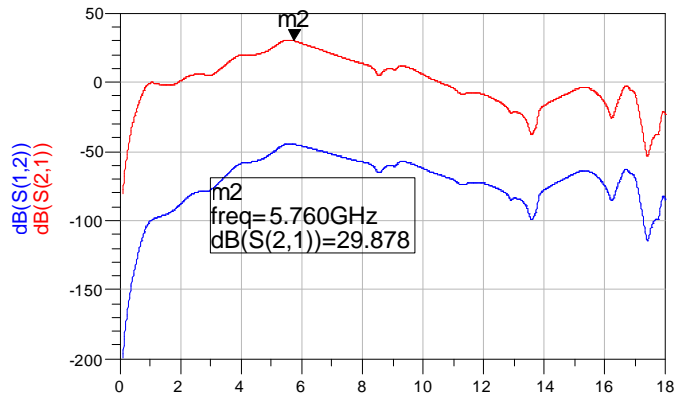

10368 MHz 2 Stage ATF-36077 LNA

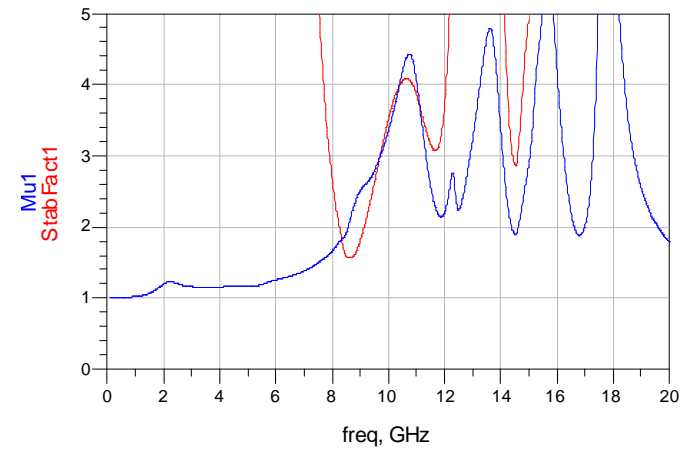
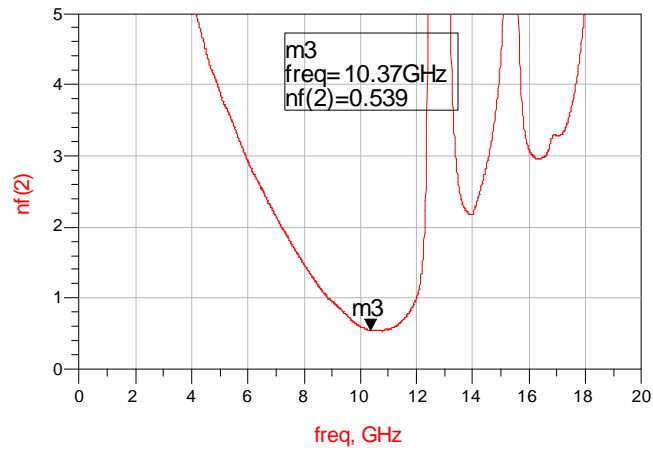
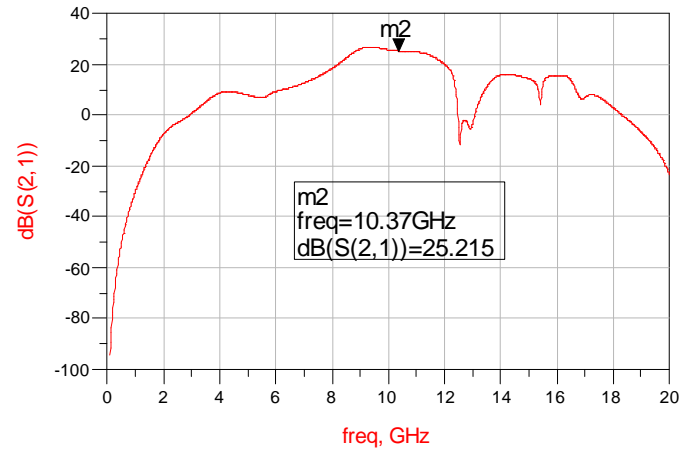
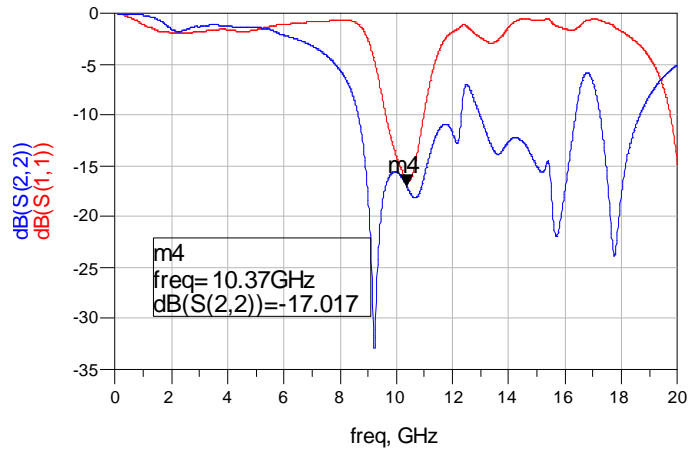


10368 MHz Single Stage ATF-36077 LNA

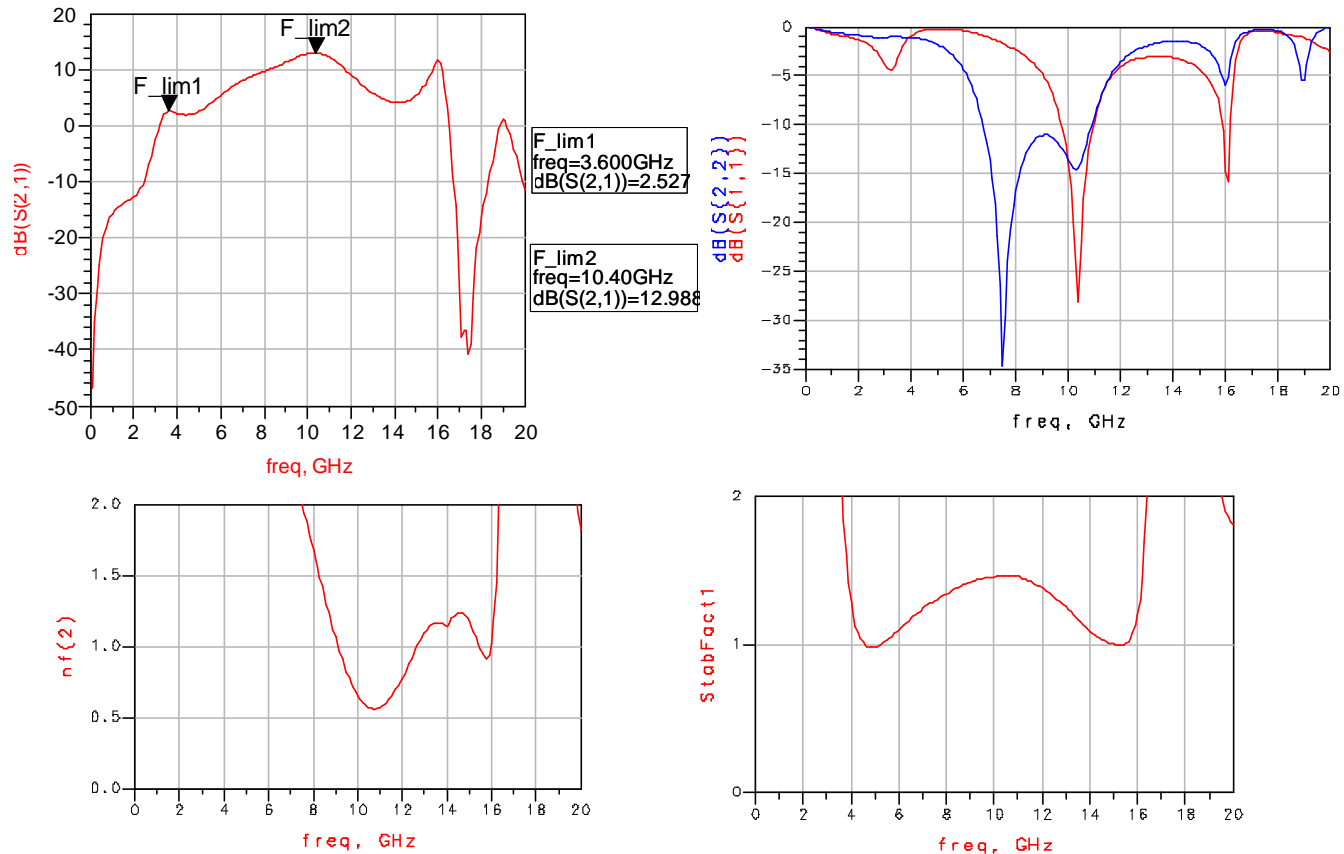

Gain peaking at 3.5 and 16 GHz can contribute to problems when cascading stages

8450 MHz 2 Stage ATF-36077 LNA

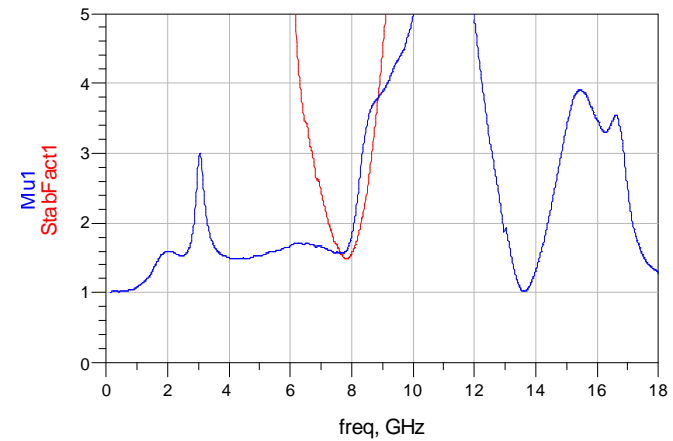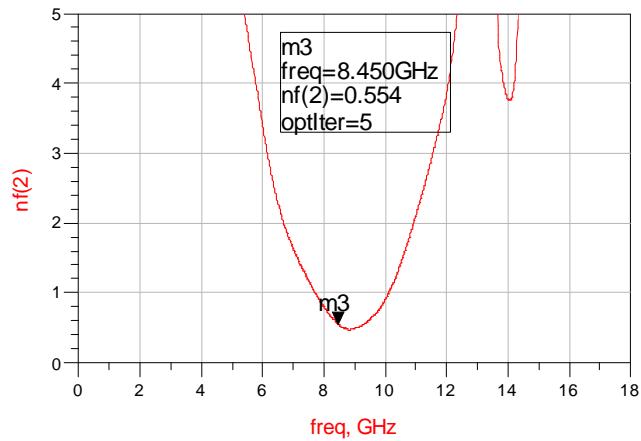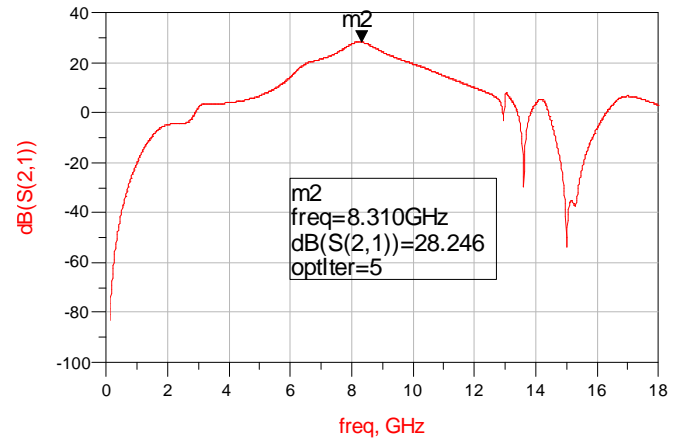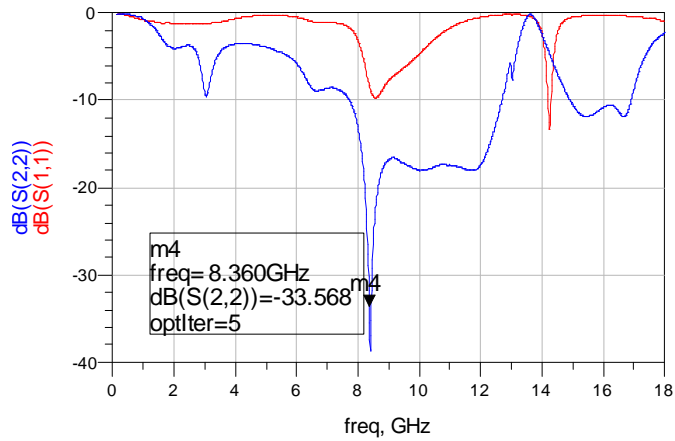

Summary

- New 2 stage LNA designs should offer a major improvement in stability over cascading individual stages.
- My presentation will be uploaded to www.ntms.org after the conference
- Any questions?
- Thanks and 73 de W5LUA