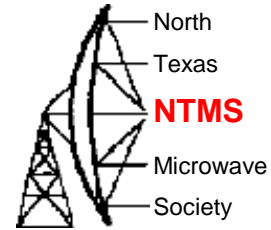


AA5C 222 MHz Transverter

Greg McIntire, AA5C



February 5, 2022

AA5C 222 MHz XVTR




- Objectives
 - Replace original home brew 50-220 MHz XVTR from the 90s with a 28-222 MHz XVTR for portable use or in the shack
 - Reference the LO to accurate 10 MHz source for digital (MSK144) work
 - ≥ 30 Watts RF out
 - Noise Figure ≤ 3 dB
 - Controls for use with external SSPA
- Approach
 - Start with a W1GHZ Mark 3 222 MHz XVTR Board
 - Add IF, PA module, TX driver, control, and switching


222 MHz XVTR Block Diagram

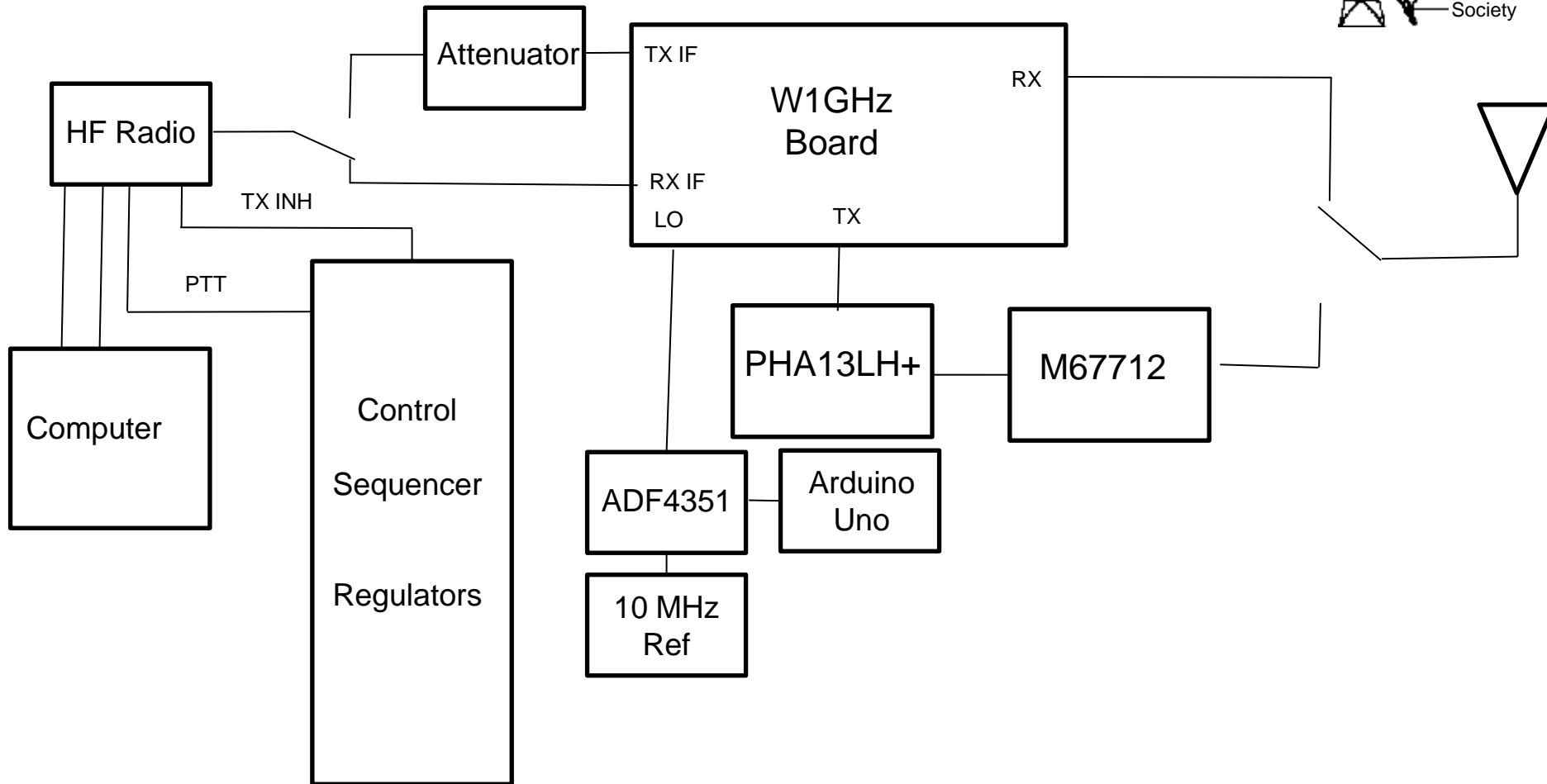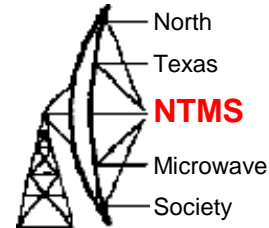

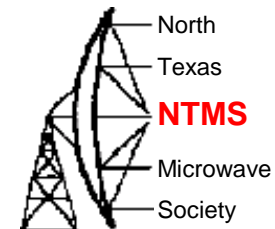
W1GHZ Mark 3 (2021) 222 MHz XVTR Board – Component Side



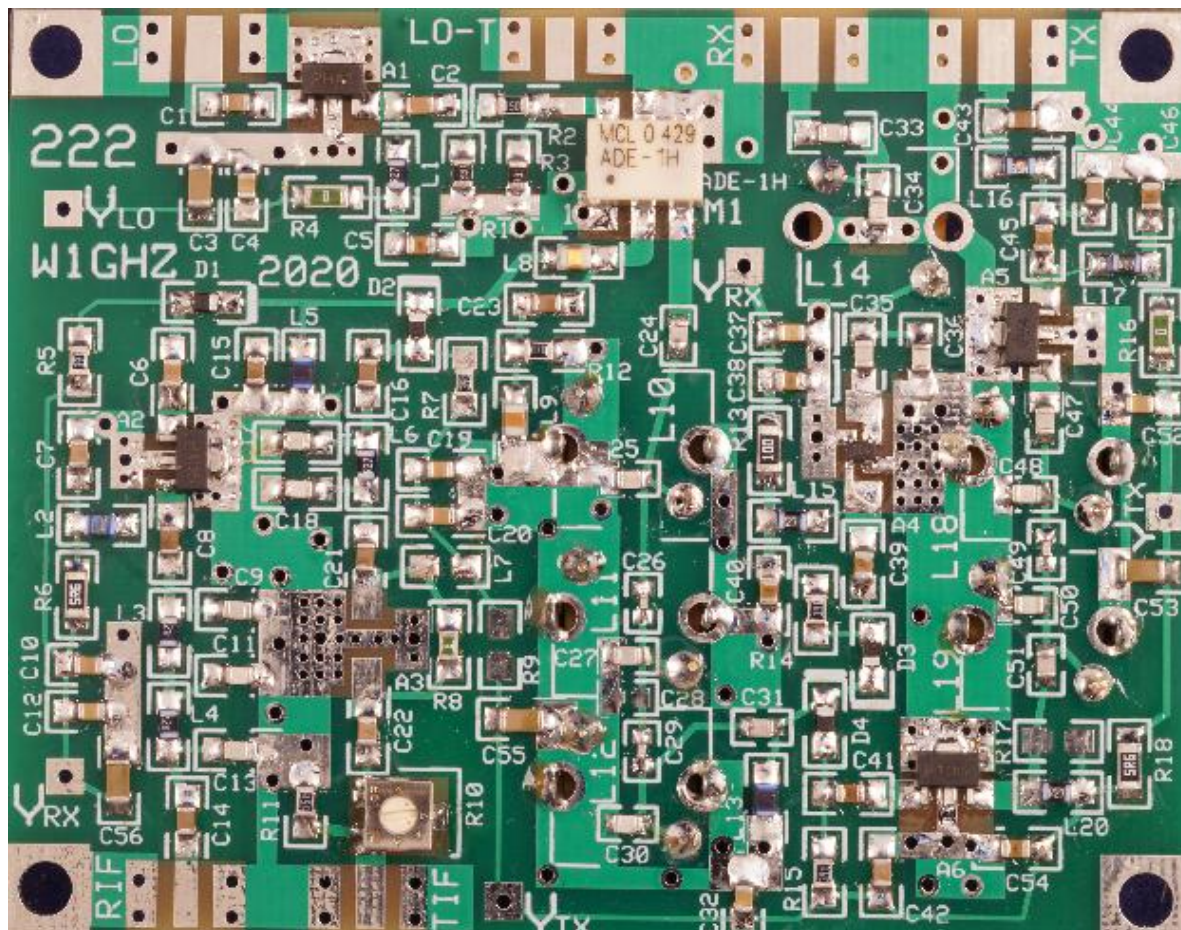
- Boards available from W1GHZ
- Paul can provide a project list of parts to order from Mouser (about \$70)
- Circuit Options
 - Mixer type and LO buffer
 - TX IF amp
 - LO test port



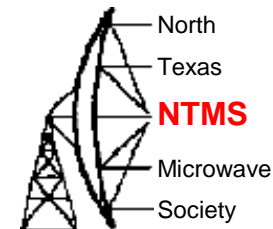
W1GHZ Mark 3 (2021) 222 MHz XVTR Board – Back Side



Cover intentionally left off

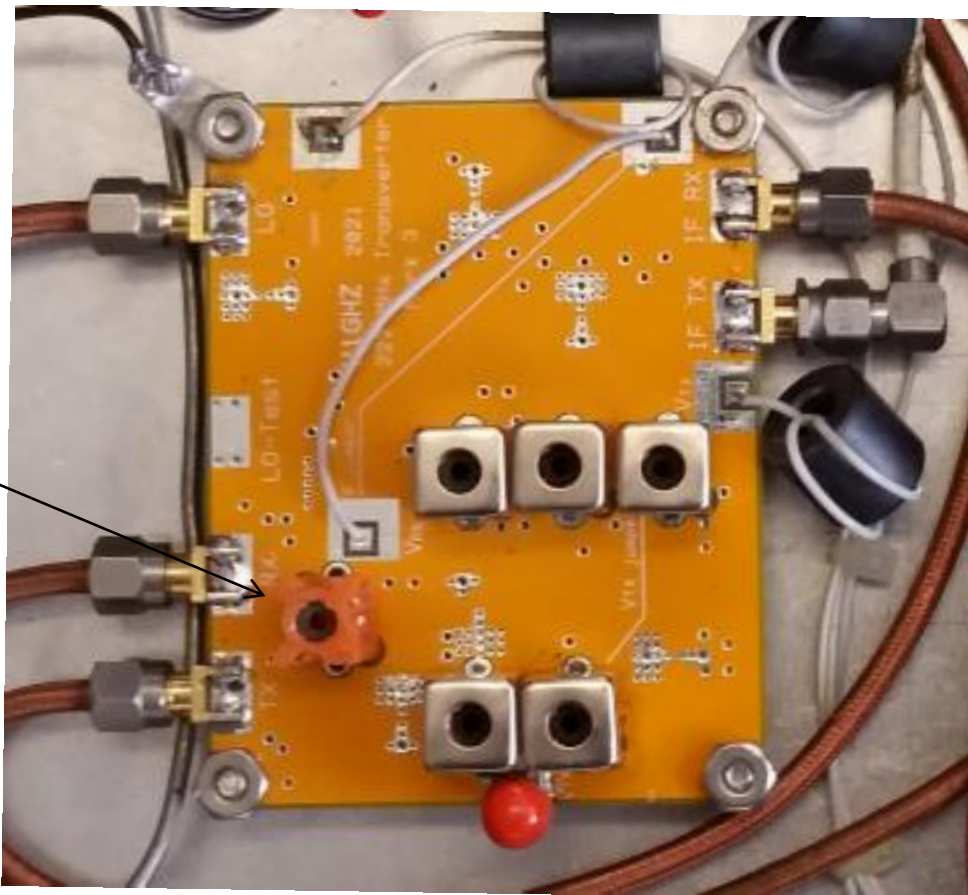

222 MHz XVTR Front Panel

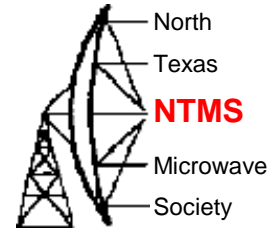


- Controls

- Power
- Enable TX
- PA Bias

- Indicators


- Power
- ADF4351 Locked
- Relative RF Output Power
- XVTR Keyed

222 MHz XVTR Back Panel

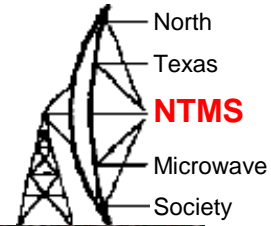

- Power In
- Fuse
- PTT In – ground to TX
- TX Inhibit – 12VDC current limited in RX mode, off in TX mode
- RF
- IF
- Ext Amp Key – relay contacts off sequencer

222 MHz XVTR Interior

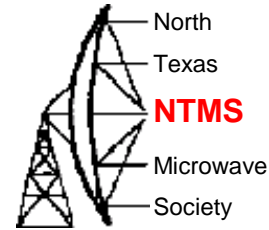


10 MHz OCXO Ref

TX Driver

PA

8" x 17" x 3" chassis

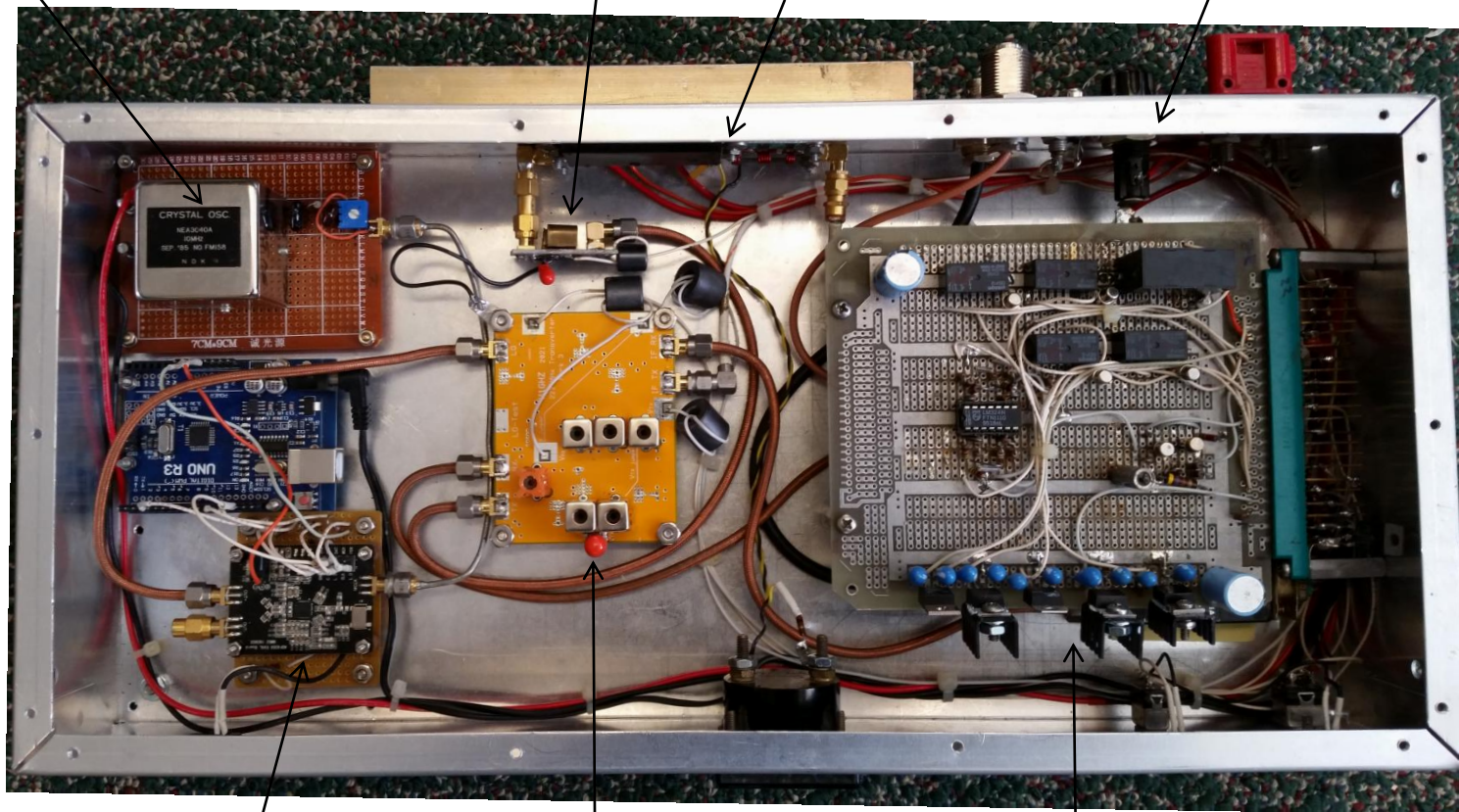



Arduino Uno

ADF4351

W1GHZ Board

Control/Sequencer/Regulators

RF and IF Relays and IF TX Attenuator

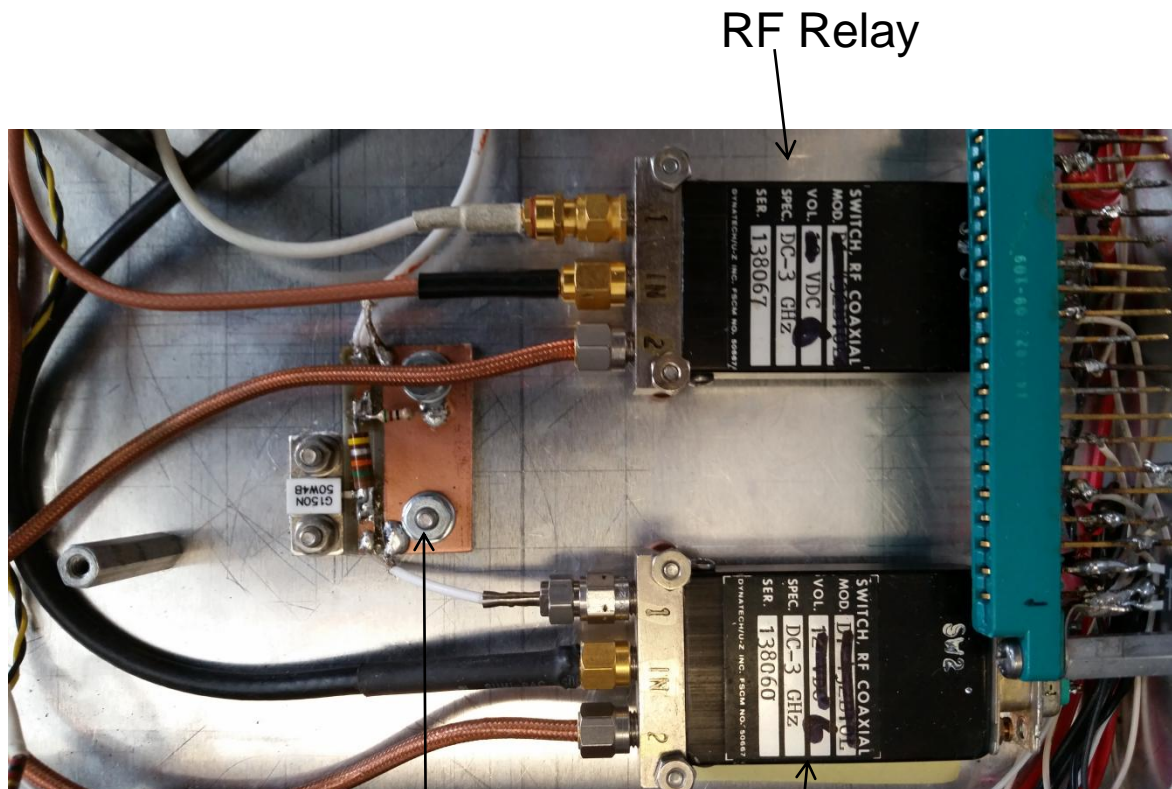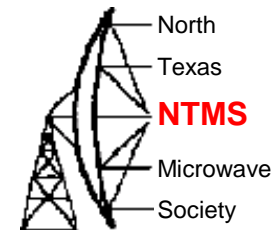


RF Relay

55 dB Attenuator

IF Relay

Located Under the Control Board to Save Space


28 MHz IF TX Attenuator

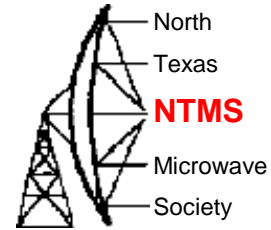


- 55 dB IF Attenuator
 - G150N 50W4B used for termination
 - 150 Watt Flange Mount
 - Used chassis for heat sink
 - DC-2.7 GHz
 - <\$8 at Mouser
- Target IF Rig is a Yaesu FT897D
 - No XVTR output available
 - Minimum selectable output power on 28 MHz is 5W
 - No variable drive control
 - Provides PTT output
 - Accept TX INH for holding off RF output




Power Amplifier Section

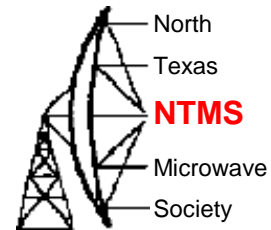

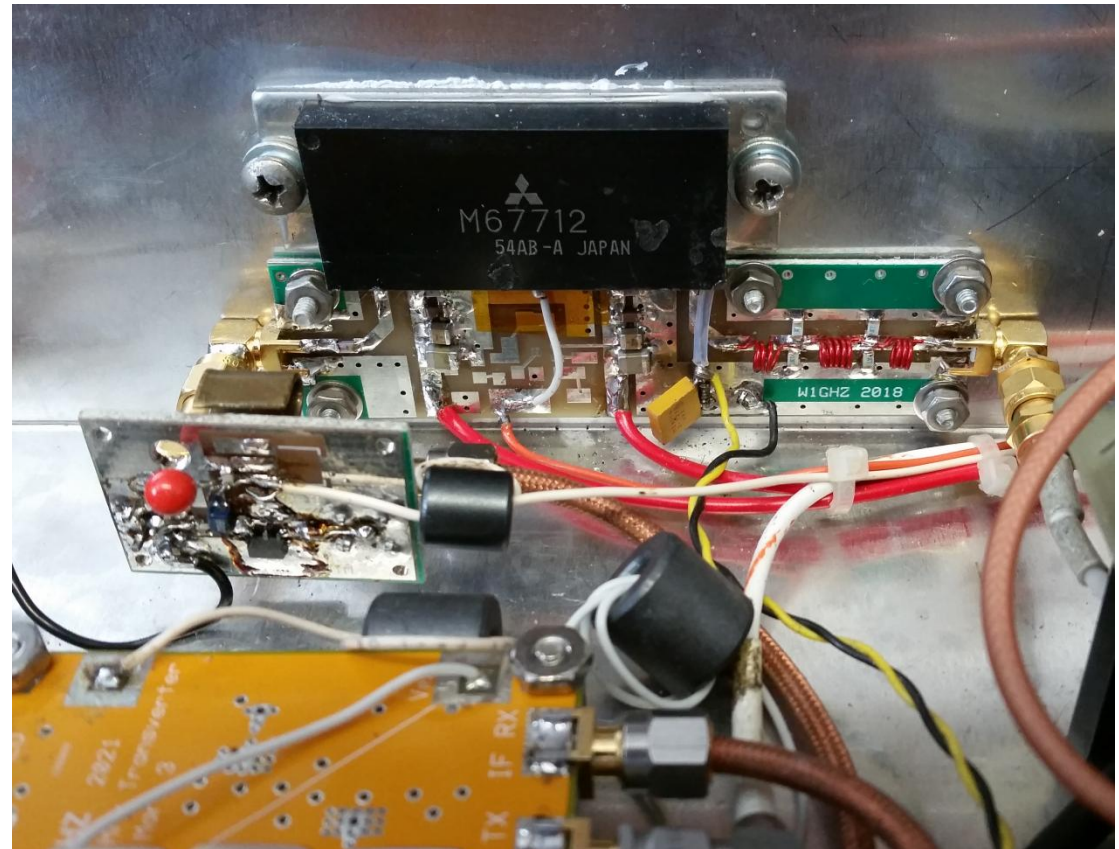- M67712 PA Module
 - 30W min, 40W max
 - +27 dBm max RF in
- PHA-13HLN+ Driver
- Output Low Pass Filter
- Output Power Detector
 - 1N5711 diode in parallel with 0.1 uF cap
 - Insulated lead close to output line for coupling
- M67712 bias line run from LM317 to control output power via front panel pot




RF Driver Amplifier

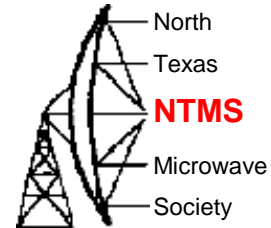


- Amplifies output of W1GHz Board to fully drive M67712 PA module
 - W1GHz board max output = +17 dBm. I set HF drive for -15 dBm input to the XVTR board to balance TX chain power levels
 - 27 dBm from driver to M67712 module for 40W out
- Used Mini-Circuits PHA-13HLN+ MMIC
 - 1 MHz to 1 GHz part
 - 23 dB gain at 250 MHz
 - P1dB 28.4 dBm at 250 MHz
 - SOT-89 Package
 - ~250 mA at 8V = 2W power input => lots of plated through holes and heat sinking on back of board for cooling
 - ~ \$10 each at Mini-Circuits
- Two Lessons Using This Part
 - VERY static sensitive
 - Had failure at rated 8 VDC Vd so reduced Vd to 6 VDC

222 MHz XVTR Performance

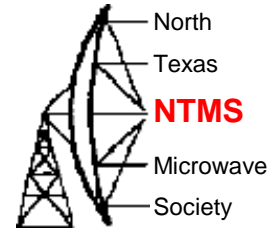

- Transmit
 - 40 Watt output power - max from M67712 module
 - Power meter set for full scale at 40 W output
 - PA Bias control provides variable drive level to 1 KW SSPA
- Receive
 - 2.1 dB NF
 - 22.8 dB gain
- General
 - Takes OCXO about 15 minutes to warm up but then very stable

222 MHz XVTR Summary

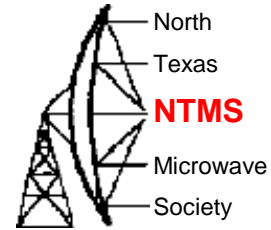

- Result is a nice, modern 28 MHz to 222 MHz XVTR for about \$200 total parts
- W1GHZ board worked well and Paul provides good documentation
 - Several areas of flexibility depending upon your needs
 - Did have a TX oscillation issue that was dependent on board height above the chassis
- Mitsubishi power modules still available for a reasonable price on eBay
- Sequencer mandatory
 - Easy to blow out IF RX back end if you aren't careful
 - TX INHIBIT control to Yaesu FT-897D a weak but manageable link in the system.