

Impedance Matching Techniques

Jose H Arreguin Martinez

KG5YQO

Outline

- Importance of Impedance Matching
- Matching with discrete components
- Matching with Quarter wavelength
- Stepped Impedance
- Practical Impedance Matching – Quarter Wavelength Coax

Importance of Impedance Matching

- Needed for High Power Amplifiers

- Example:

- $V_{DD} = 50V, P_{out} = 100W$
 - $\frac{V_{DD}^2}{R} = 2 \times P_{out}$, Consider AB Class or “Greater”
 - $\frac{50^2}{2 \times 100} = R, R = 12.5\Omega$, Most likely lower impedance than this approximation

- GaN Amplifiers

- MMRF5014 – Datasheet on the right
 - Narrowband Optimal at lower impedances for power gain and efficiency

f MHz	Z _{source} Ω	Z _{load} Ω
500	1.3 + j3.9	5.9 + j3.5
1000	1.0 + j0.3	5.5 + j2.9
1500	0.8 - j0.5	3.4 + j2.0
2000	1.2 - j2.0	4.7 + j0.3
2500	2.7 - j3.8	3.7 + j1.4

Z_{source} = Test circuit impedance as measured from gate to ground.

Z_{load} = Test circuit impedance as measured from drain to ground.

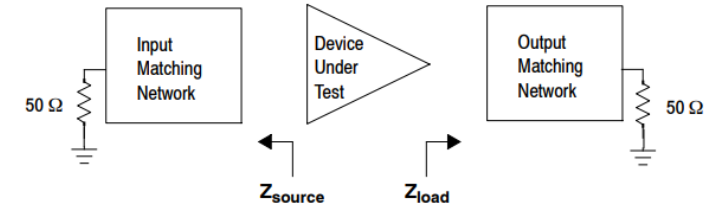


Figure 7. Narrowband Fixtures: Series Equivalent Source and Load Impedances

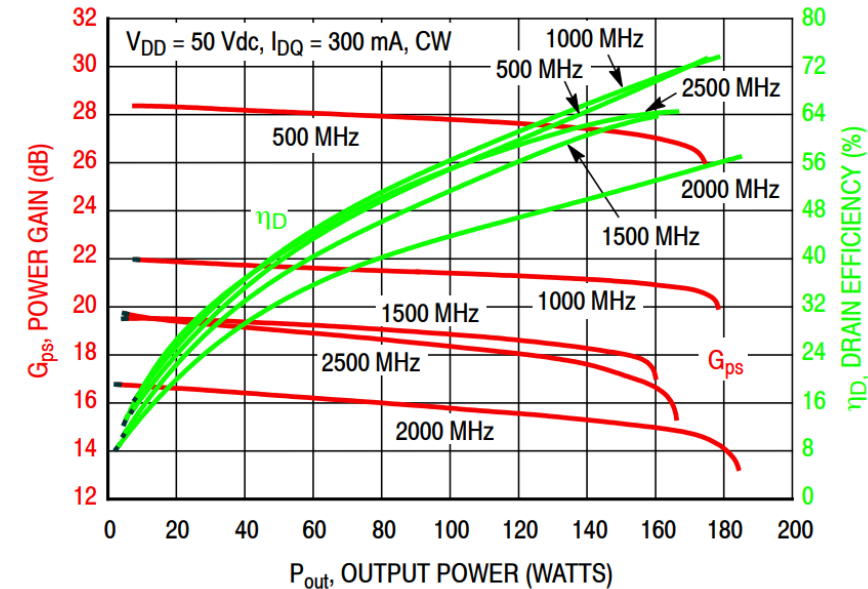


Figure 6. Power Gain and Drain Efficiency versus CW Output Power

Matching with Discrete Components

- Advantages:



- Simple

- Disadvantages:

- Limited to HF, VHF, UHF
- Narrowband



- Note: $Q = \frac{f_c}{BW}$

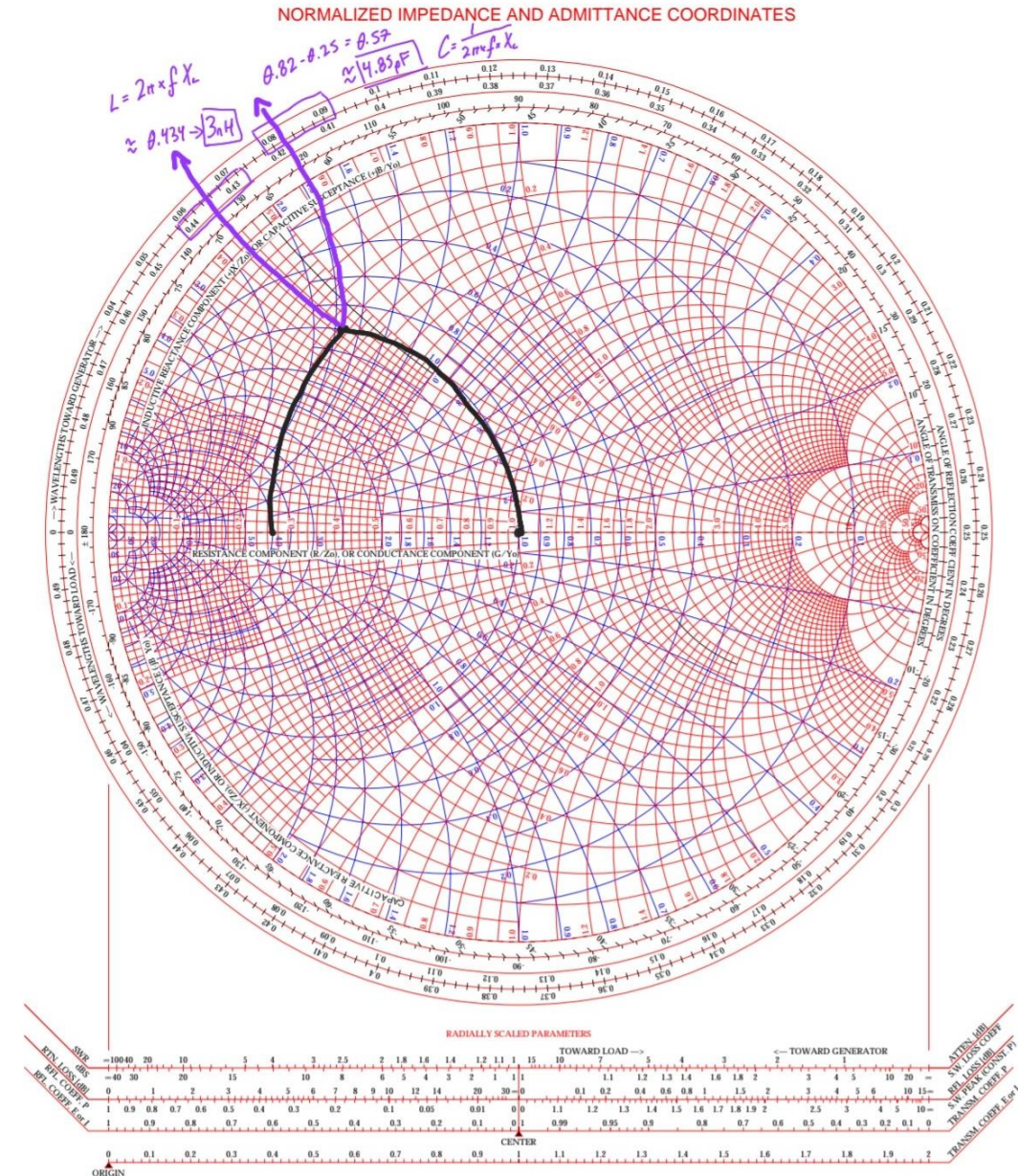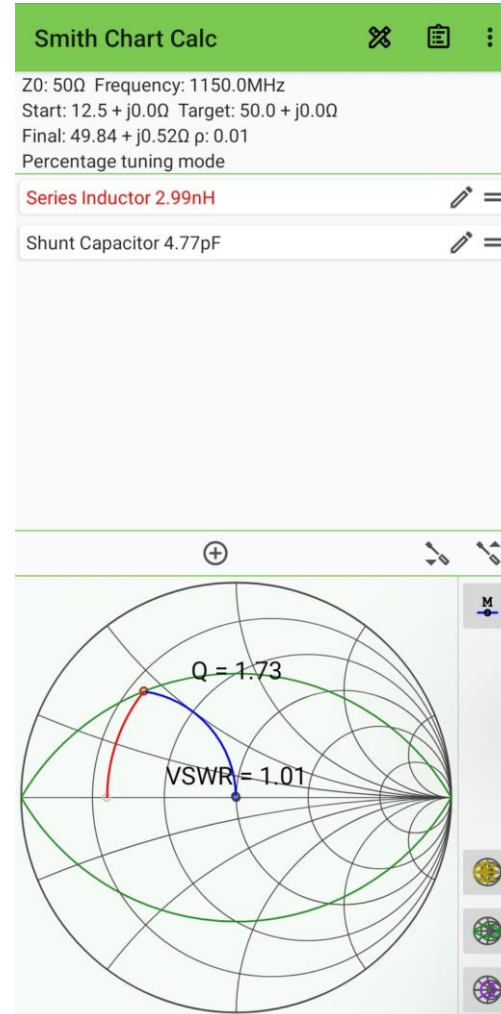- $BW = \frac{1150 \text{ MHz}}{1.73} = 664 \text{ MHz}$



Example



- 10 dB BW = 518 MHz

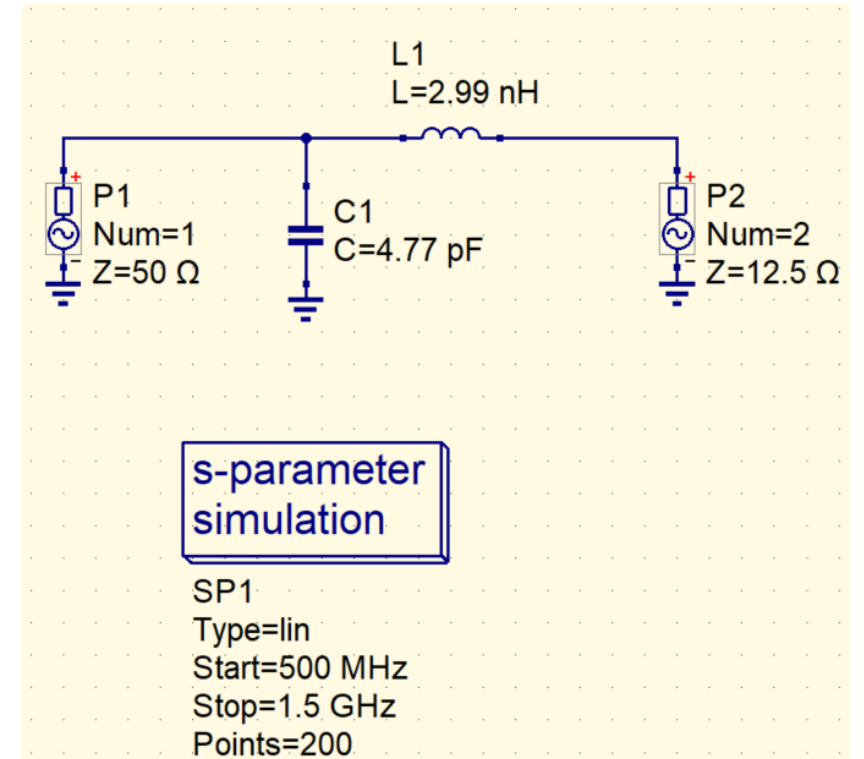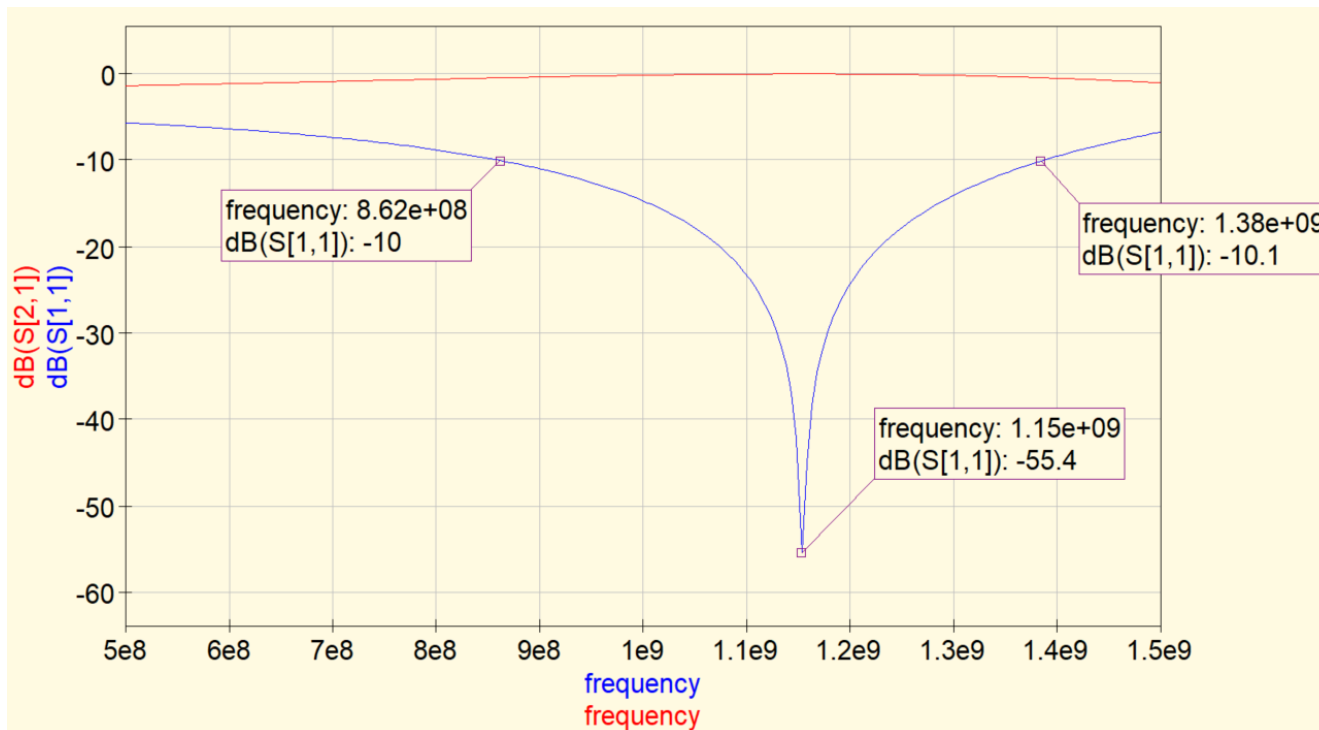

Quarter Wavelength Transformer

- Advantages:
 - “Simple”
 - Usable at higher frequencies
- Disadvantages:
 - Narrowband
 - Difficult to tune if first shot doesn't come out as expected.



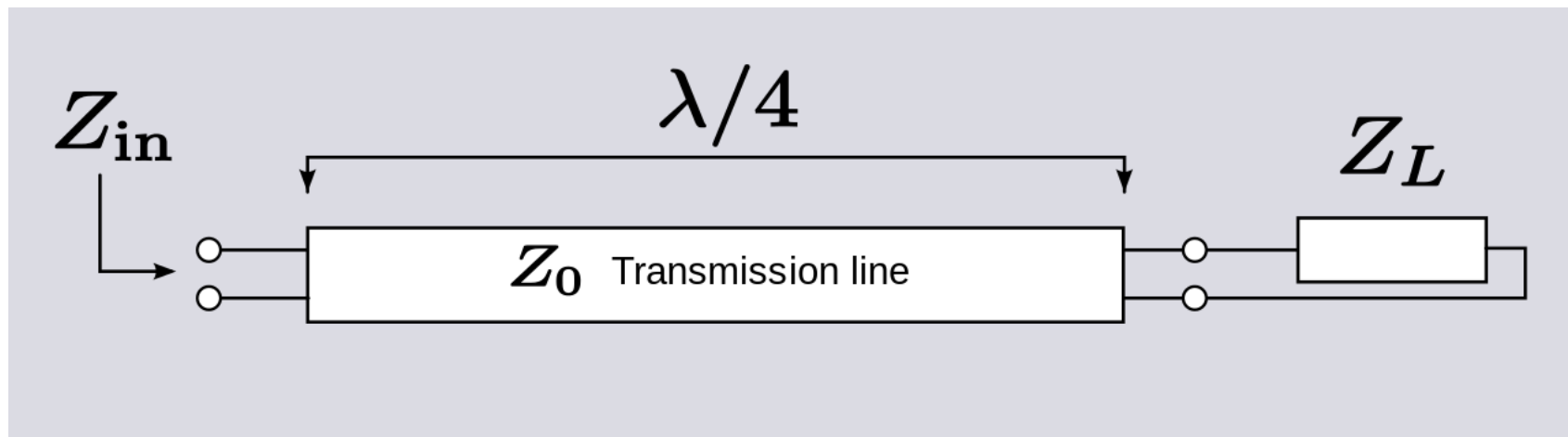
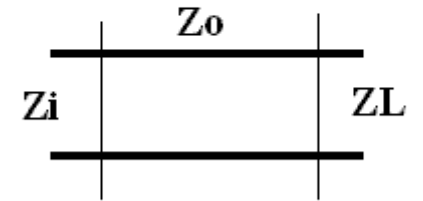
$$Z_i = \frac{Z_0^2}{Z_L} \quad Z_0 = \sqrt{Z_i Z_L}$$



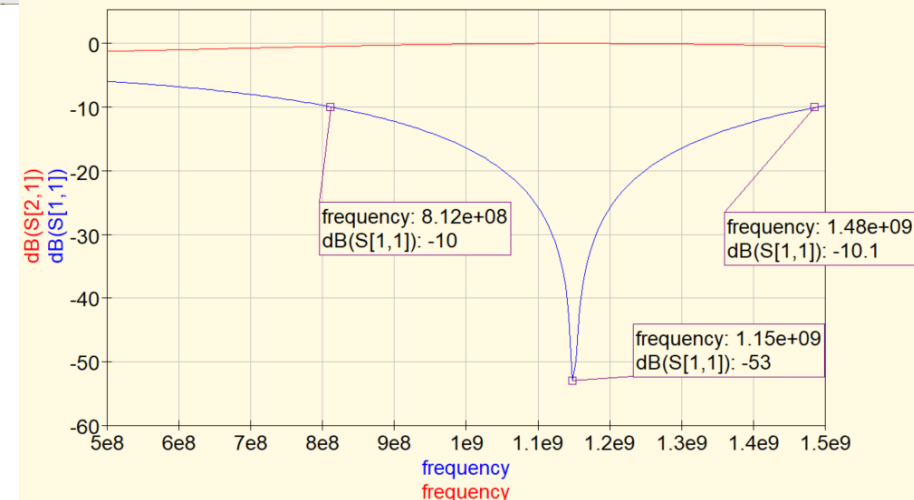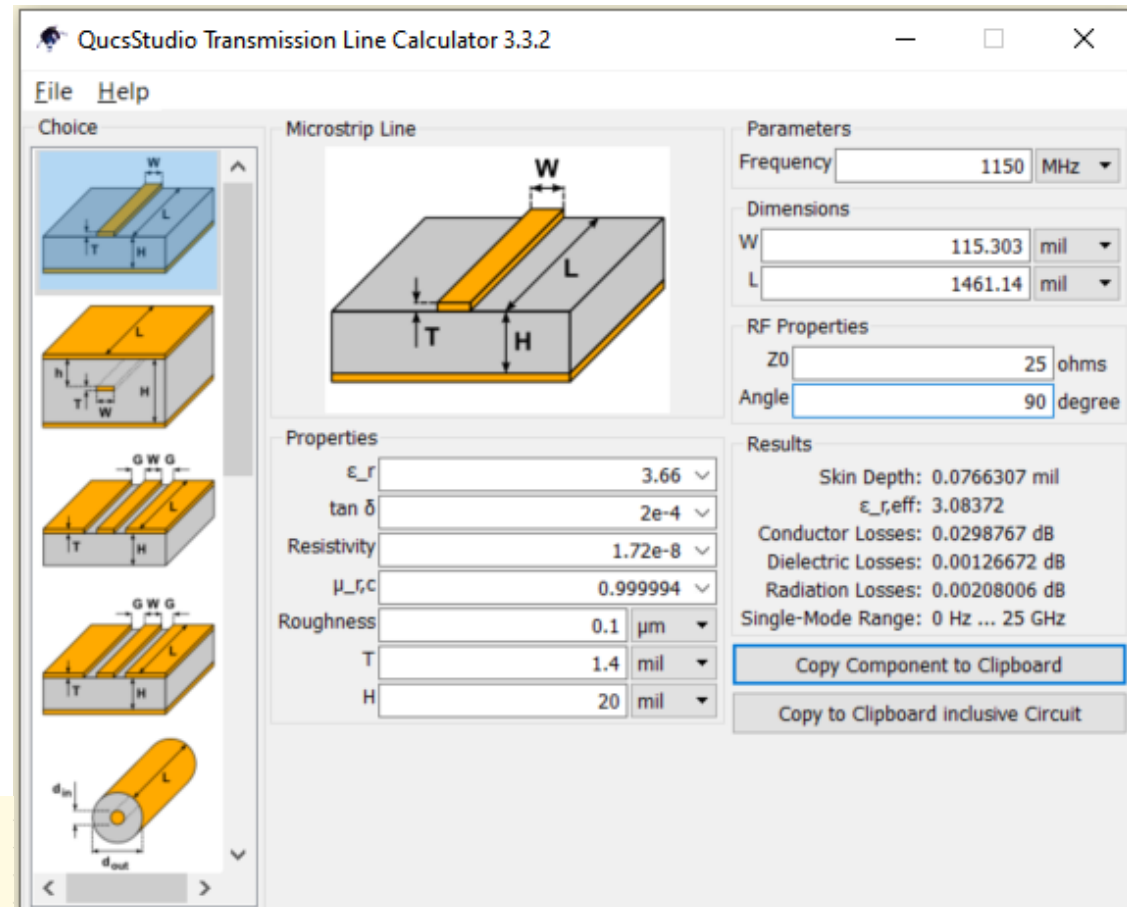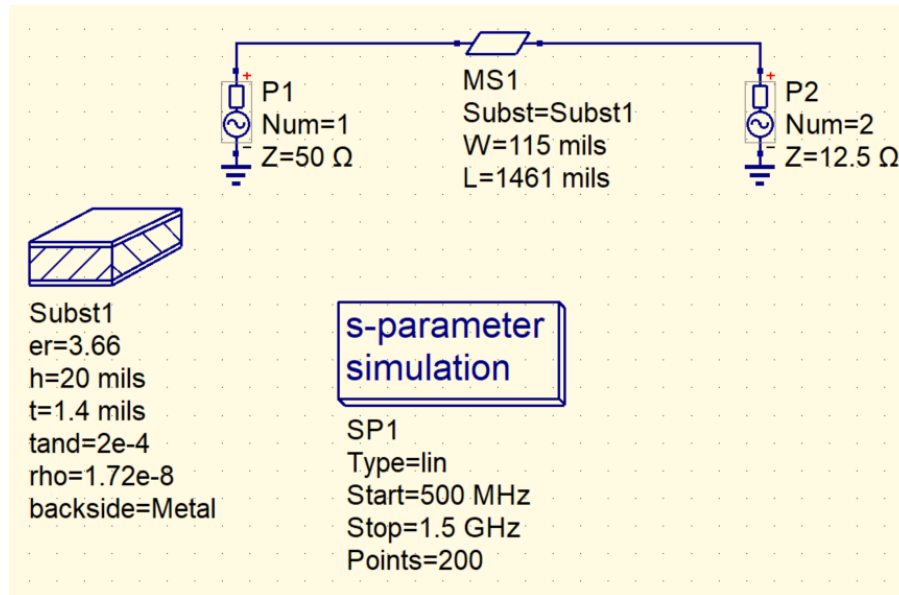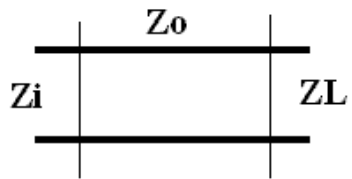Example

- R04350B, 20 mil thickness, 1oz
 - $Z_0 = \sqrt{50 \times 12.5}$
 - $Z_0 = 25 \Omega$
- BW = 668 MHz

$$Z_i = \frac{Z_0^2}{Z_L} \quad Z_0 = \sqrt{Z_i Z_L}$$



Stepped Impedance

- Advantages:


- Broadband

- *Note:* $Q = \frac{f_c}{BW}$

- $BW = \frac{1150 \text{ MHz}}{0.77} = 1493 \text{ MHz}$



- Disadvantages:

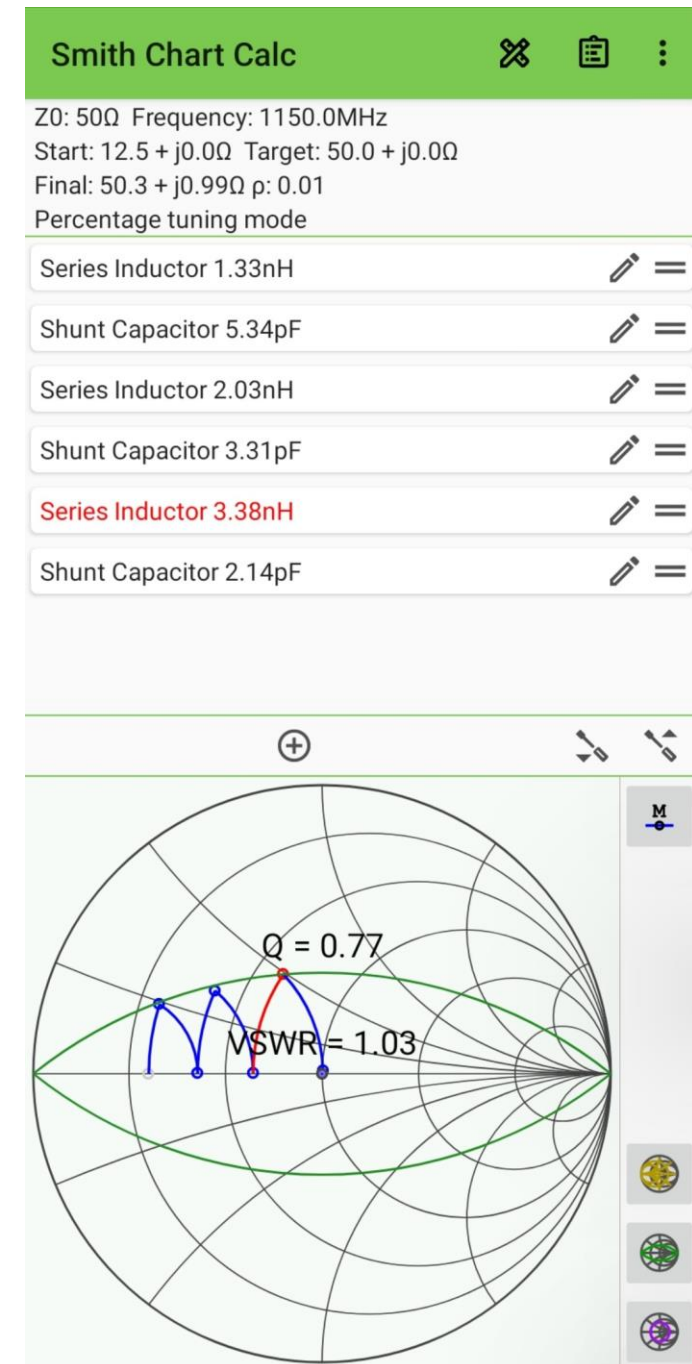- Difficult to implement and correct if board doesn't turn out as expected.





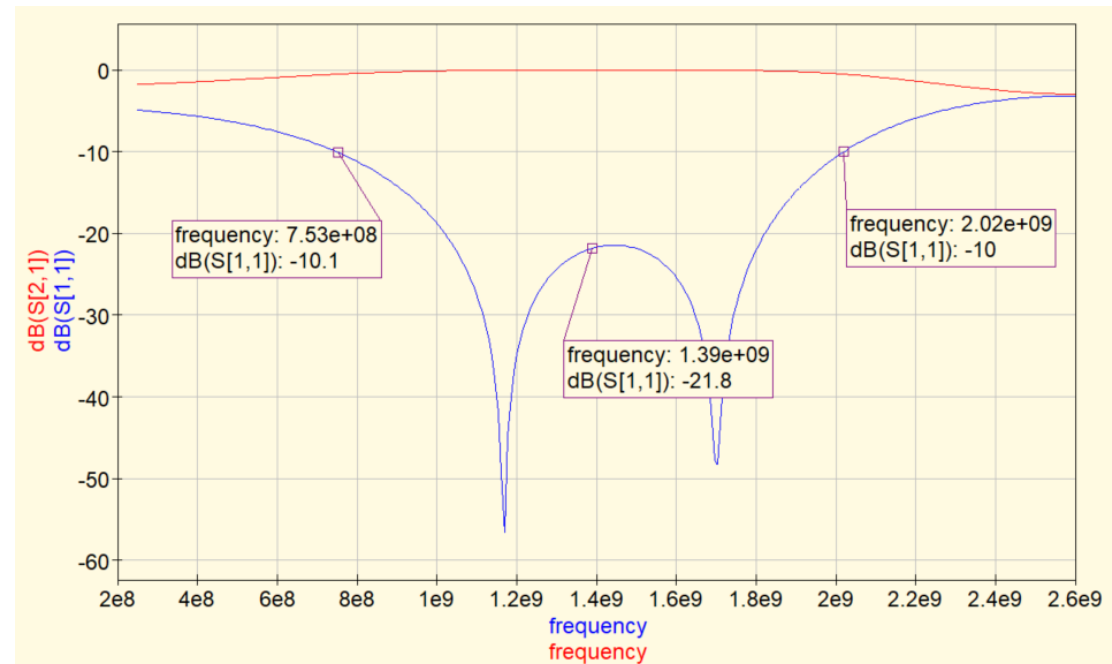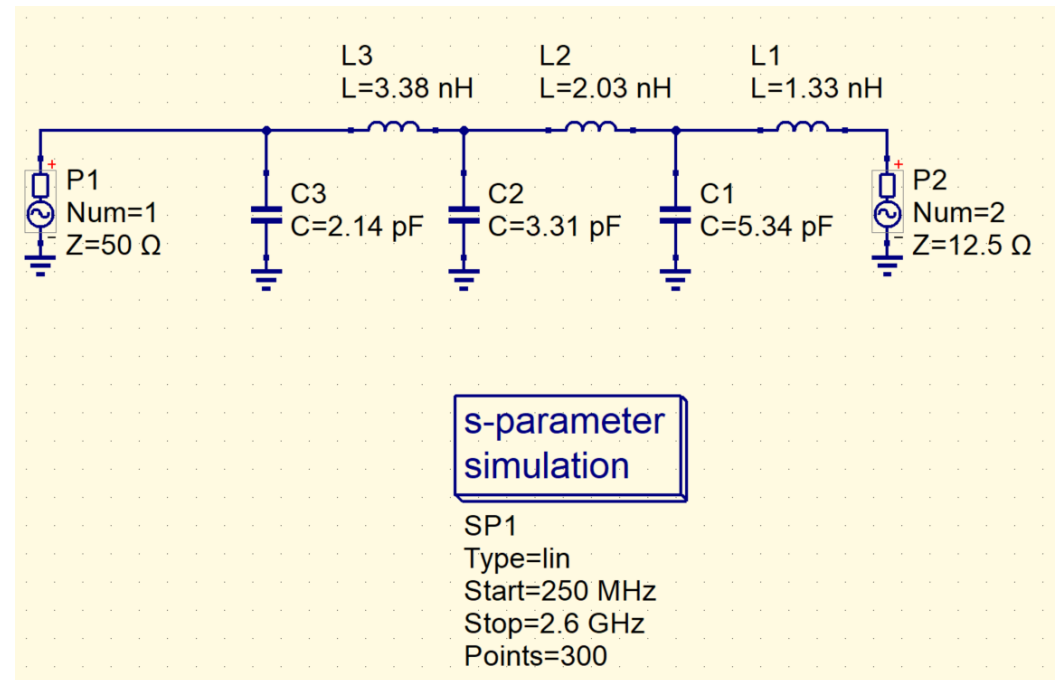Example

- Simulated BW = 1267 MHz
- Although, impractical due to inductances/capacitances non-ideal.
- Required to design using microstrip distributed elements.





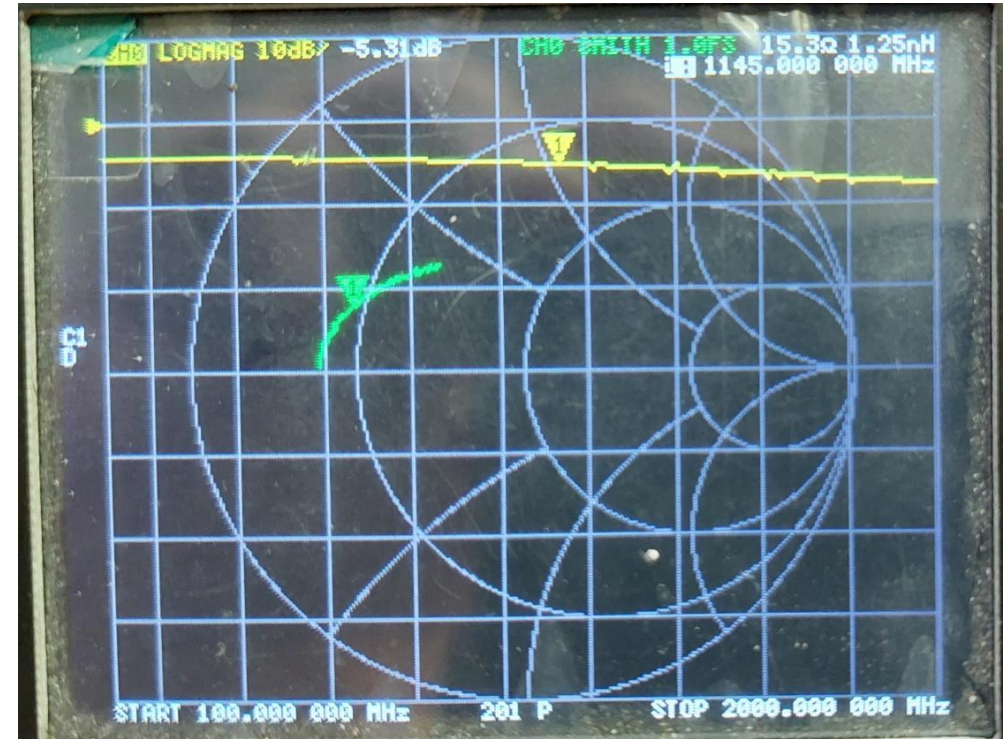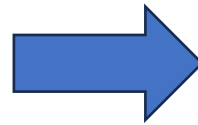Practical Impedance Matching – Direct connection from 50Ω to 12.5Ω – no matching



Practical Impedance Matching – Quarter Wavelength Coax

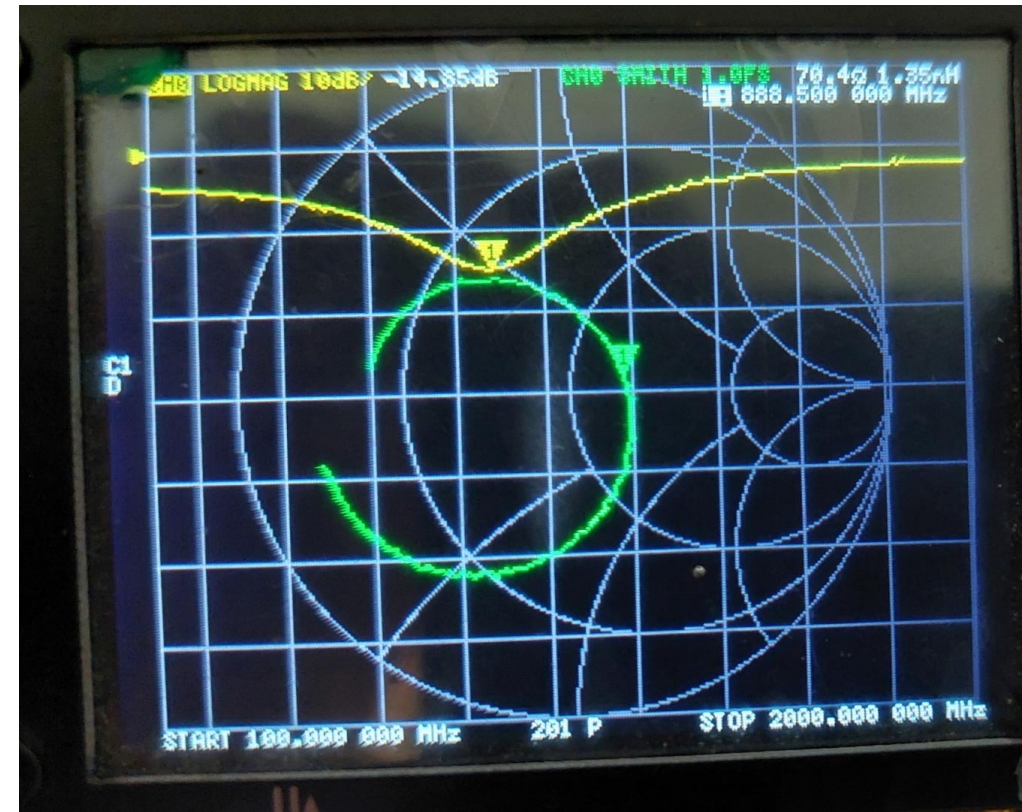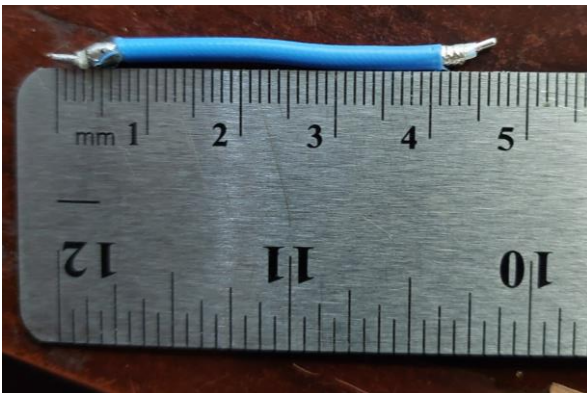- Assumed Propagation velocity: 70% (V_p)
- $\frac{c}{f} \times V_p = \lambda \text{ in Coax}, \frac{300}{1150} \times 0.70 = 182\text{mm}$
- $\lambda/4 = 45\text{mm}$
- 888.5 MHz



Practical Impedance Matching – Quarter Wavelength Coax - Tuning


- Knowns:

- 888.5 MHz
- 182 mm length, λ

- Unknowns

- V_p ?
- $\frac{c}{f} \times V_p = \lambda$ $V_p = \lambda \times \frac{f}{c}$

- $V_p = 53.9\%$

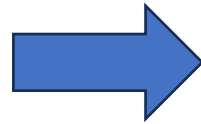






- Assumed Propagation velocity:
53.9% (V_p)

- $\frac{c}{f} \times V_p = \lambda$ in Coax, $\frac{300}{1150 \text{ MHz}} \times 0.539$
= 140mm

- $\lambda/4 = 35.1\text{mm}$

Practical Impedance Matching – Quarter Wavelength Coax - Tuning

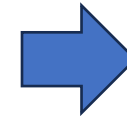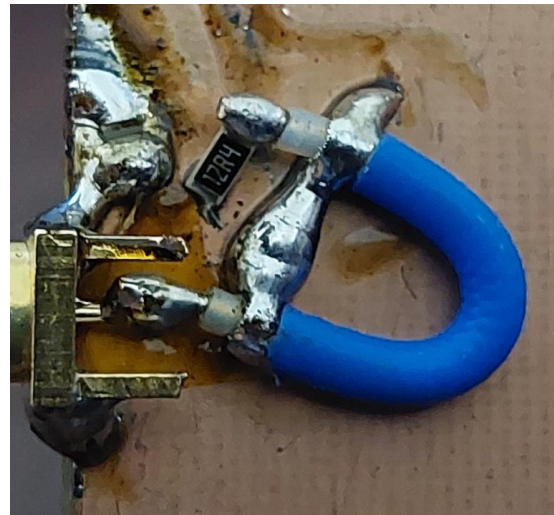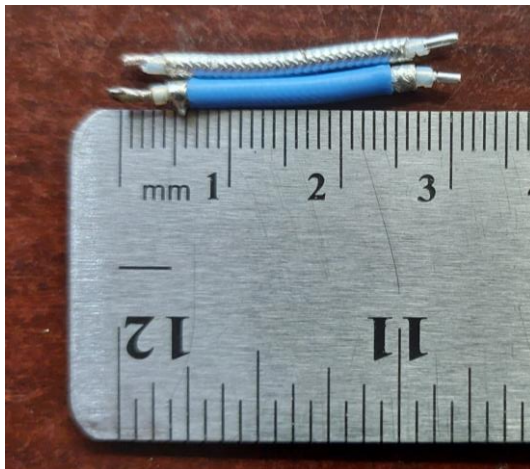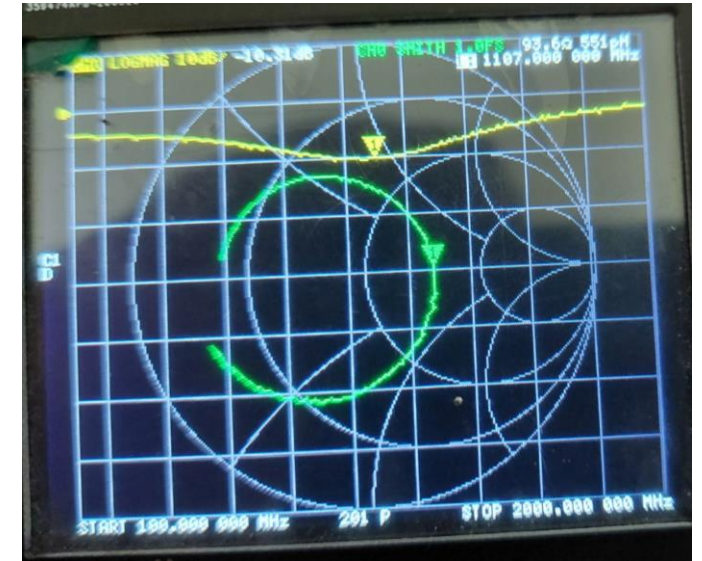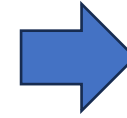- Without Insulator
 - $f_c = 1107$ MHz, 10.3 dB Return Loss
- With Insulator
 - $f_c = 1088$ MHz, 13 dB Return Loss



References

- Link to the QucsStudio software download
- qucsstudio.de/download/

Questions?

