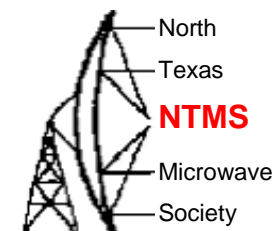



W5HN



# VHF drivers for Microwave local oscillators



Dave Robinson WW2R, G4FRE

# History


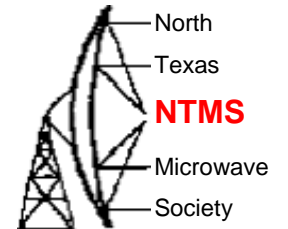


1. My DEMI xverter drifts on 1296 EME (but 10G one doesnt!). Need to fix especially for JT65c
2. Been looking at DMK type circuits for a while; unexpectedly poor phase noise
3. WA1ZMS had given presentation at Martlesham Round Table on 134GHz equipment which renewed my interest in solving the problem using Direct Frequency Synthesis



# Generic DFS

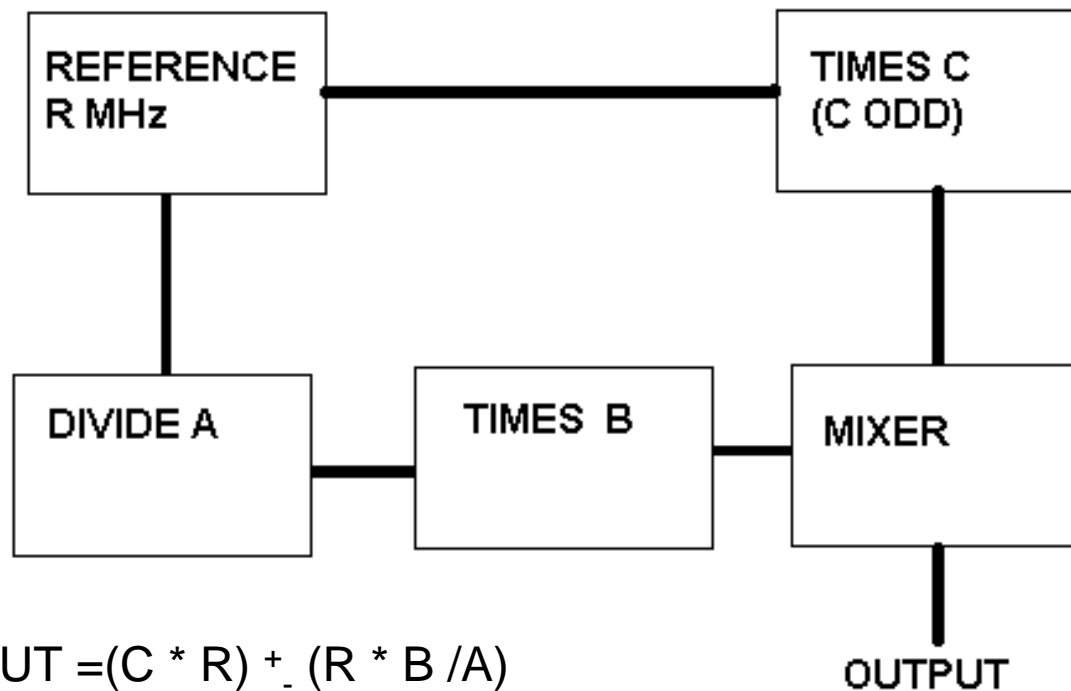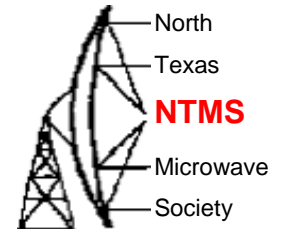


# WA1ZMS DFS

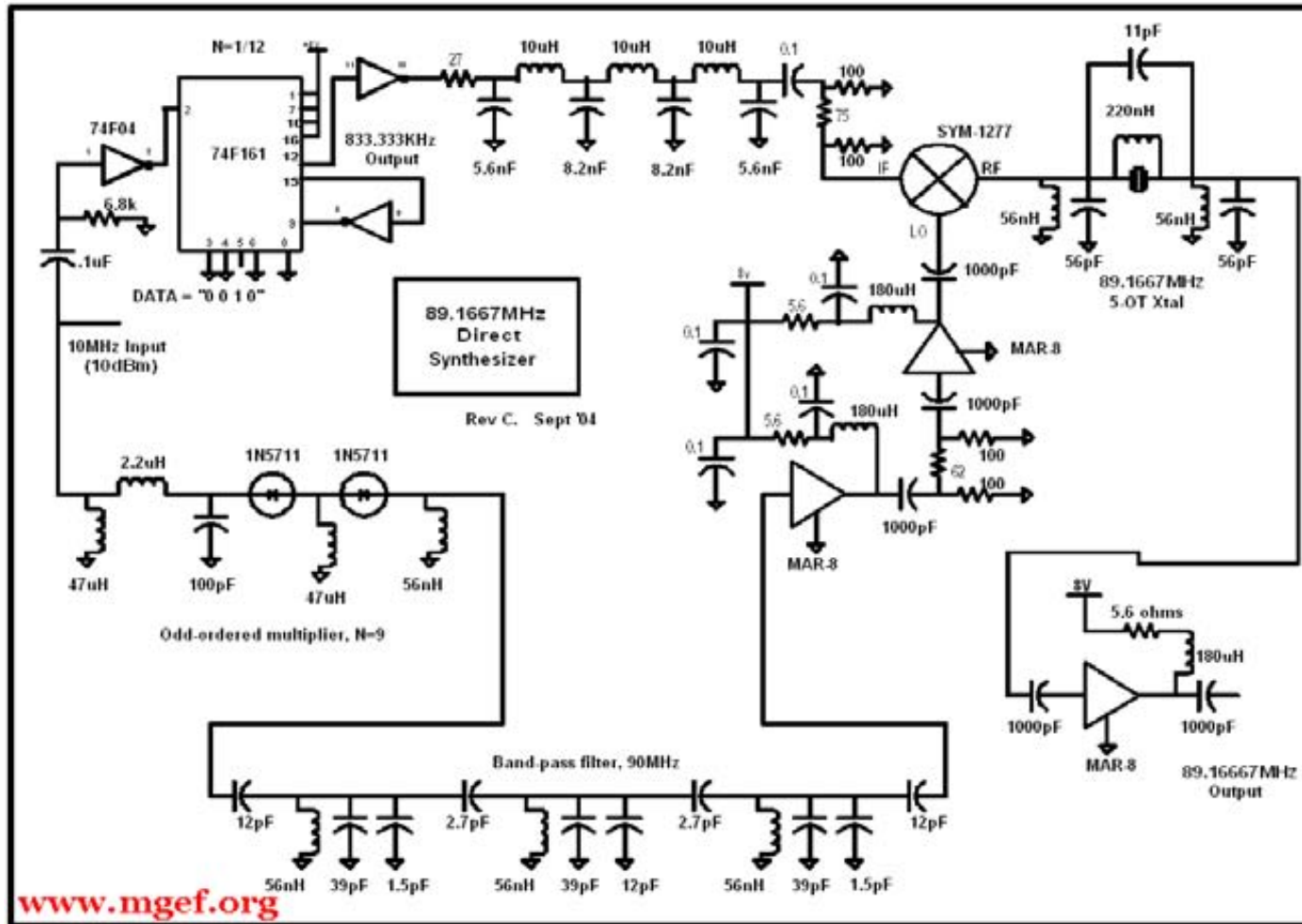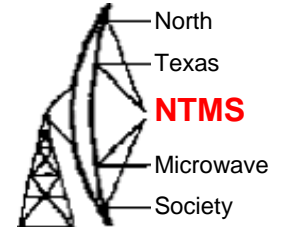



# DFS9096 Block Diagram

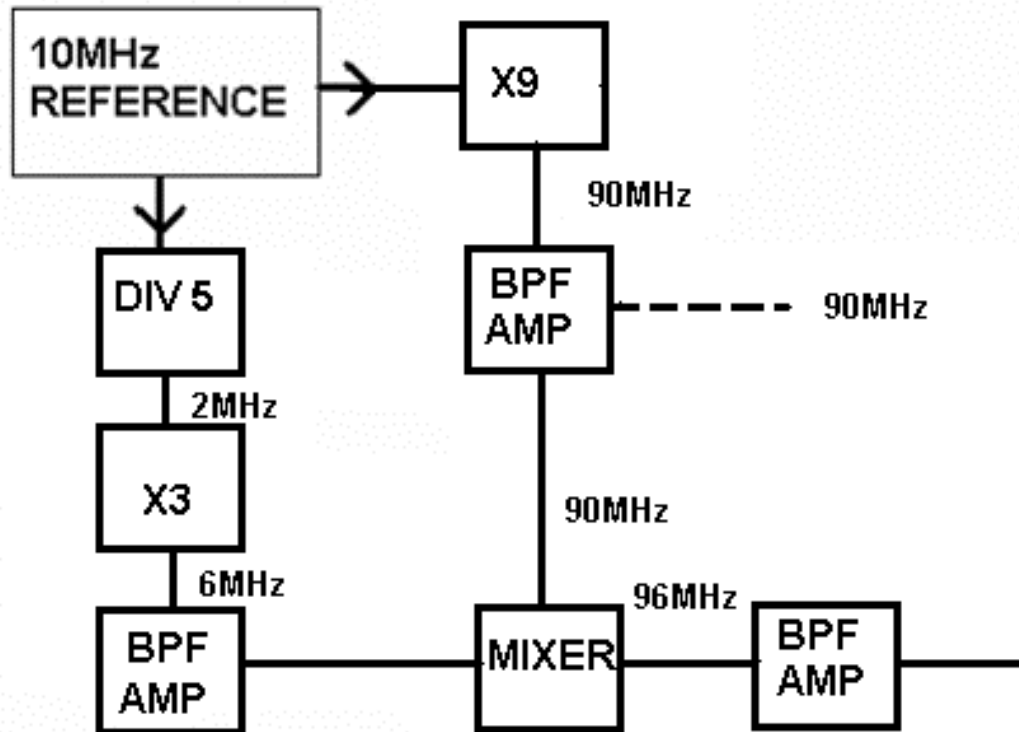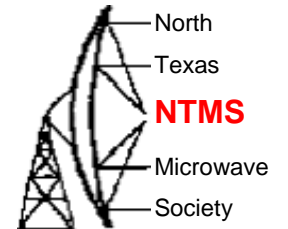

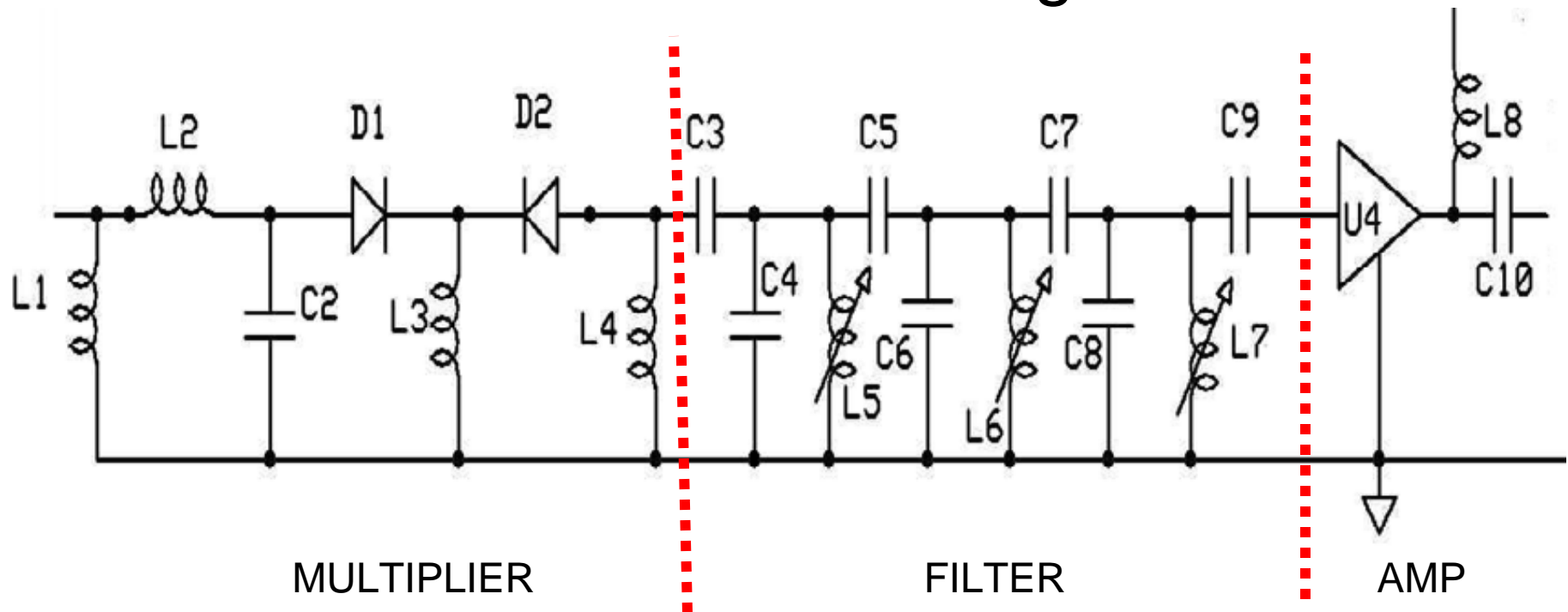First wanted to try 90MHz multiplier/filter circuit of WA1ZMS design





# Multiplier Prototype

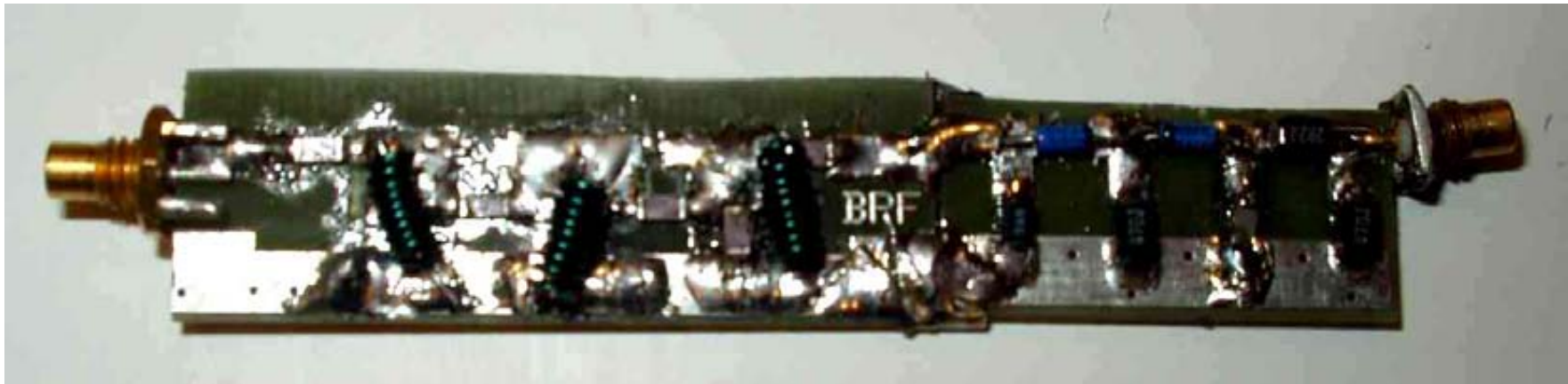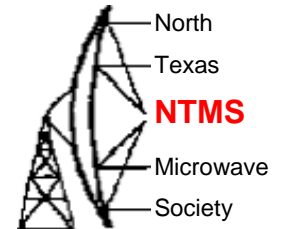

With mod amp 10dBm in at 10MHz gave 13.8dBm at 90MHz.

With crystal filter could be used as driver for 2304/144 Local oscillator



# 90MHz Mult/Filter/Amp output

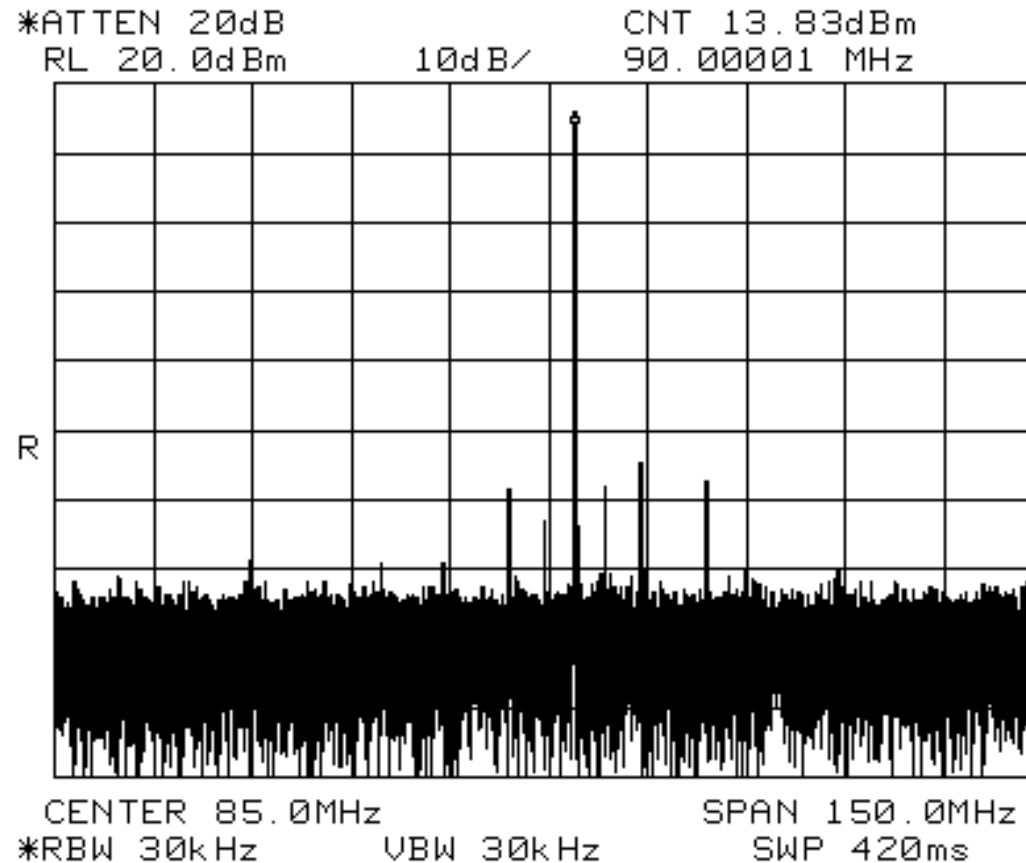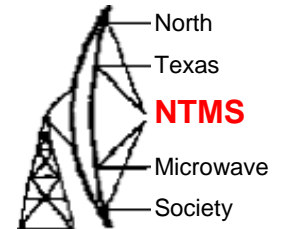

Note: Stray signals around 90MHz are VHF Broadcast stations (due to lack of screening)



# 74F161 Divider

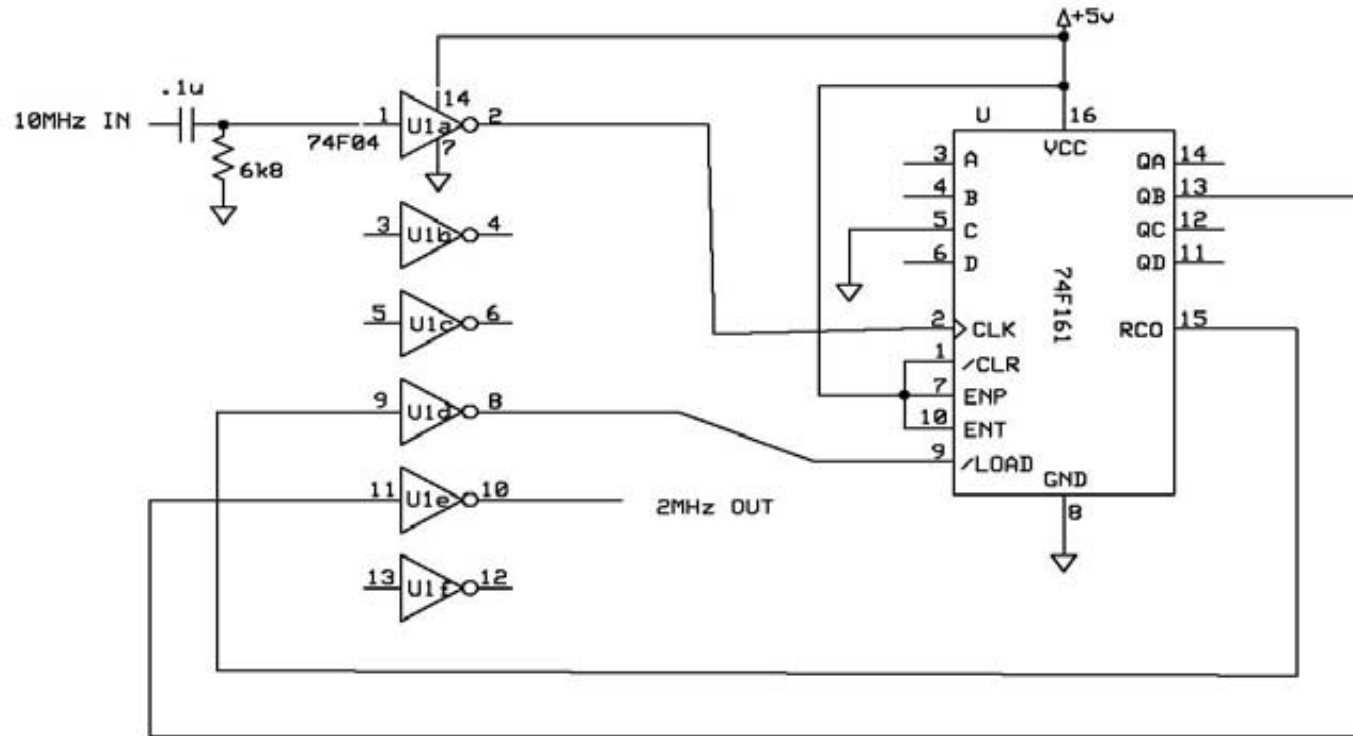
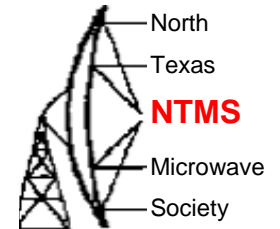


A, B, C, D pulled up internally, therefore preset (DCBA) = 1011 = 11.



74161 will count down from 16 to 11 = 5 before resetting.

Choose Q output that has closest to 50% duty cycle



# G4DDK DFS96

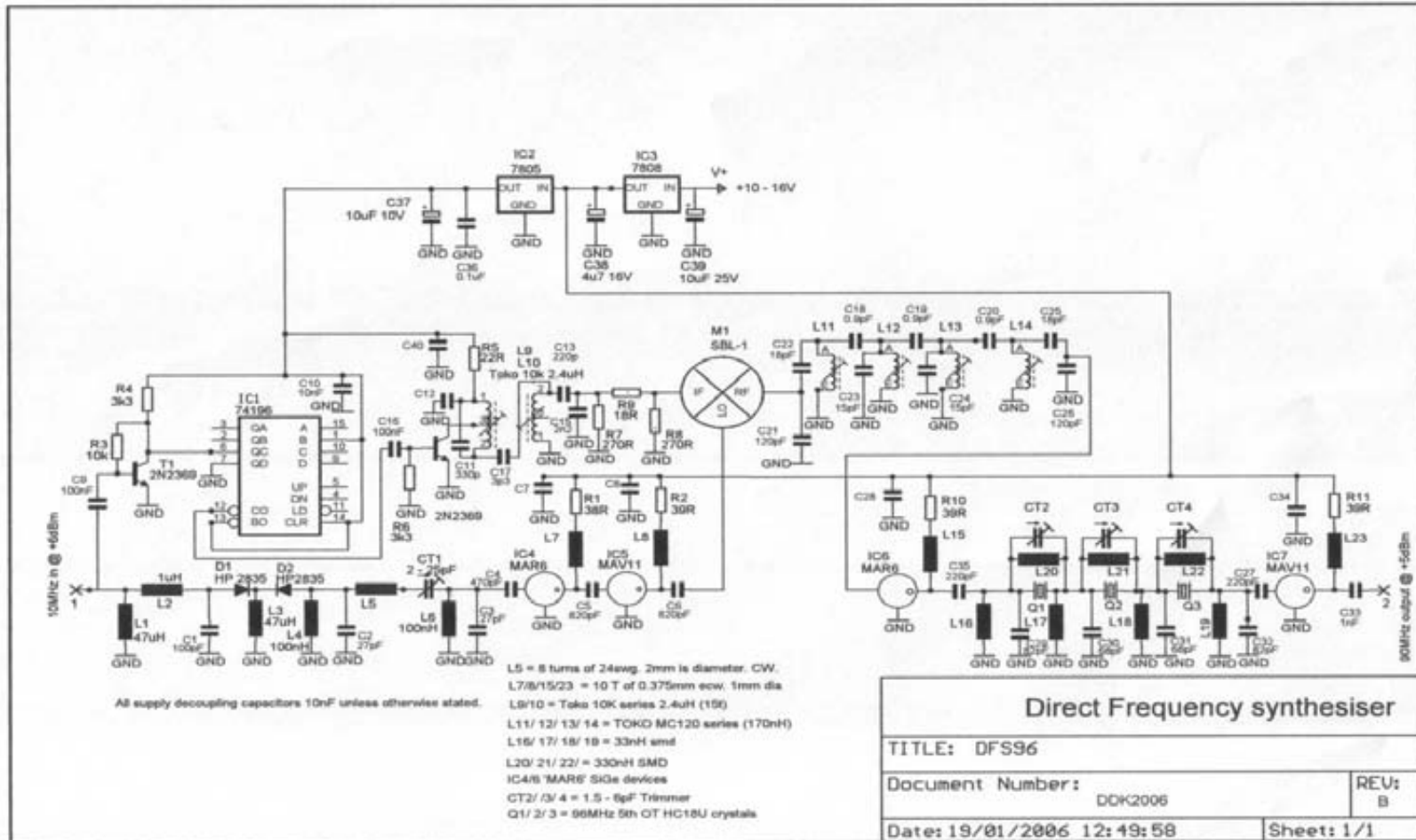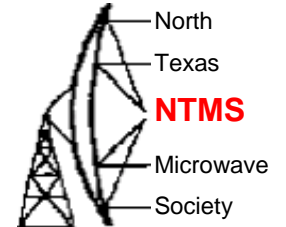

# G4DDK Unit

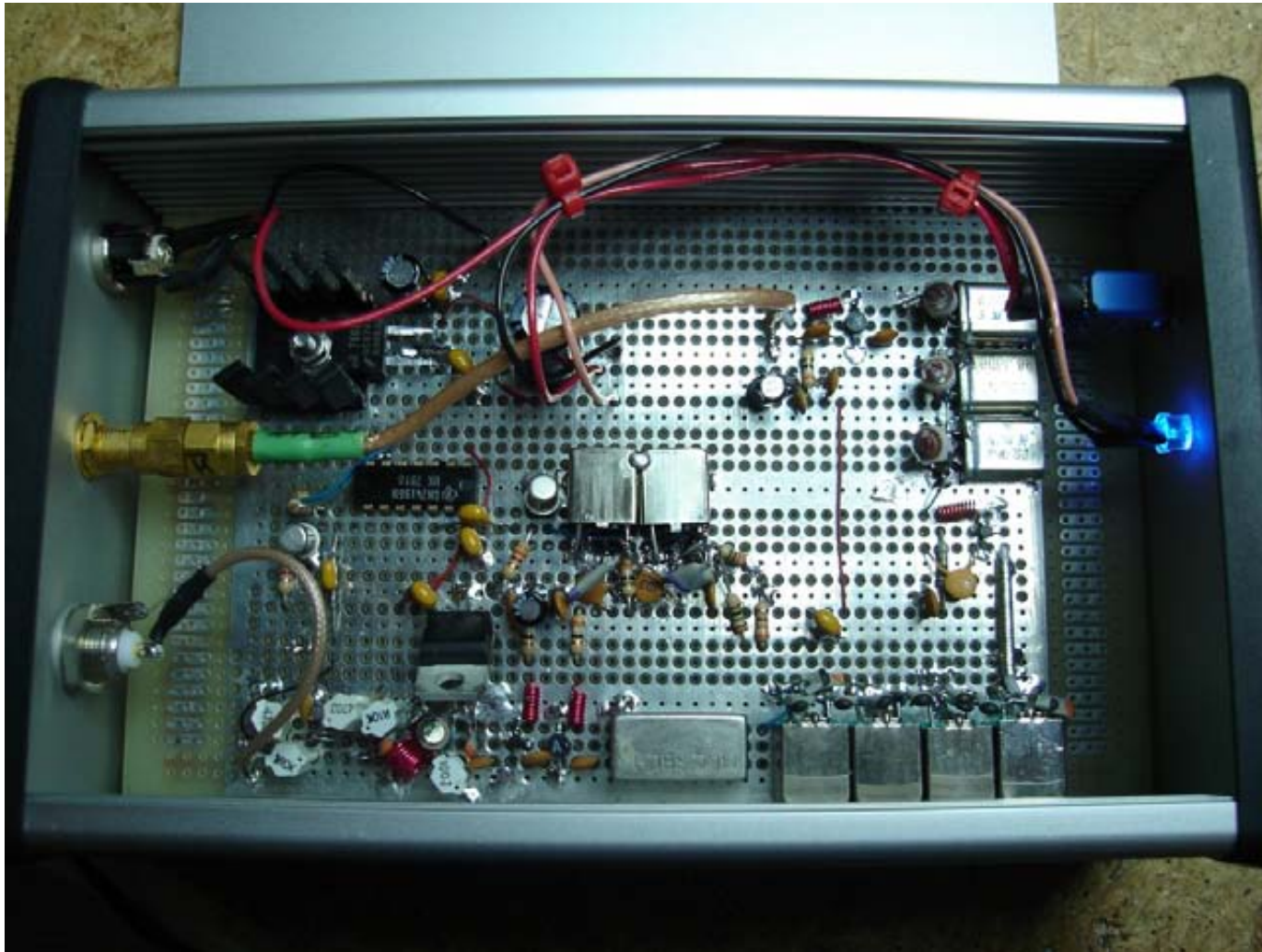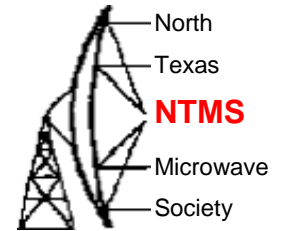


# WW2R DFS9096

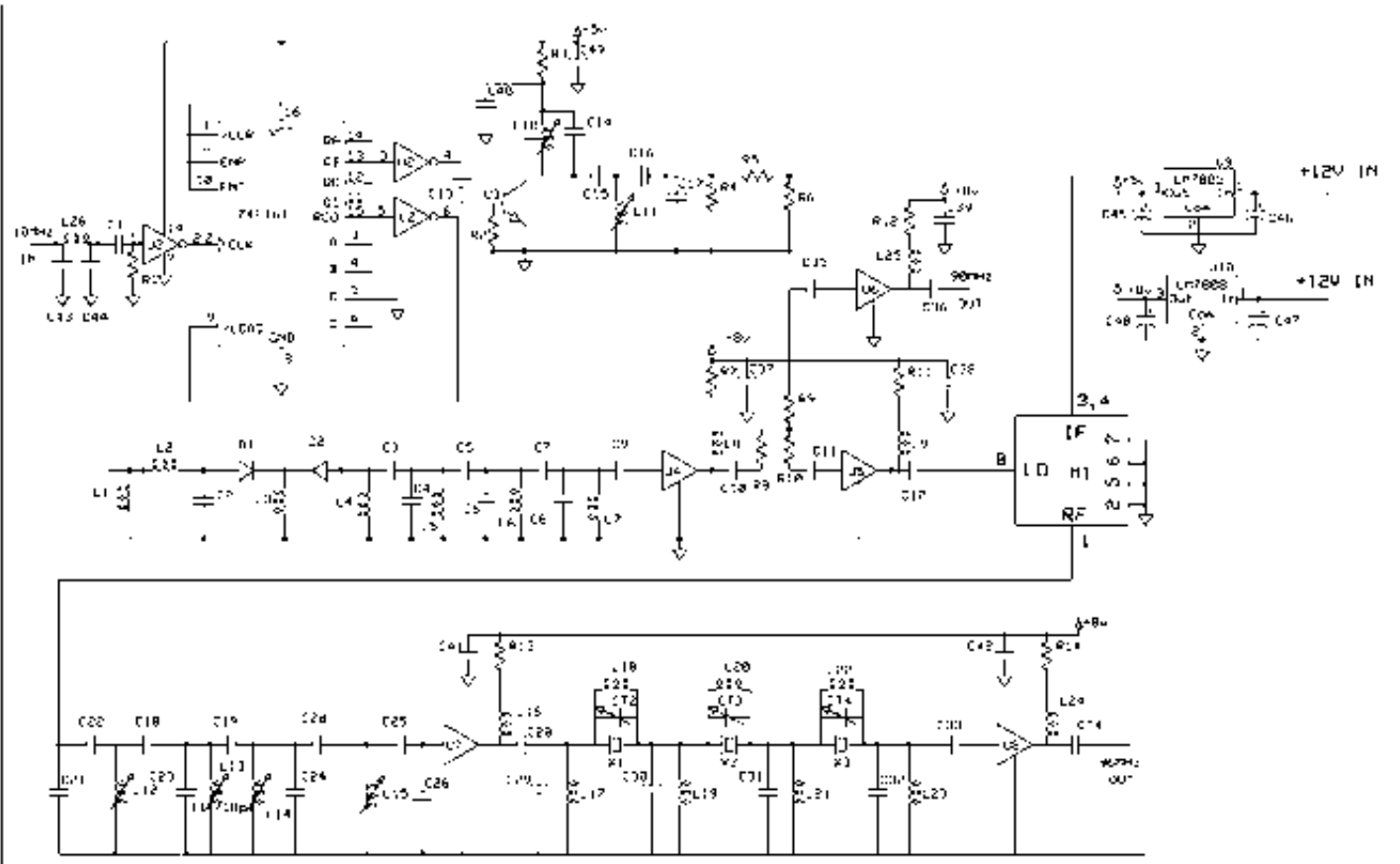
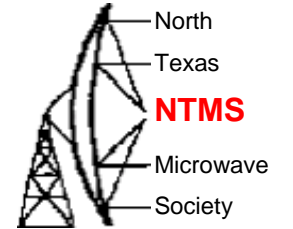


FRE Engineering  
DFS9096  
Dave Robinson      Rev 1.1  
1 May 2006


# DFS9096

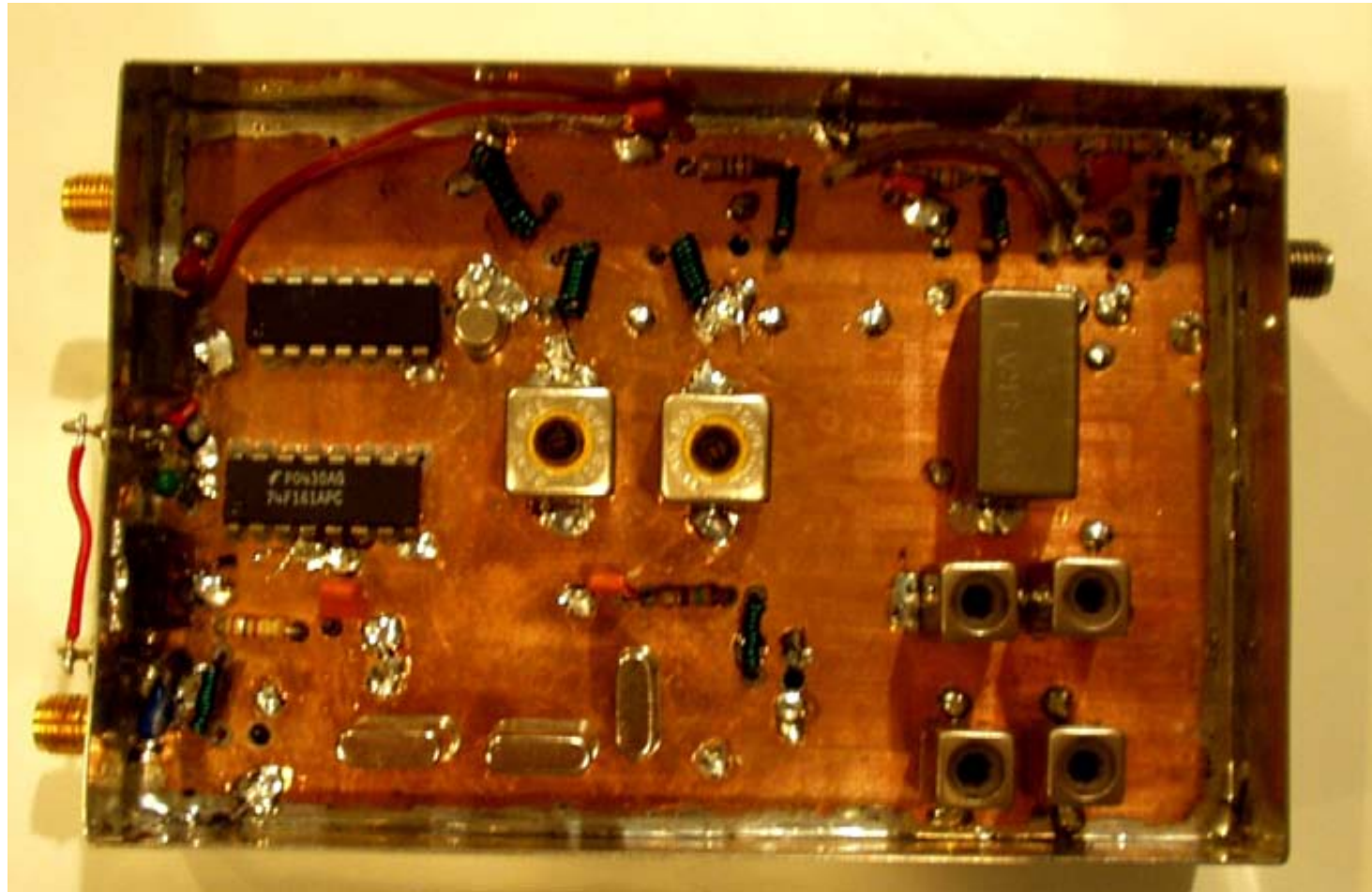


# 6MHz signal into mixer

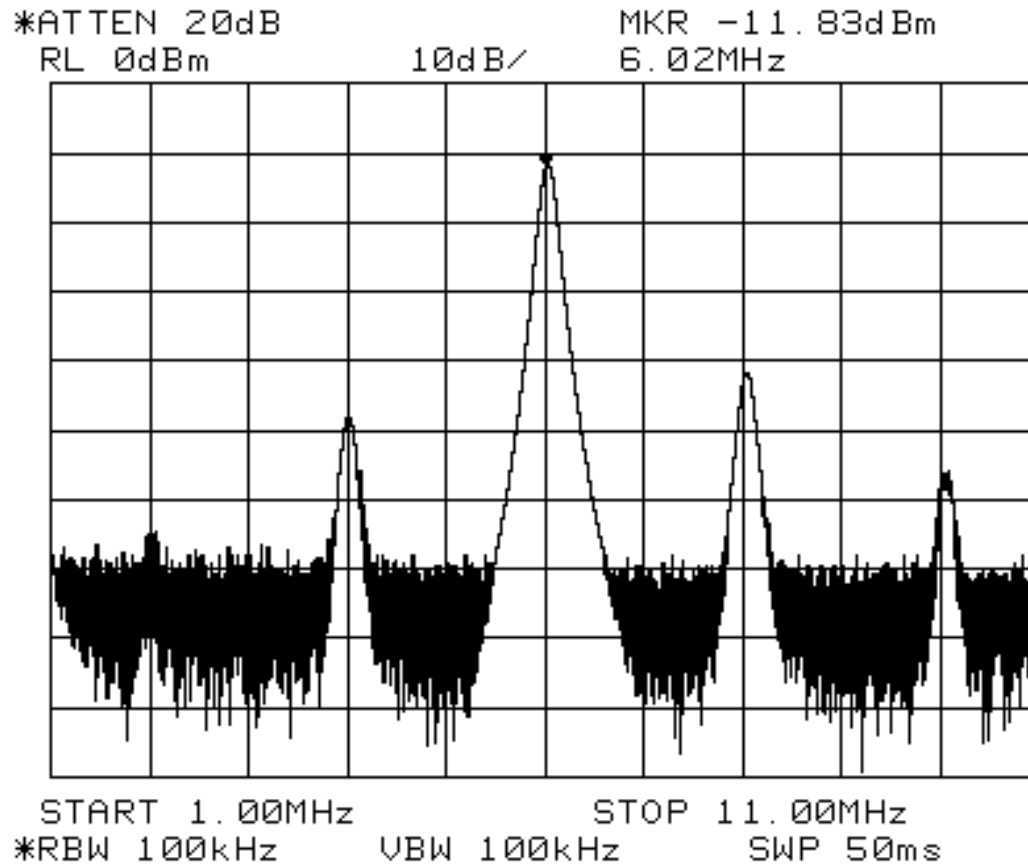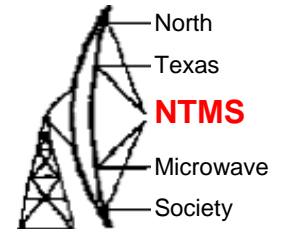

# 96MHz output from mixer


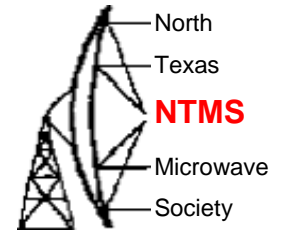


\*ATTEN 20dB  
RL 10.0dBm 10dB/ CNT -2.33dBm  
96.00 MHz

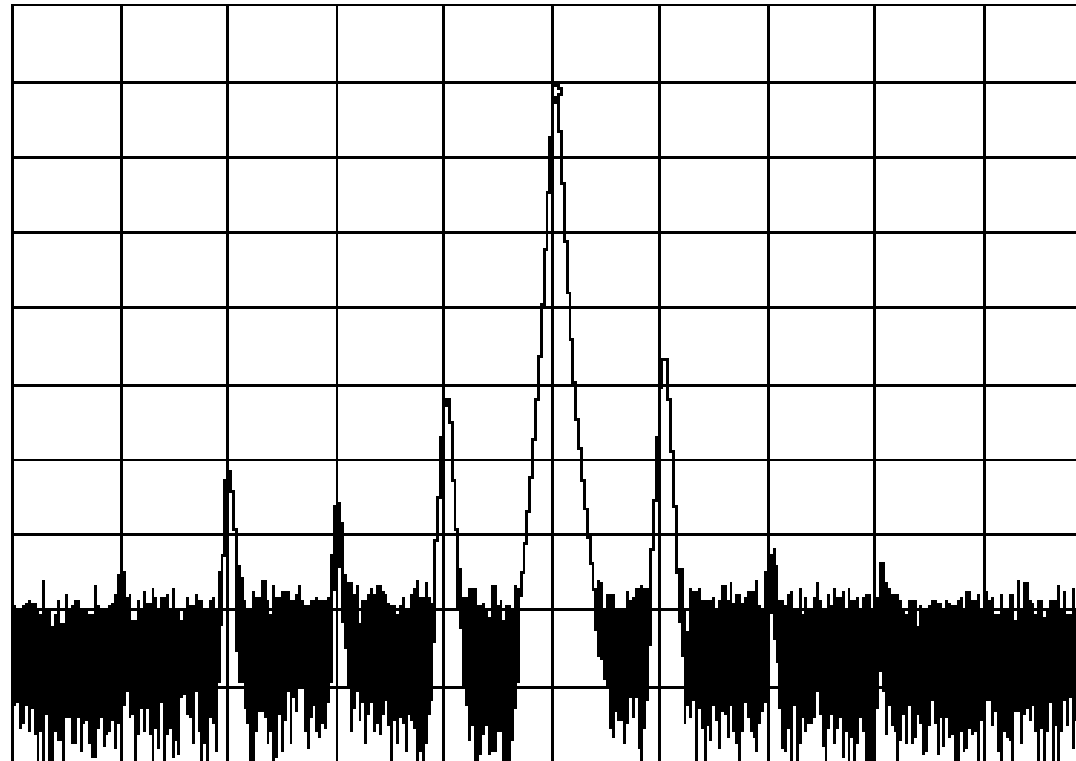

CENTER 96.00MHz SPAN 20.00MHz  
\*RBW 100kHz VBW 100kHz SWP 50ms


# 96MHz Crystal Filtering

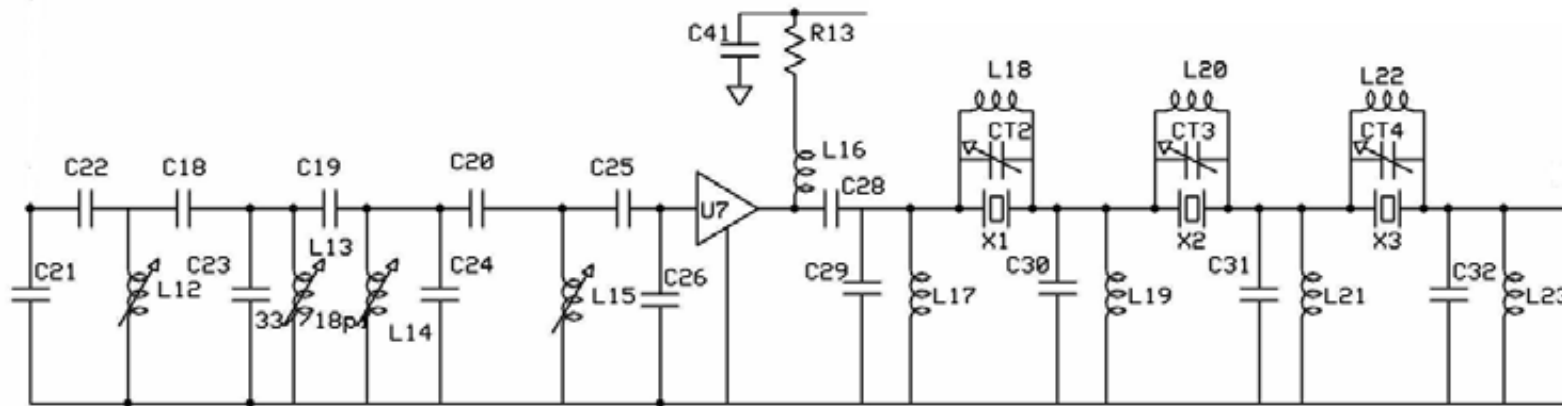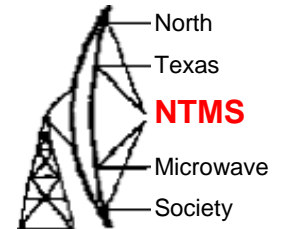

Crystal filter improves medium and far out phase noise as well as broader spectrum




# 96MHz O/P

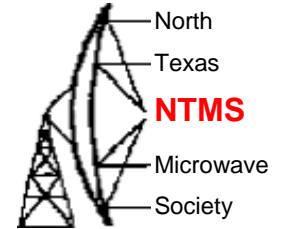

\*ATTEN 20dB  
RL 10.0dBm

10dB/

CNT 9.33dBm  
96.00001 MHz

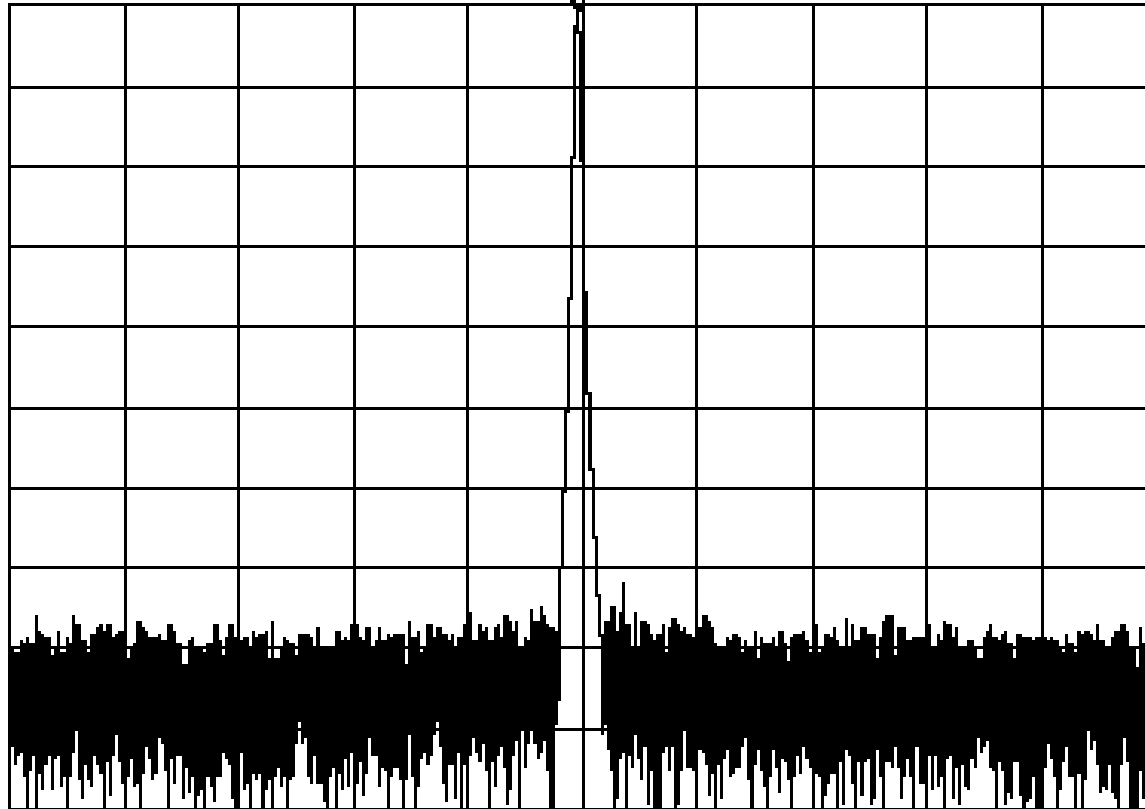


CENTER 96.00MHz  
\*RBW 100kHz

VBW 100kHz



SPAN 50.00MHz  
SWP 50ms

# Summary

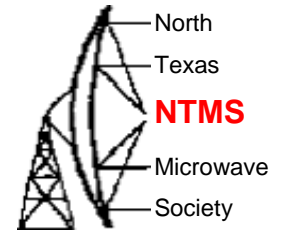


- Technique good for some frequencies but impossible for others with 10MHz reference
- $\text{Output} = (C * R) \pm (R * B / A)$
- Easy Freqs to achieve: 92, 98, 116, 101MHz
- Harder Freqs to achieve: 106.5, 101.5, 94.75

# Other Possibilities

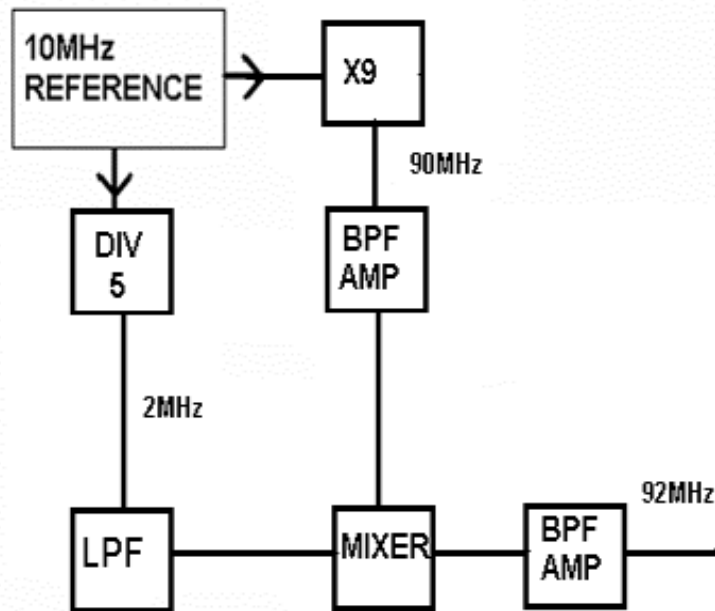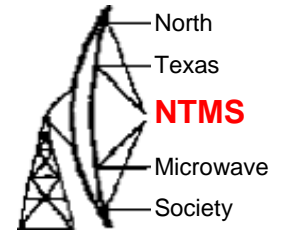


3456/144MHz

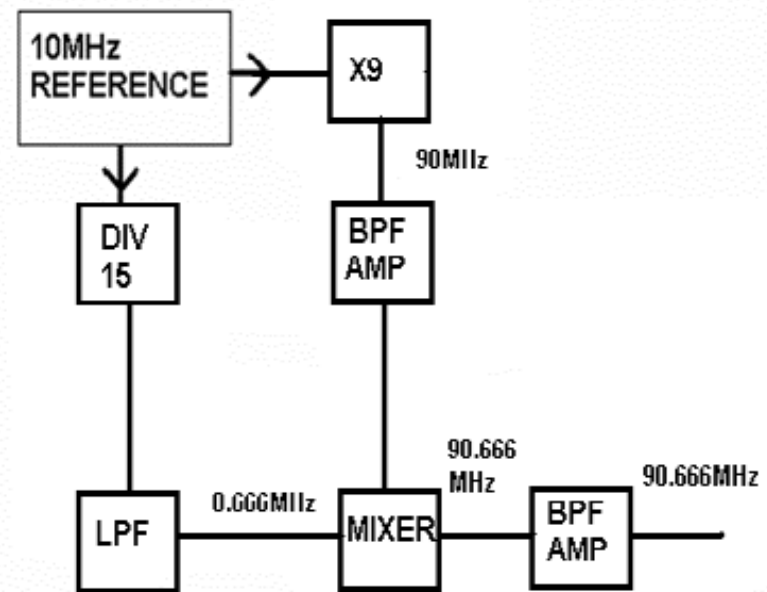

2320/144MHz

# References

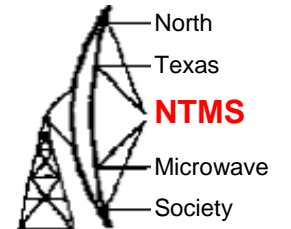

1. <http://www.wenzel.com/documents/2diomult.html>
2. [http://mgef.org/zms\\_134\\_VUCC.htm](http://mgef.org/zms_134_VUCC.htm)