
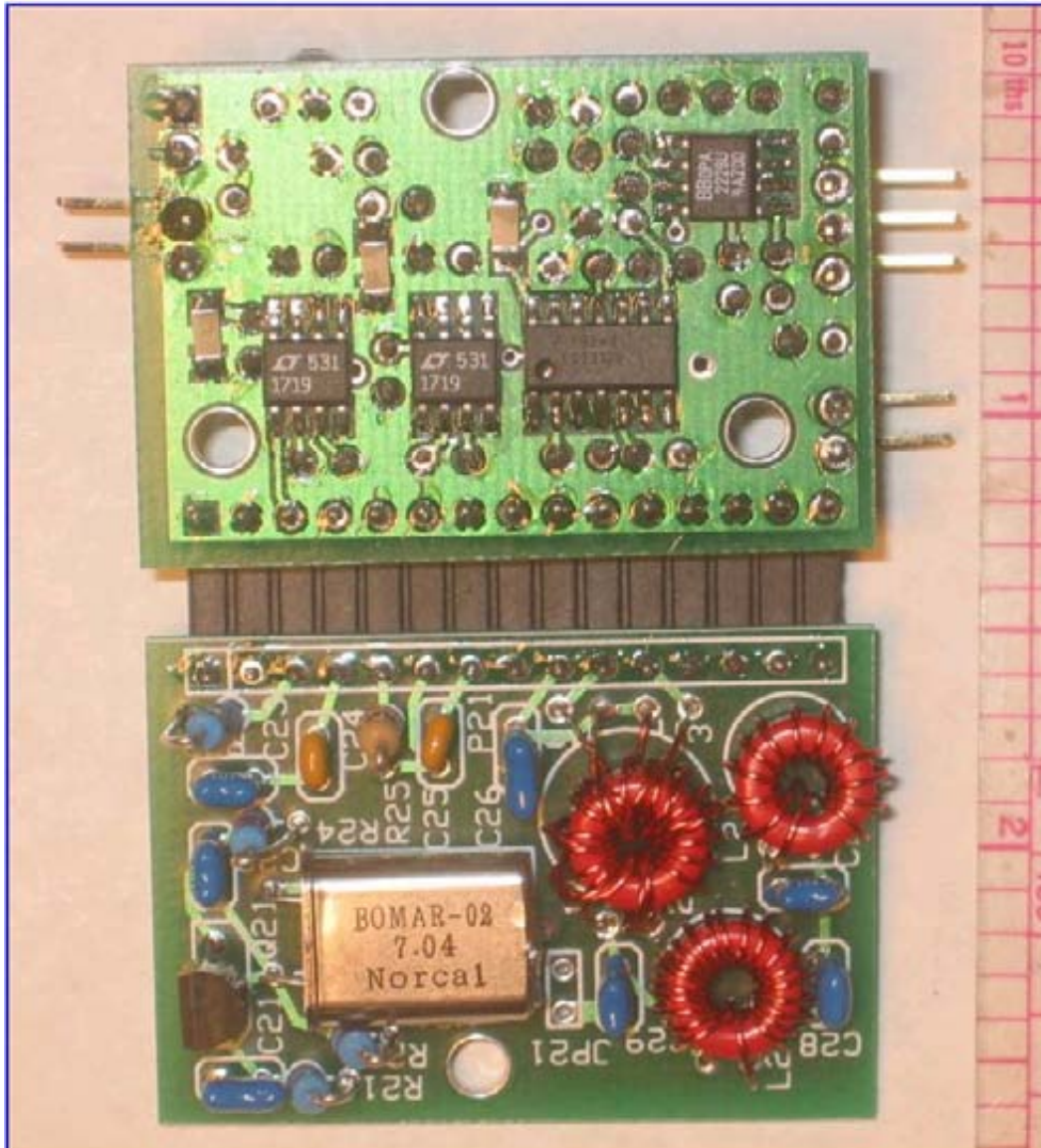


# Using the Soft Rock 5 as a Microwave IF Spectrum Analyzer

By  
Al Ward  
W5LUA  
February 4, 2006
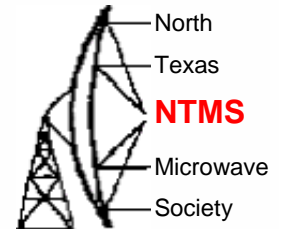
# Soft Rock 5 Designed by Tony Parks KB9YIG



**2 Board Approach**  
**Top board has the**  
**LNAs, Comparators**  
**and QSD**


**Bottom board has**  
**the frequency**  
**sensitive**  
**components – LO ,**  
**band pass filter and**  
**phase shift network**

**Only**  
**\$26.50 !**

<http://ewjt.com/kd5tfd/sdr1k-notebook/sr40/v5-1stlook/index.html>

<http://amqrp.org/kits/softrock40/version5.html>

<http://www.hamsdr.com/Home.aspx>

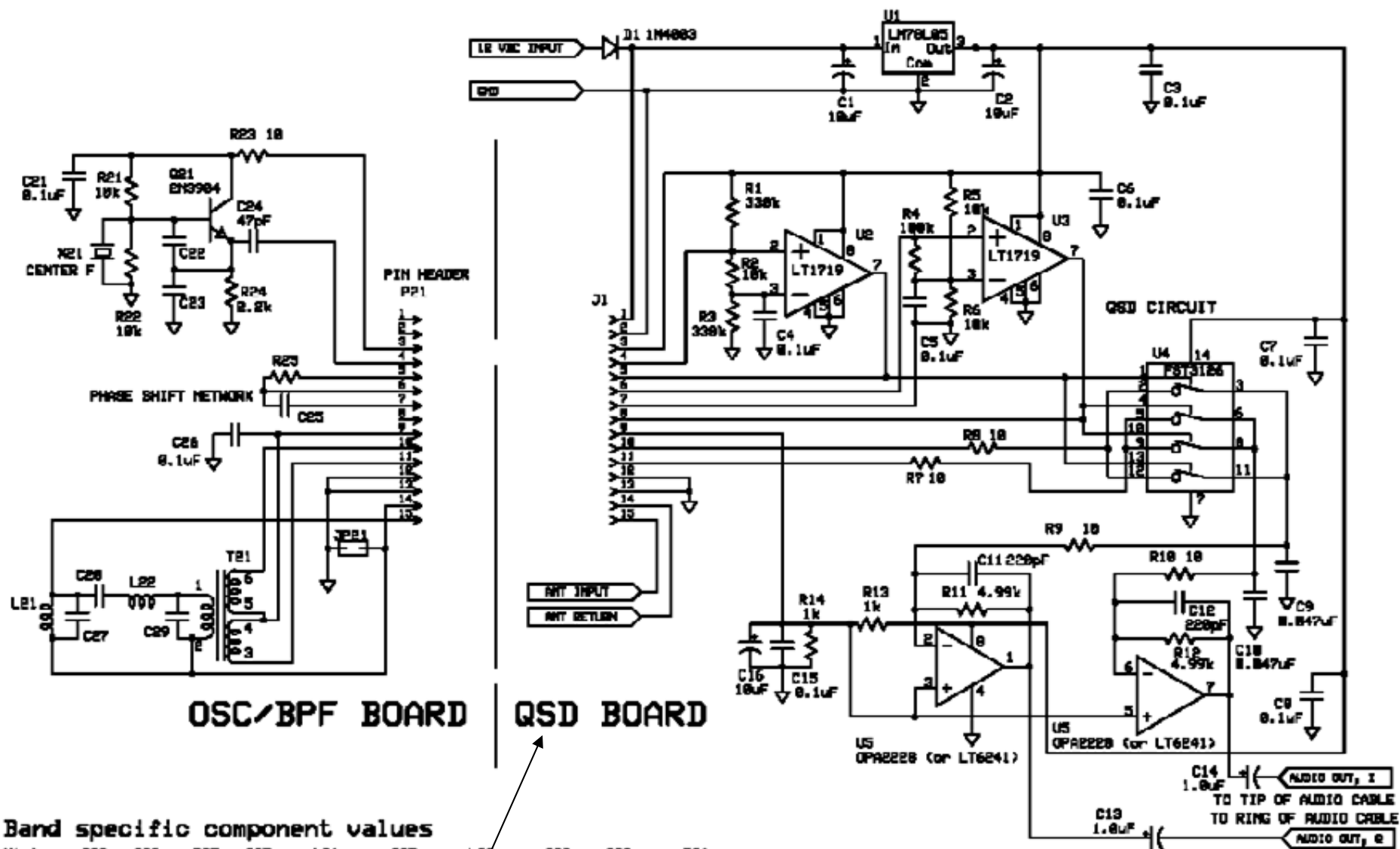

Quadrature Sampling Detector

**FLEX RADIO FRIENDS**

**SoftRock\_v5.0**



Tony K29YIC

Rev 5.0

11/25/2005


Page 1 of 1

# Block Diagram of the Soft Rock 5

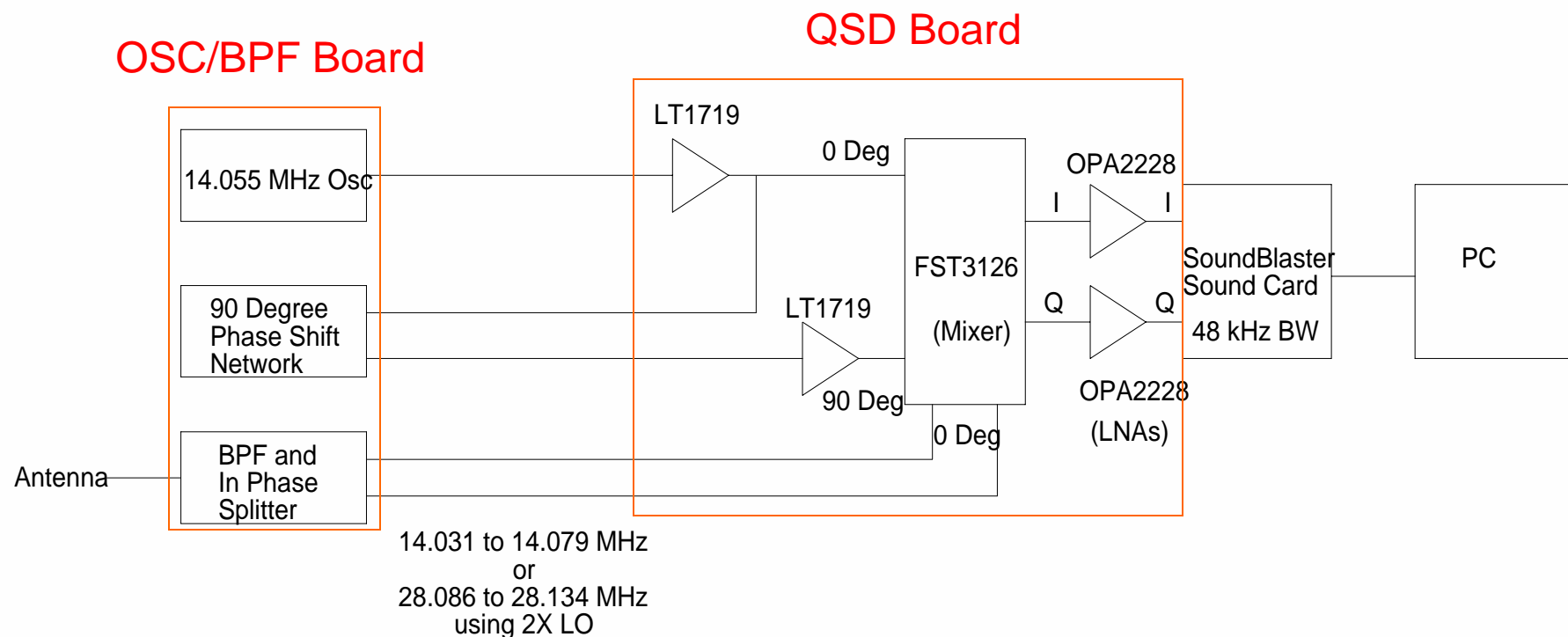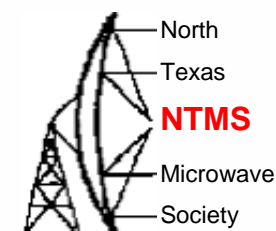

I found that the basic SoftRock 5 with a little MMIC gain in front of it will also operate as-is at 10 M once the input BPF is bypassed. The center frequency on 10M is now 28.110 MHz. On the first unit I built, I coupled in 10M RF at the junction of L22 and C29. For the second unit, I just built a 10 M BPF per the following table. Both worked well but still needed some more MMIC gain between my xvtrs and Soft Rock 5 to help set SoftRock 5 noise level.
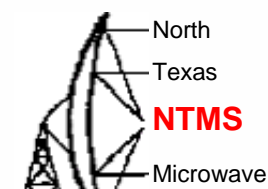
# SoftRock v5.0 Band Specific Component Values



Band (MHz)	C22 (pF)	C23 (pF)	C24 (pF)	C25 (pF)	C27 (pF)	C28 (pF)	C29 (pF)	L21 (uH)	L21 wind/core	L22 (uH)	L22 wind/core	T21 core	T21 primary	T21 secondaries
1.800	470	470	220	620	6800	470	6800	1.1	16T #30 on T30-2	14	57T #30 on T30-2	T30-2	16T #30	7T/7T #30 bifilar
3.500	470	470	220	330	1000	360	1000	1.4	18T #30 on T30-2	3.9	30T #30 on T30-2	T30-2	18T #30	8T/8T #30 bifilar
7.000	270	270	47	150	470	180	470	0.73	13T #26 on T30-2	1.9	21T #26 on T30-2	T30-2	13T #26	6T/6T #26 bifilar
10.100	270	270	47	100	330	120	330	0.52	11T #26 on T30-2	1.2	17T #26 on T30-2	T30-2	11T #26	5T/5T #26 bifilar
14.000	180	180	47	47	270	100	270	0.36	10T #26 on T30-6	0.92	16T #26 on T30-6	T30-6	10T #26	5T/5T #26 bifilar
18.068	150	150	47	47	180	69	180	0.36	10T #26 on T30-6	0.71	14T #26 on T30-6	T30-6	10T #26	5T/5T #26 bifilar
21.000	150	150	47	47	150	62	150	0.29	9T #26 on T30-6	0.61	13T #26 on T30-6	T30-6	9T #26	4T/4T #26 bifilar
24.890	120	120	47	47	120	47	120	0.24	8T #26 on T30-6	0.52	12T #26 on T30-6	T30-6	8T #26	4T/4T #26 bifilar
28.000	100	100	47	33	120	47	120	0.18	7T #26 on T30-6	0.44	11T #26 on T30-6	T30-6	7T #26	3T/3T #26 bifilar

From SoftRock 5 Yahoo User's Group


Band (MHz)	R24 (k)	C22 (pF)	C23 (pF)	C24 (pF)	C25 (pF)	C27 (pF)	C28 (pF)	C29 (pF)	L21 (uH)	L21 wind/core	L22 (uH)	L22 wind/core	T21 core	T21 primary	T21 secondaries
1.800	3.3	470	470	220	680	6800	470	6800	1.1	16T #30 on T30-2	14	57T #30 on T30-2	T30-2	16T #30	7T/7T #30 bifilar
3.500	2.2	470	470	220	330	1000	360	1000	1.4	18T #30 on T30-2	3.9	30T #30 on T30-2	T30-2	18T #30	8T/8T #30 bifilar
7.000	2.2	270	270	47	150	470	180	470	0.73	13T #26 on T30-2	1.9	21T #26 on T30-2	T30-2	13T #26	6T/6T #26 bifilar
10.100	2.2	270	270	47	100	330	150	330	0.52	11T #26 on T30-2	1.2	17T #26 on T30-2	T30-2	11T #26	5T/5T #26 bifilar
14.000	2.2	180	180	47	47	270	100	270	0.36	10T #26 on T30-6	0.92	16T #26 on T30-6	T30-6	10T #26	5T/5T #26 bifilar
18.068-21.000	2.2	150	150	47	47	180	100	180	0.36	10T #26 on T30-6	0.71	14T #26 on T30-6	T30-6	10T #26	5T/5T #26 bifilar
24.890-28.000	2.2	100	100	47	47	120	56	120	0.24	8T #26 on T30-6	0.52	12T #26 on T30-6	T30-6	8T #26	4T/4T #26 bifilar

From Tony Parks KB9YIG



<http://www.amqrp.org/kits/dds60/index.html>

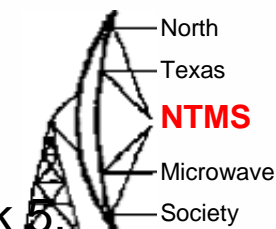This should be a good way to broaden the receive capability of the Soft Rock 5.



## DDS-60 Kit

A 0-60 MHz coverage VFO with built-in amplifier and variable output level from 0 to 4V p-p, manually adjusted with a trimpot or software controlled with a digipot.

[About the AmQRP Club](#)  
[Frequently Asked Questions](#)  
[Site](#)  
[Projects](#)  
[QRP Forum](#)  
[Contesting](#)  
[References](#)  
[Links](#)



[Top View \(click for larger image\)](#)



[Bottom View \(click for larger image\)](#)

[Overview](#) | [Schematic](#) | [Ordering](#) | [Availability](#) | [Ways to Use](#) |

[Assembly & User Manual](#) | [Quick Assy Guide](#) | [Builder's Notes](#) |

Article: ["Working with Surface Mount Technology \(SMT\) Parts"](#)

Tech Topic: [DDS-60 Spectral Purity Study](#)

Kit Status: In stock.

### Overview


Some three years ago we introduced the original **DDS Daughtercard** ([www.amqrp.org/dds](http://www.amqrp.org/dds)) to the QRP community, providing a low cost and modular way to add a precisely-adjustable 0-30 MHz signal generator to one's project. All you had to do was add an AD9850 DDS chip (available as a free sample from the good people at Analog Devices) and +12V, and then any number of popular microcontrollers could control the DDS Daughtercard to have it serve as a rock-solid VFO. Over 1,000 of these little cards were sold!

Well, there is still a demand for this inexpensive little kit and an ever-growing list of uses for it so we updated the basic design and are now ready to provide the *new and improved* **DDS-60 daughtercard**. This self-contained functional module generates a good-quality RF signal from **1-60 MHz** by using a small pc board to contain just the bare DDS essentials – an Analog Devices AD9851 DDS chip, a clock oscillator, a 5th-order elliptic filter and an adjustable-level RF amplifier. Additionally, an onboard 5V regulator is provided so you only need provide a battery or power supply ranging anywhere from 8-16V DC. The three digital control lines, the power supply, and the output signal are all available on a pin header at the board edge, and the DDS-60 is pin-compatible with the original DDS Daughtercard. The [schematic](#) is shown below on this page.

The 8-position pin header at the board edge serves to allow DDS-60 to be plugged into and used in any project you might have on your bench, regardless of which microcontroller is employed. Just provide a single strip socket (e.g., a 16-pin IC socket split lengthwise) on the project board and plug in the DDS Daughtercard. Heck, you don't even need a dedicated microcontroller – use a cable connected to the parallel printer port of your PC and use public domain PC software to control the DDS board! See the [Ways to Use](#) section for a number of custom solutions for you to easily control your DDS-60 daughtercard.

Once your controller-of-choice serially loads the 40-bit control word into the DDS, the raw waveform is presented to an elliptic filter that removes unwanted high-end frequency components, resulting in a signal of sufficient quality to serve as a local oscillator for a transceiver. We regularly see great signal quality, with harmonic content of -40 dB.


# DDS-60 using the AD9851

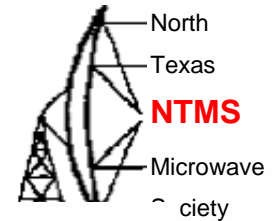

## Specifications



- Power requirements: 8-16V DC at 130 ma (typical).
- RF Output – fully adjustable to +16 dBm, or about 4V p-p.
- Output signal not affected by varying +V supply voltage – great for battery operation. |
- Near-constant output level from 1-60 MHz.
- Good signal purity – harmonics down approximately 40 dB from the fundamental.
- Pin-compatible with the original DDS Daughtercard module
- Only few changes needed in existing AD9850 software drivers

## Schematic

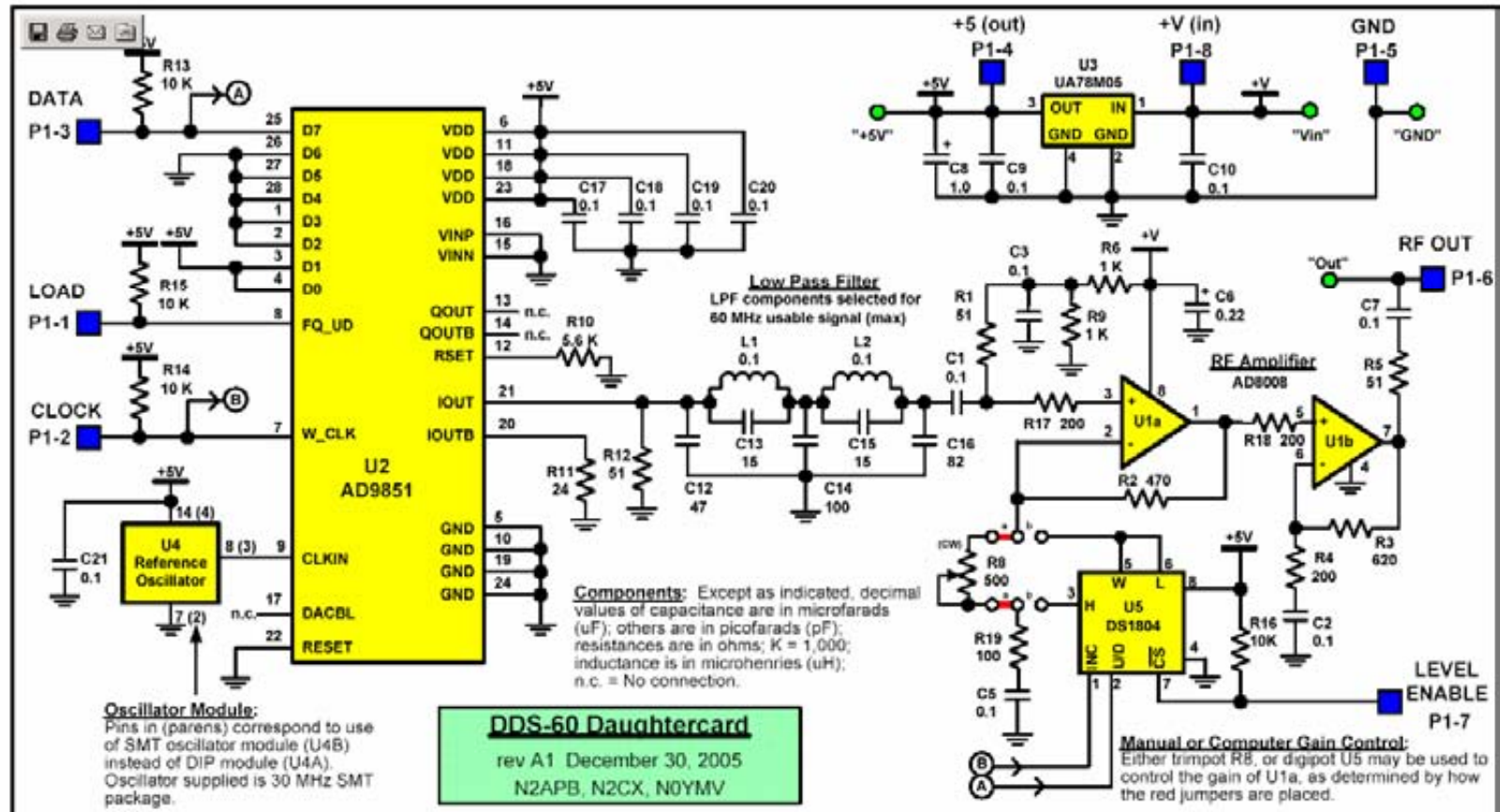



# NM5M On 1296.100 MHz CW

Spanning 1296.086 to 1296.134 MHz

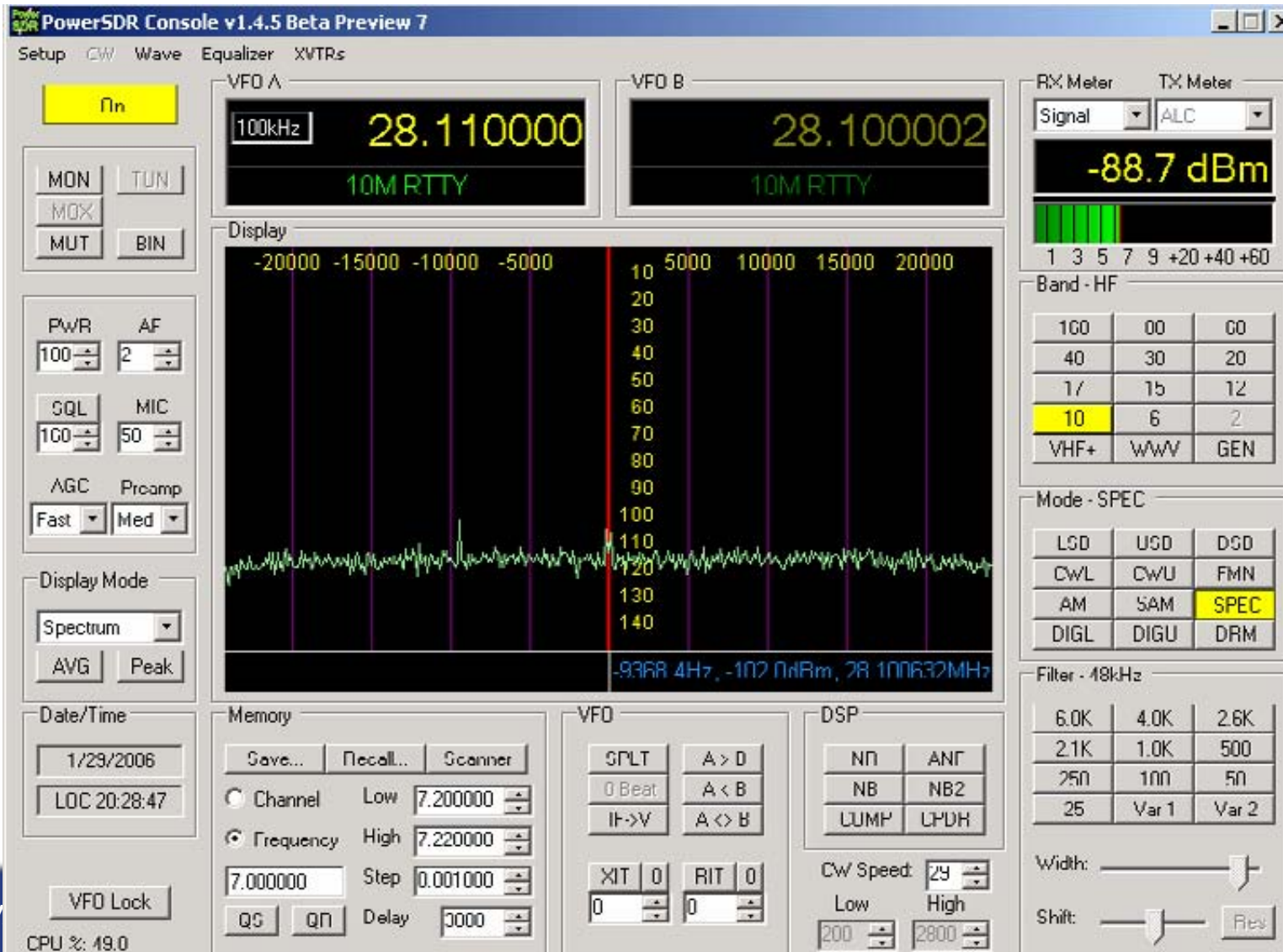
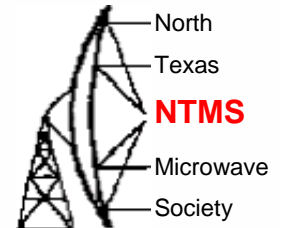






# NM5M On 1296.100 MHz CW

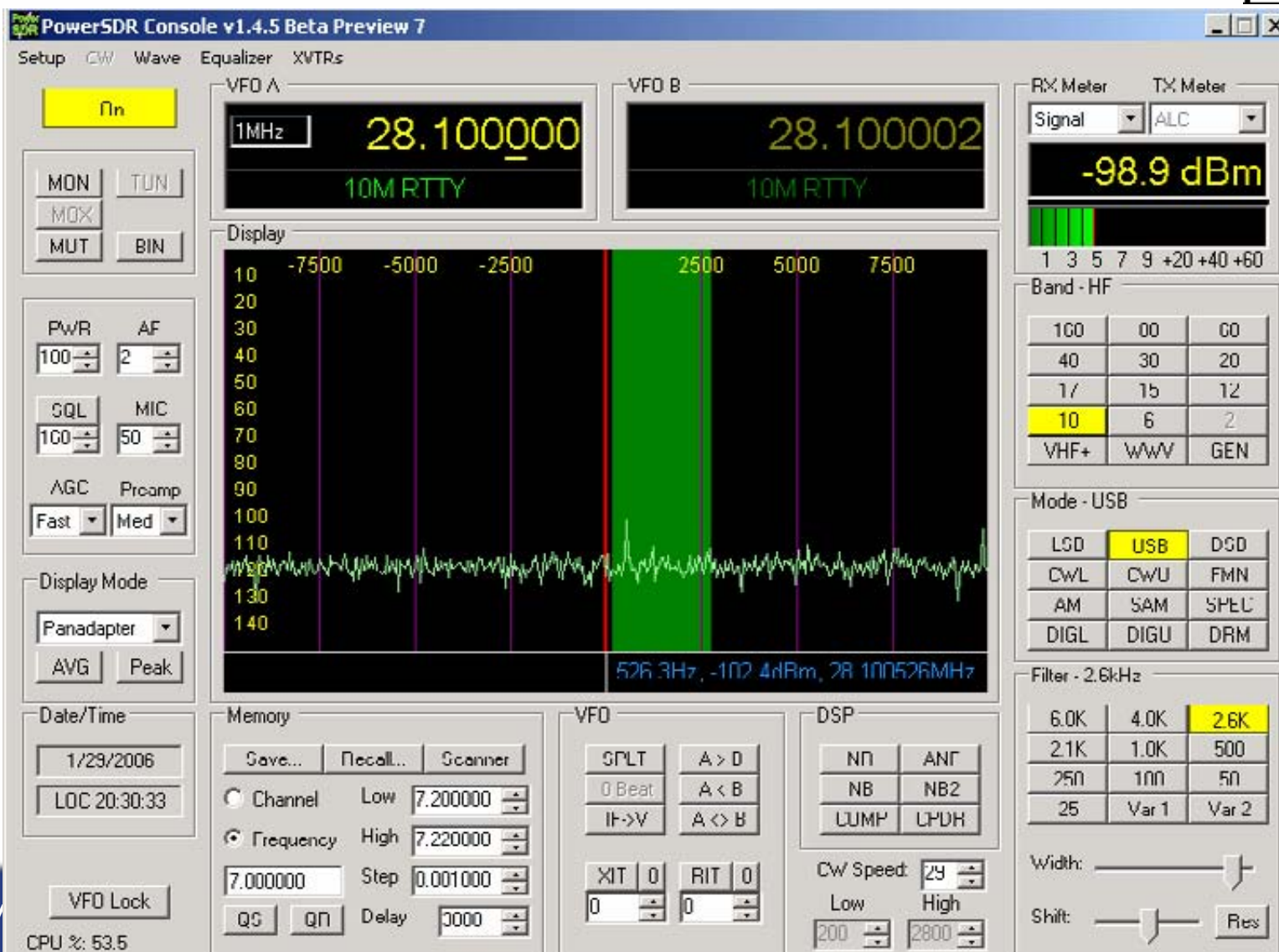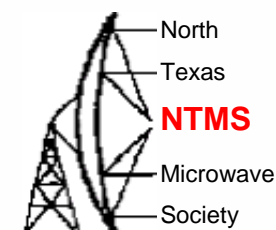

# KA5BOU on 1296.100 MHz USB

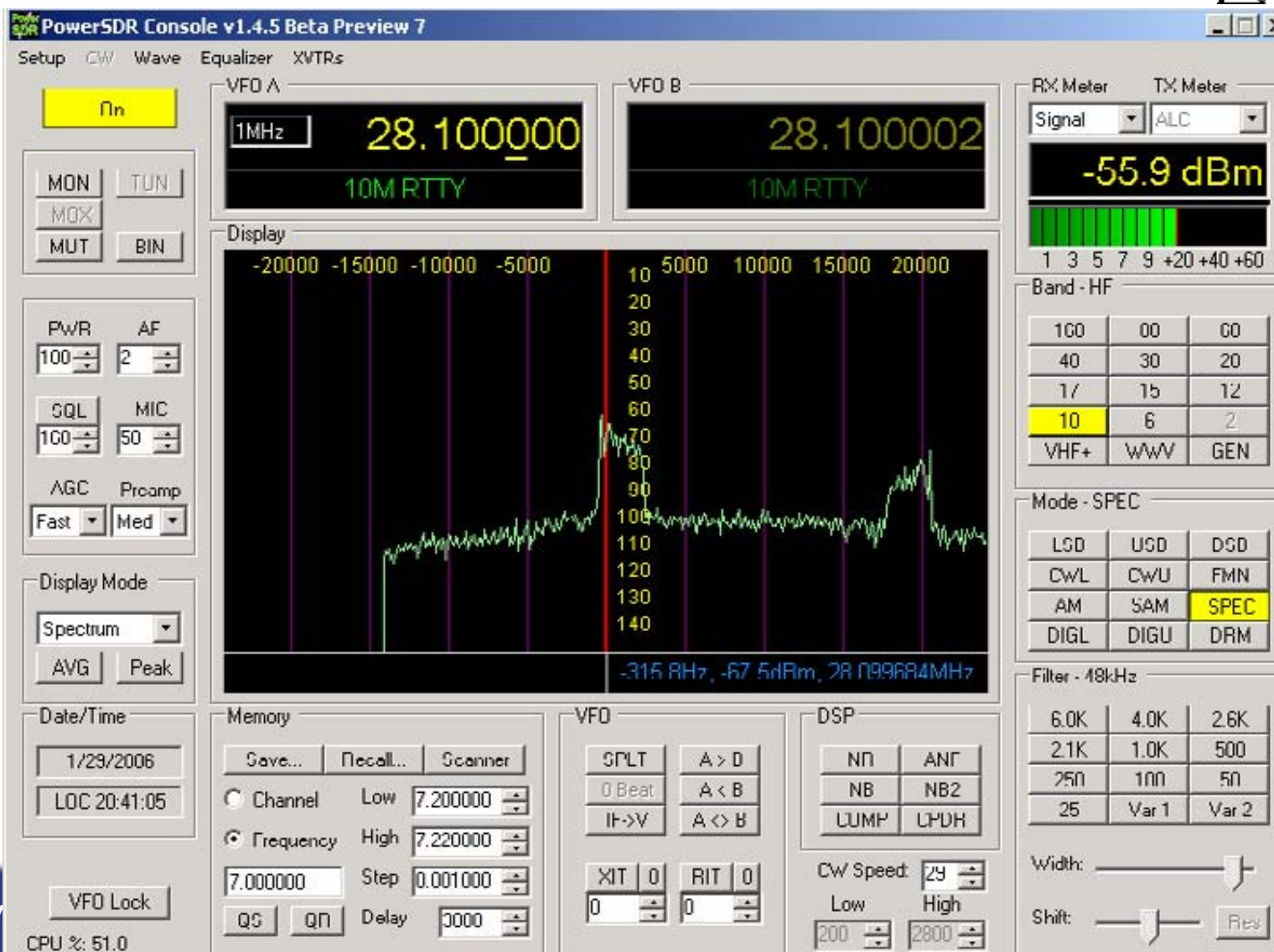
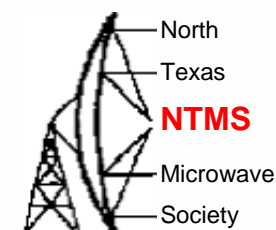


# KA5BOU on 1296.100 MHz USB

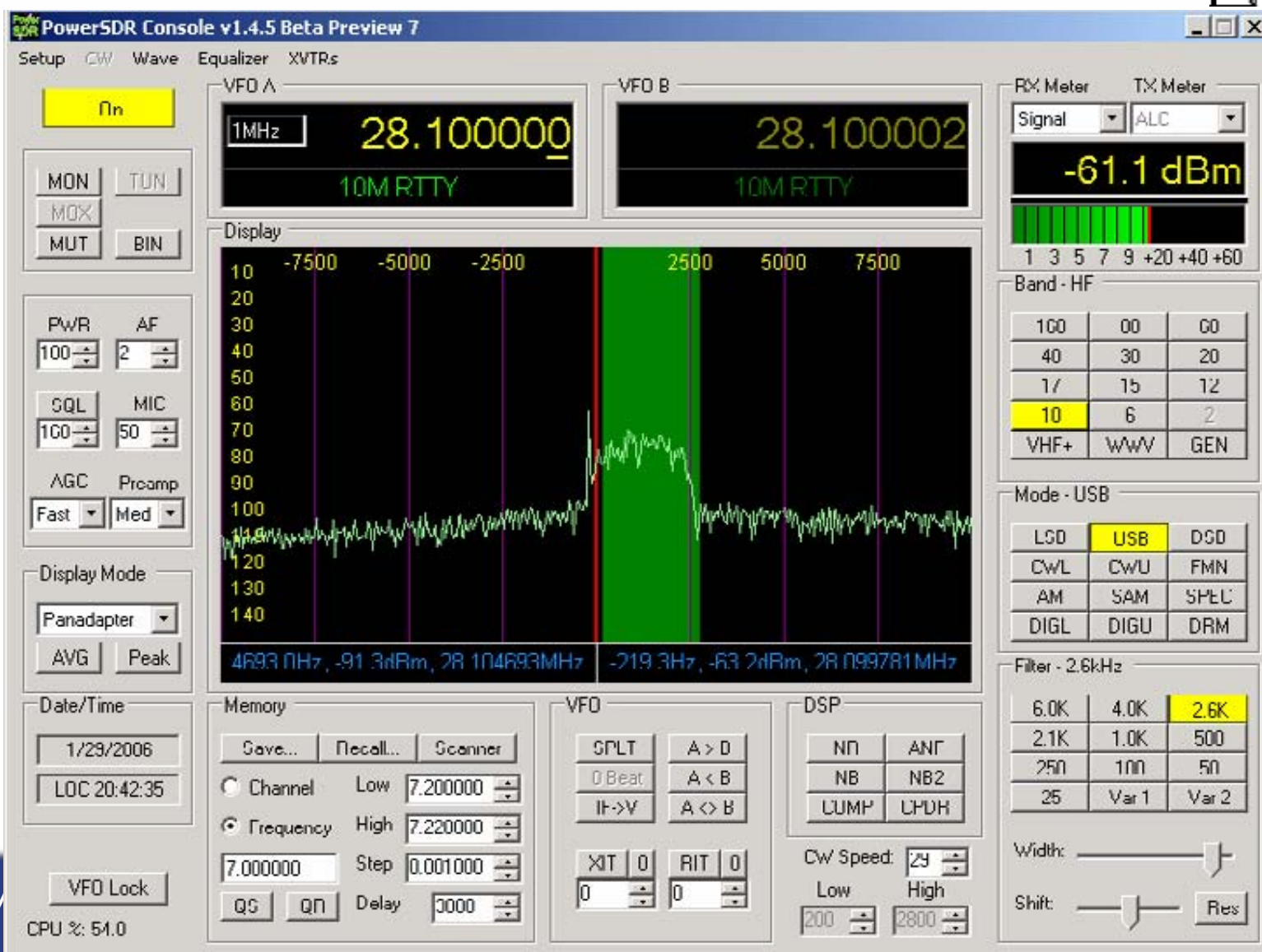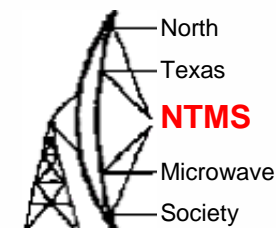





# KA5BOU Overloading my Sound Card!

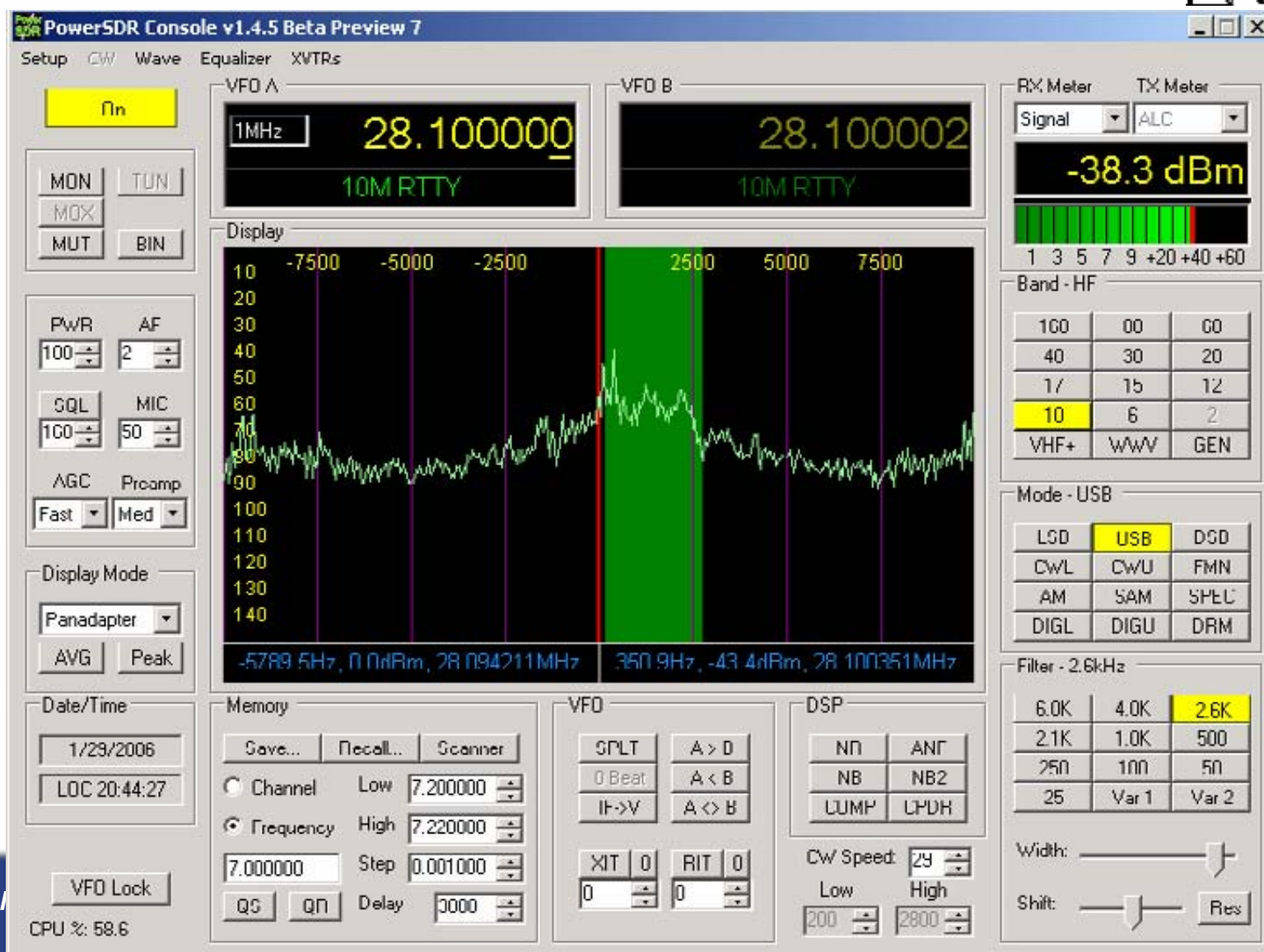
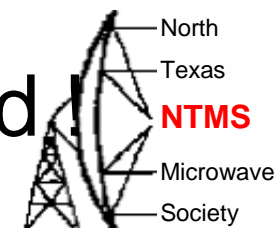





# NM5M On 1296.100 MHz USB

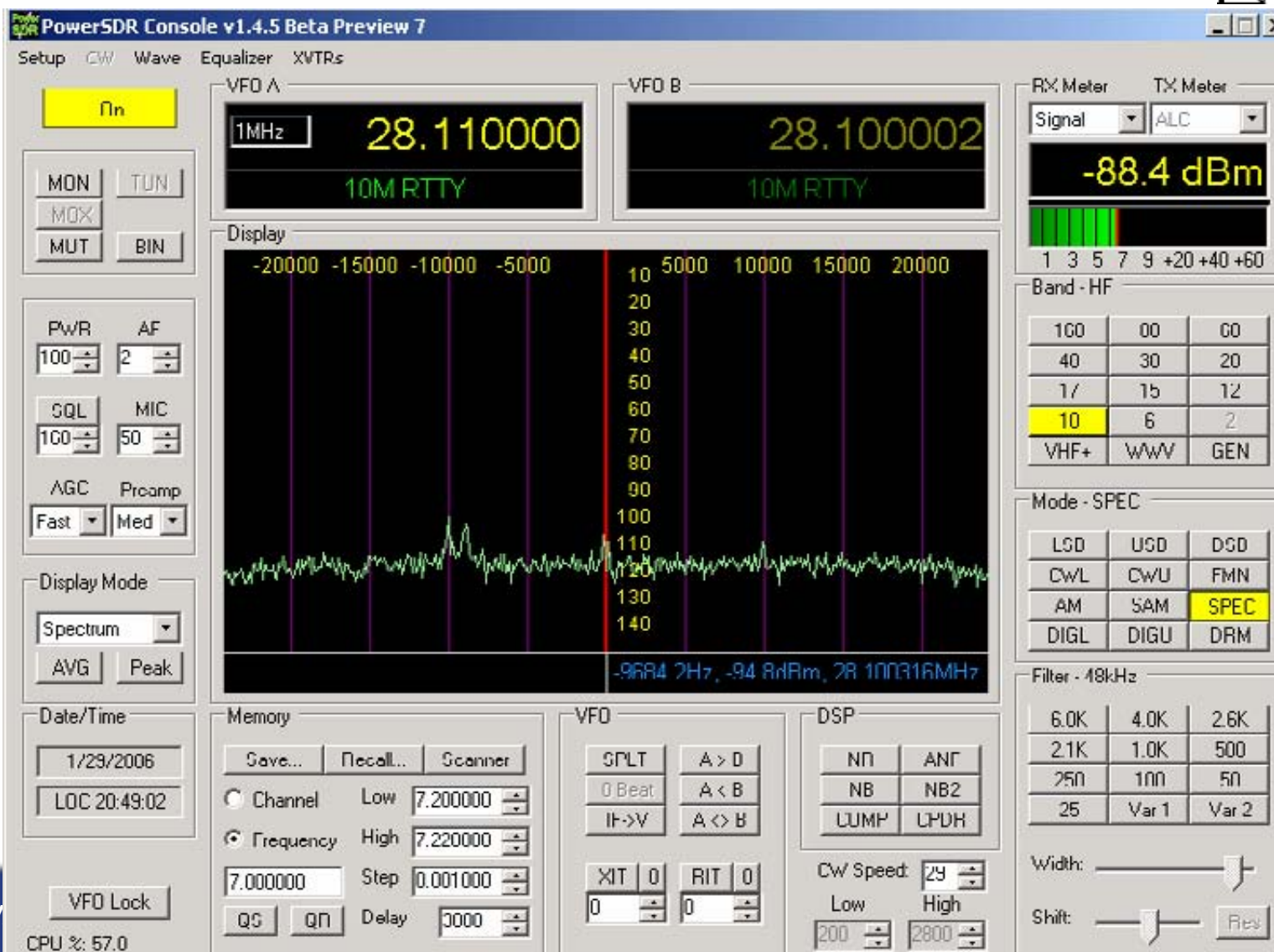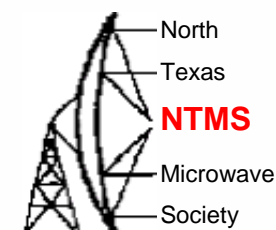

# NM5M on 1296.100 MHz SSB

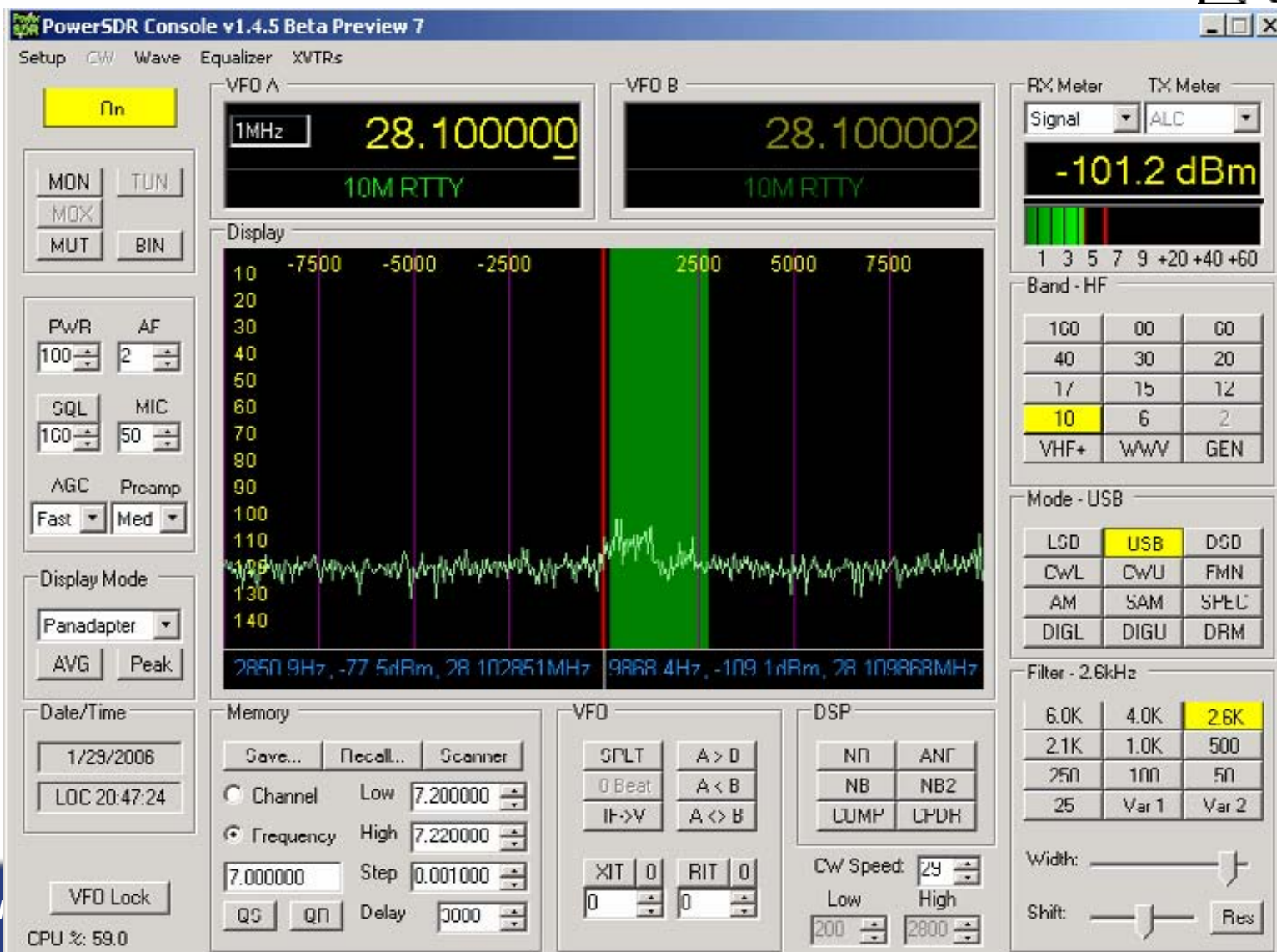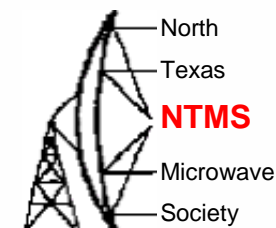

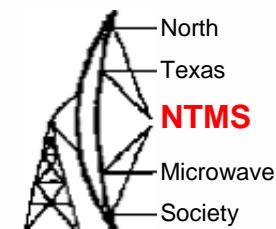
# A Recent Post from the Soft Rock 40 Yahoo User's Group



- SoftRock v5.0 OSC/BPF kits are now available for bands other than 40 and 20 meters. I have a limited supply of the band kits as follows:
  - > 160m with center frequency at 1.8432 MHz
  - > 80m with center frequency at 3.560 MHz
  - > 30m with center frequency at 10.125 MHz
  - > 17m with center frequency at 18.096 MHz
  - > 15m with center frequency at 21.06 MHz
  - > 12m with center frequency at 24.906 MHz
  - > 10m with center frequency at 28.06 MHz
  - > Each kit is complete with circuit board, crystal and all other components including BPF caps for the specific band.
  - > Bands at frequencies greater than 14.06 MHz are still considered experimental as we evaluate the performance the SoftRock will provide on these bands. Test data will be posted as soon as possible for the higher frequency bands.
  - > Due to the limited number of kits, (small quantity parts purchased more expensive), I need to ask a little more for these kits at \$9.50 (US/Canada) and \$10.50 (DX). If you would just like the crystal for a band and the associated BPF components including the cores and wire, that sub-kit can be purchased for \$4 (\$4.50 for DX). All prices include the mailing costs.
  - > Please check with me before you enter a PayPal order to make sure I still have a kit for the band you are interested in.
  - > Thanks and 73,
  - > Tony KB9YIG

raparks@ctcisp.com

<http://www.dxatlas.com/Rocky/>

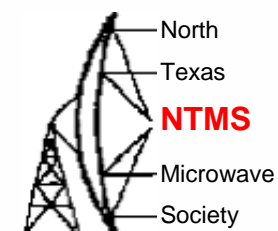


# Rocky 1.41

FREEWARE

by Alex VE3NEA




ve3nea@dxatlas.com

SDR software for SoftRock40

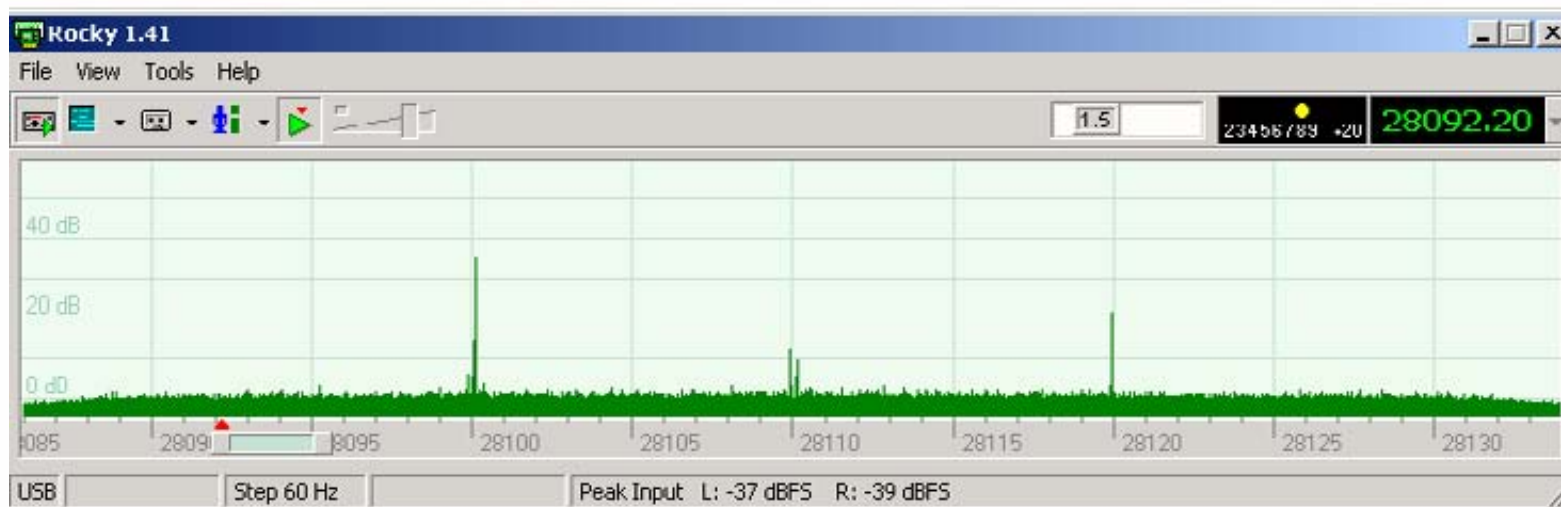



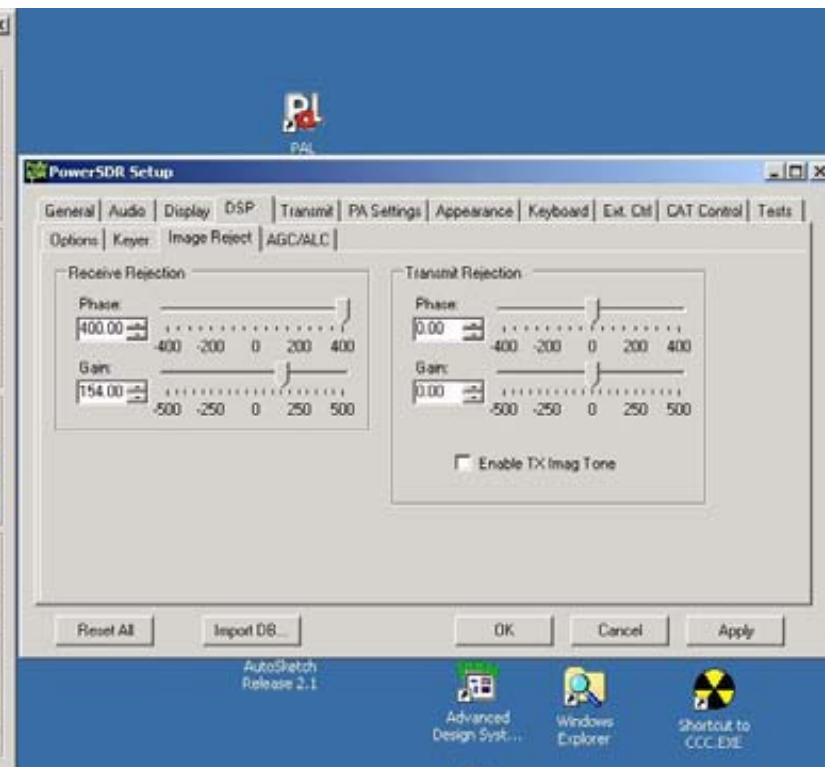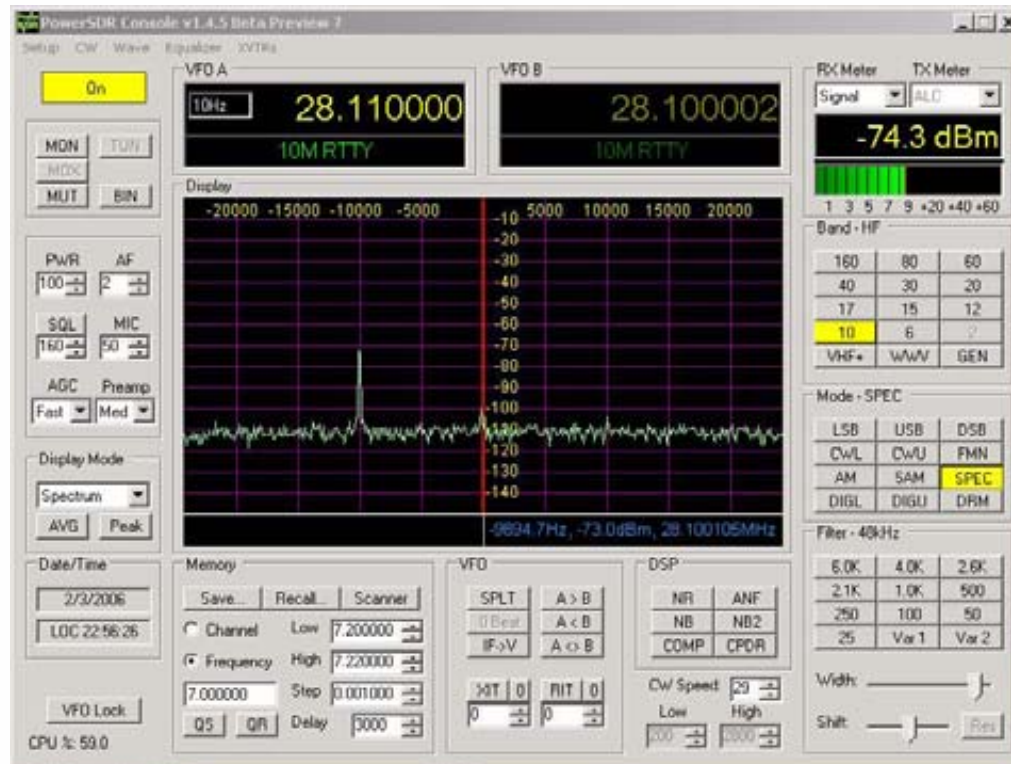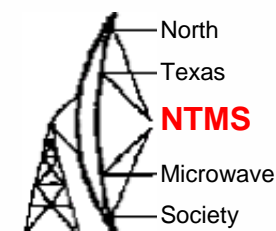
# Optimizing I & Q Amplitude and Phase for best Image Rejection



# Summary

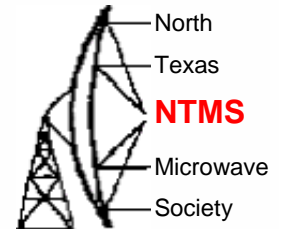

- Great for a microwave IF spectrum analyzer – Frequency coverage is crystal frequency plus and minus 24 kHz
- Software is free!
- Receiver can become a well calibrated small signal power meter for the lab
- With the DDS-60, the combination can provide receive coverage from 1 to 60 MHz – only need to provide front-end BPF if connected to antenna
- Can also be set up as a spectrum analyzer at the first IF frequency of your favorite “rice-box” radio at a fraction of the cost of an IC-756pro, IC7800 and IC-9000
- Transmitter mate to the SR5 in the works by the QRP guys
- Hard to imagine all the neat stuff they can do in software today and to think our soundcards are 48 kHz wide receivers!
- Any questions?